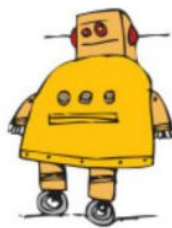


## instructables CN5711 Driving LED with Arduino or Potentiometer Instructions

[Home](#) » [instructables](#) » [instructables CN5711 Driving LED with Arduino or Potentiometer Instructions](#) 



**instructables**

### CN5711 Driving LED with Arduino or Potentiometer Instructions

#### Contents

- [1 CN5711 Driving LED with Arduino or Potentiometer](#)
- [2 Step 1: Datasheet](#)
- [3 Step 2: Drive the Led With the Built in Potentiometer](#)
- [4 Step 3: Drive the Led With a Microcontroller](#)
- [5 Step 4: Diy Version](#)
- [6 Step 5: See You Soon!](#)
- [7 Documents / Resources](#)
  - [7.1 References](#)
- [8 Related Posts](#)

### CN5711 Driving LED with Arduino or Potentiometer

#### How to Drive a Led With Arduino or Potentiometer (CN5711)



by dariocose

I like LEDs, especially for personal projects, like making torches and lights for my bike. In this tutorial I will explain the operation of a simple into drive leds that meets my needs:

- $V_{in} < 5V$  to use a single lithium battery or USB
- possibility to vary the current with a potentiometer or with a microcontroller
- simple circuit, few components and small footprint

I hope this little guide will be useful to other users!

### **Supplies:**

### **Components**


- Led driver module
- Any power led (I used 1 watt red led with 60° lens)
- Battery or power supply
- Breadboard
- Components

### **For the diy version:**

- CN5711 IC
- Potentiometer
- Prototype Board
- SOP8 to DIP8 pcb or SOP8 to DIP8 adapter

### **Tools**

- Soldering iron
- Screwdriver

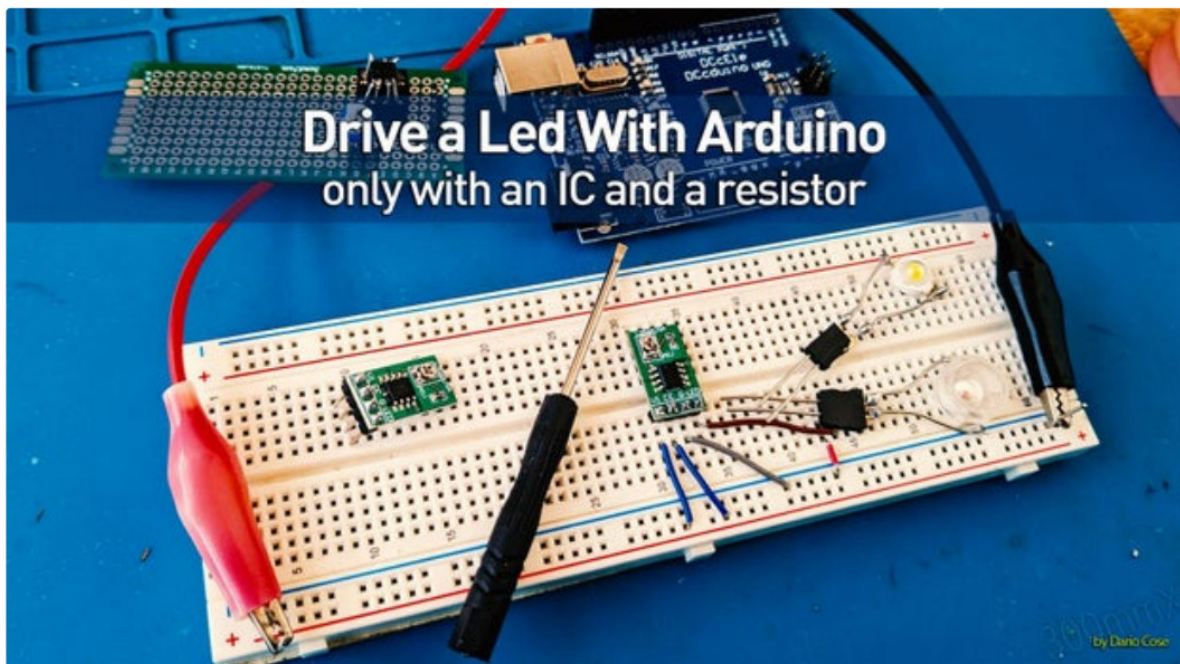

### **Step 1: Datasheet**

A few months ago I found on Aliexpress a led driver module composed of a CN5711 IC, a resistor and a variable resistor.

From the CN5711 datasheet:

#### **General Description:**

General Description: The CN5711 is a current regulation integrated circuit operating from an input voltage of 2.8V to 6V, the constant output current can be set up to 1.5A with an external resistor. The CN5711 is ideal for driving LEDs. [...] The CN5711 adopts the temperature regulation instead of temperature protection function, the temperature regulation can make the LED being turned on continuously in case of high ambient temperature or high voltage drop. [...]

**Applications:** Flashlight, High-brightness LED driver, LED headlights, Emergency lights and lighting [...]

**Features:** Operating Voltage Range: 2.8V to 6V, On-chip Power MOSFET, Low Dropout Voltage: 0.37V @ 1.5A, LED Current up to 1.5A, Output Current Accuracy:  $\pm 5\%$ , Chip Temperature Regulation, Over LED Current Protection [...]

There are 3 modes of operation for this IC:

1. With a PWM signal directly applied to the CE pin, the frequency of the PWM signal should be less than 2KHz
2. With a logic signal applied to the gate of an NMOS (Figure 4)
3. With a potentiometer (Figure 5)

Using the PWM signal it is very easy to drive the IC with a microcontroller like Arduino, Esp32 and AtTiny85.

#### **General Description**

The CN5711 is a current regulation integrated circuit operating from an input voltage of 2.8V to 6V, the constant output current can be set up to 1.5A with an external resistor. The CN5711 is ideal for driving LED. The on-chip power MOSFET and current sense block greatly reduce the number of external component count. The CN5711 adopts the temperature regulation instead of temperature protection function, the temperature regulation can make the LED being turned on continuously in case of high ambient temperature or high voltage drop. Other features include chip enable, etc. CN5711 is available in thermally-enhanced 8-pin small outline package (SOP8).

#### **Features**

- Operating Voltage Range: 2.8V to 6V
- On-chip Power MOSFET
- Low Dropout Voltage: 0.37V @ 1.5A
- LED Current up to 1.5A
- Output Current Accuracy:  $\pm 5\%$
- Chip Temperature Regulation
- Over LED Current Protection
- Operating Temperature Range:  $-40^{\circ}\text{C}$  to  $+85^{\circ}\text{C}$
- Available in SOP8 Package
- Pb-free, RoHS Compliant, Halogen Free

#### **Applications**

- Flashlight
- High-brightness LED driver
- LED headlights
- Emergency lights and lighting

## Pin Assignment



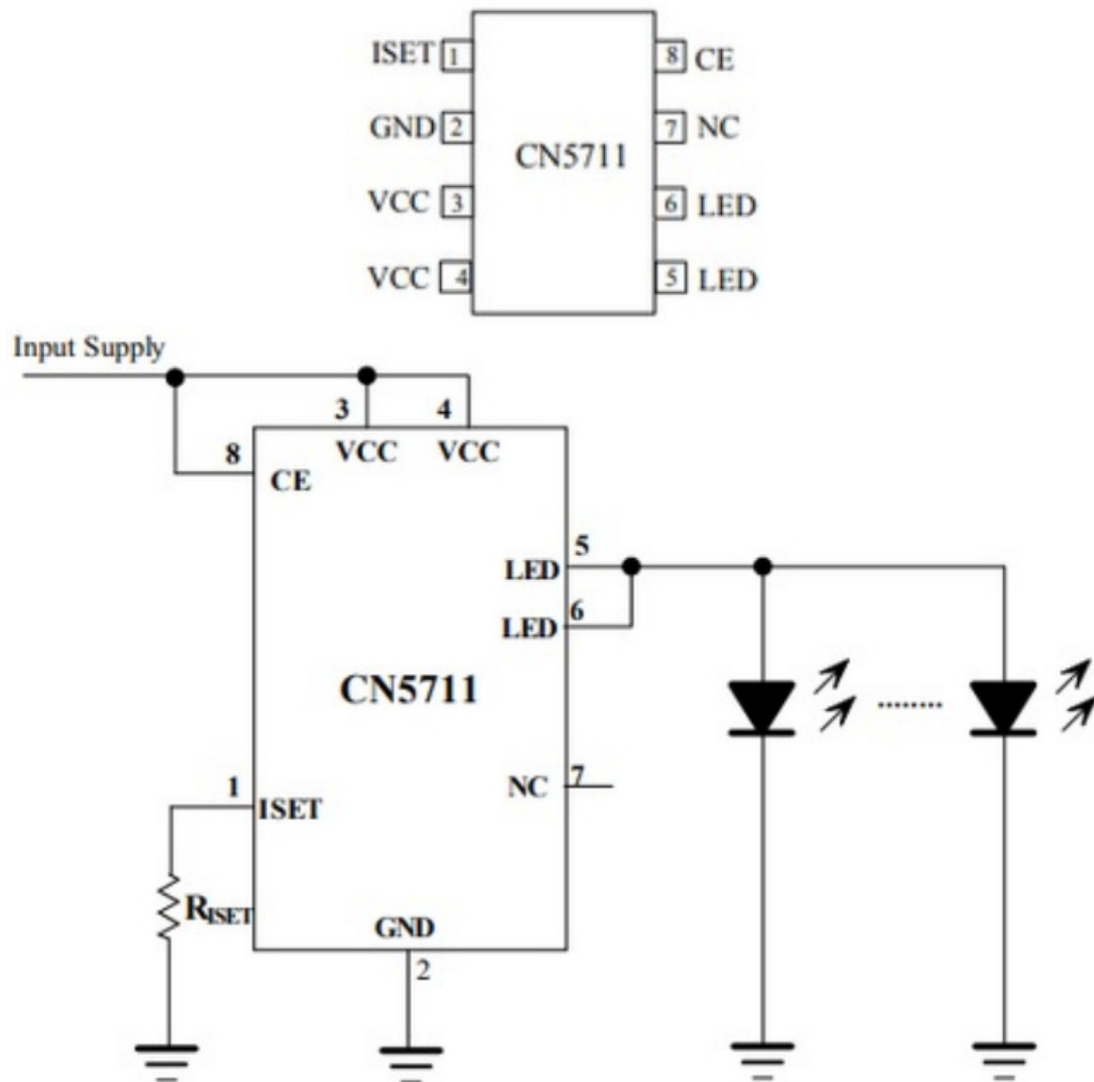


Figure 3. CN5711 drives LEDs in Parallel

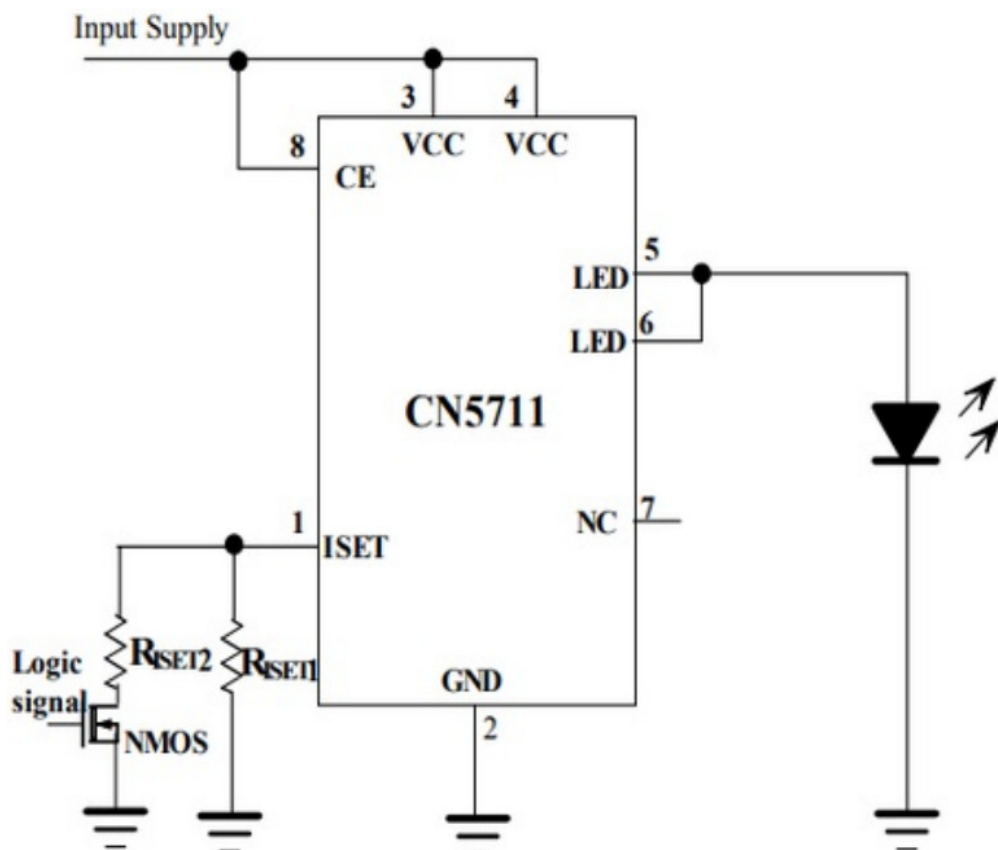

#### Figure 4 A logic signal to Dim LED

**Method 3:** A potentiometer is used to dim the LED as shown in Figure 5.

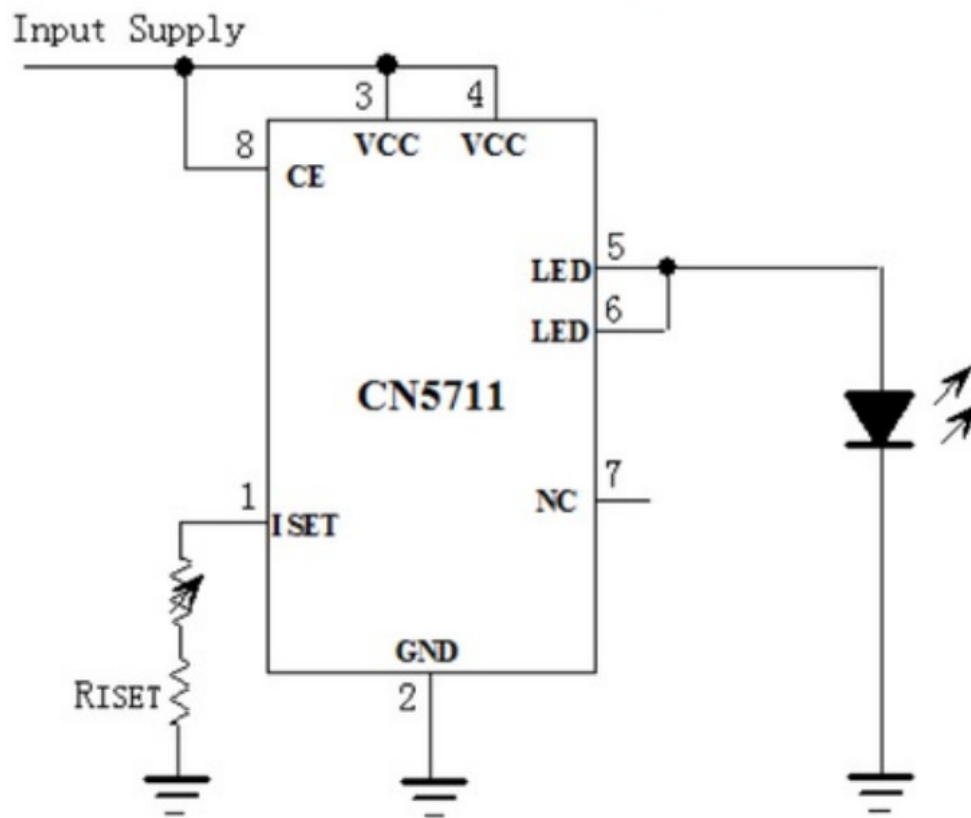

**Figure 5 A Potentiometer to Dim the LED**

#### Step 2: Drive the Led With the Built in Potentiometer

I hope the wiring is clear i n the photos and video.

V1 >> blue >> power supply +

CE >>blue >> power supply +


G >> gray >> ground

LED >> brown >> led +

To power the circuit I used a cheap power supply (made with an old atx power supply and a ZK-4KX buck boost converter) . I set the voltage to 4.2v to simulate a single cell lithium battery.


As we can see from the video, the circuit powers from 30mA to more than 200mA

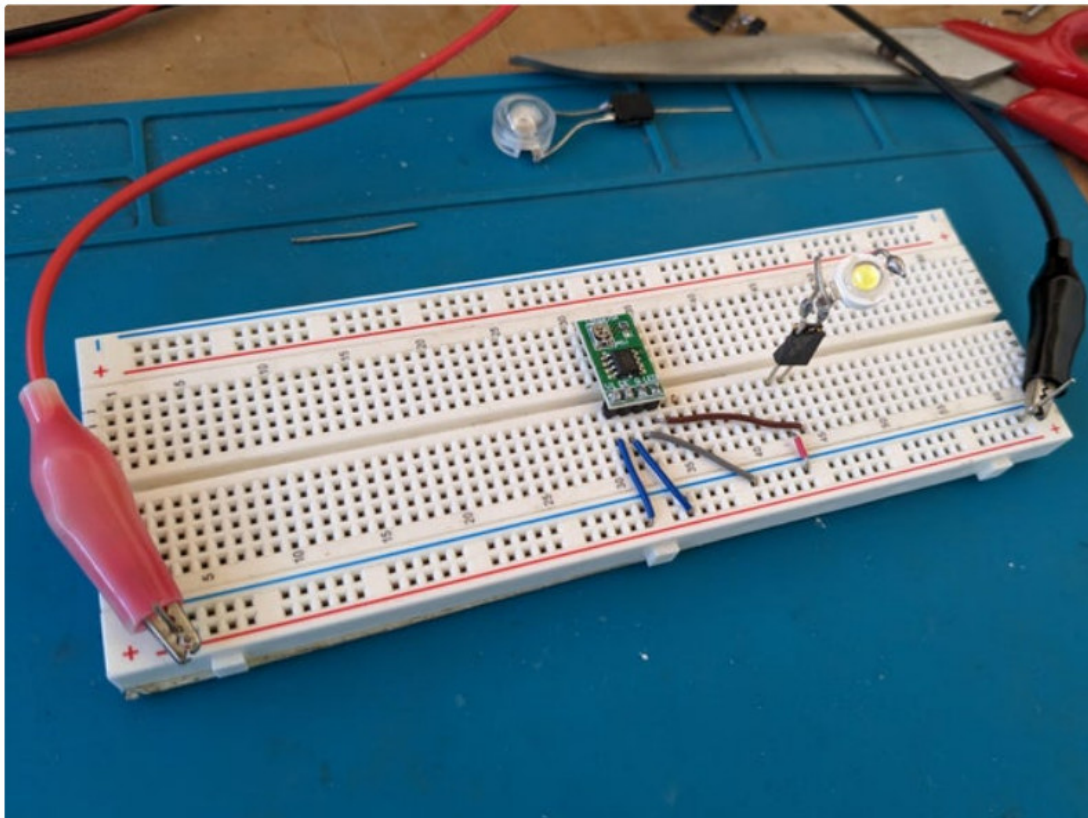[https://youtu.be/kLZUsOy\\_Opg](https://youtu.be/kLZUsOy_Opg)




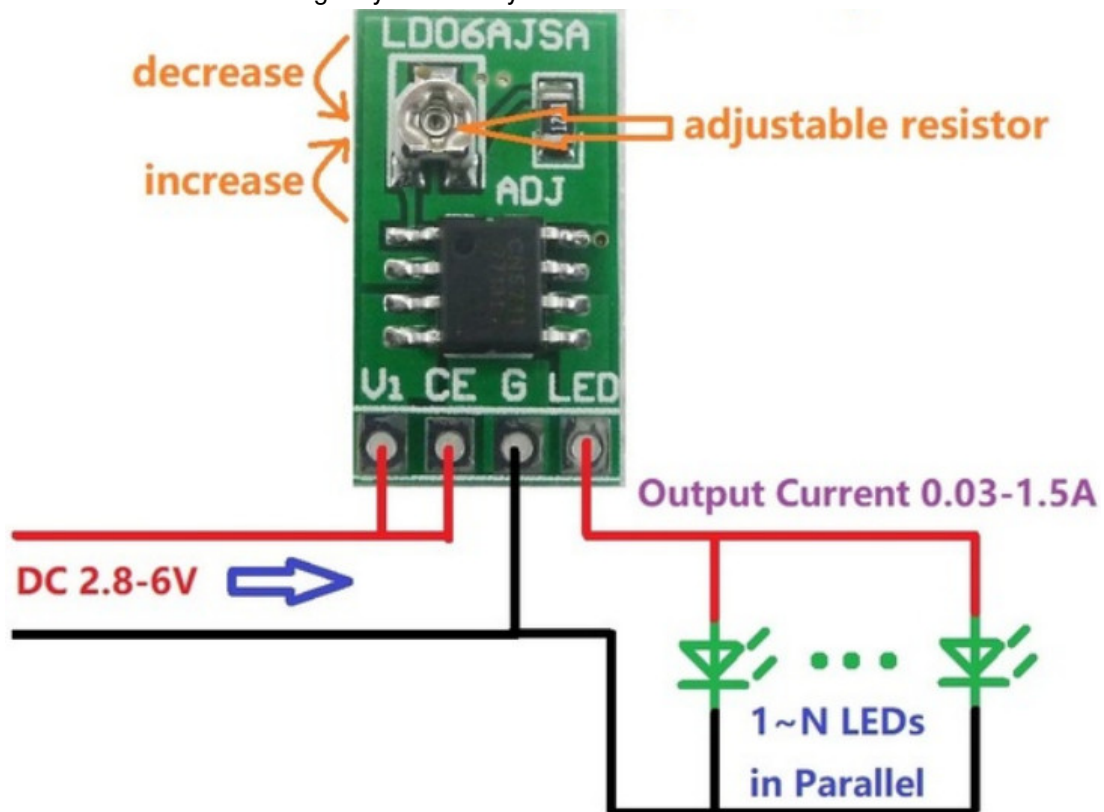
### Adjustable current through adjustable resistor.

Please use a suitable screwdriver to gently and slowly rotate





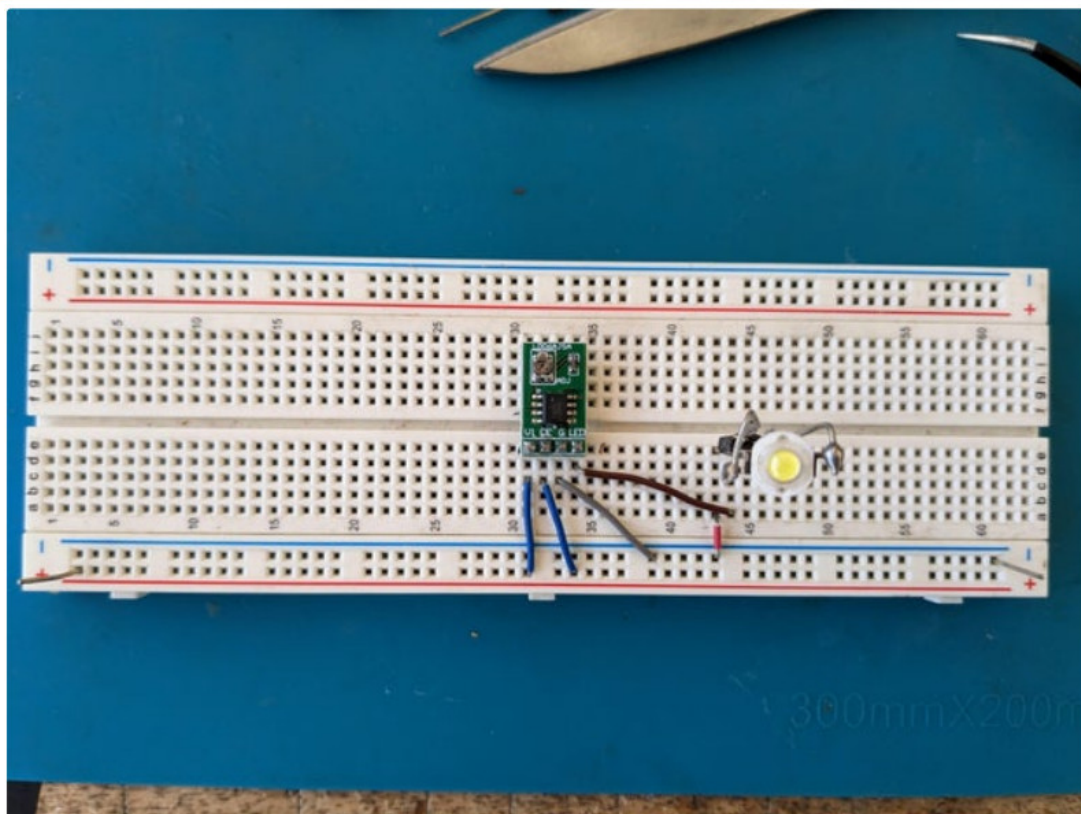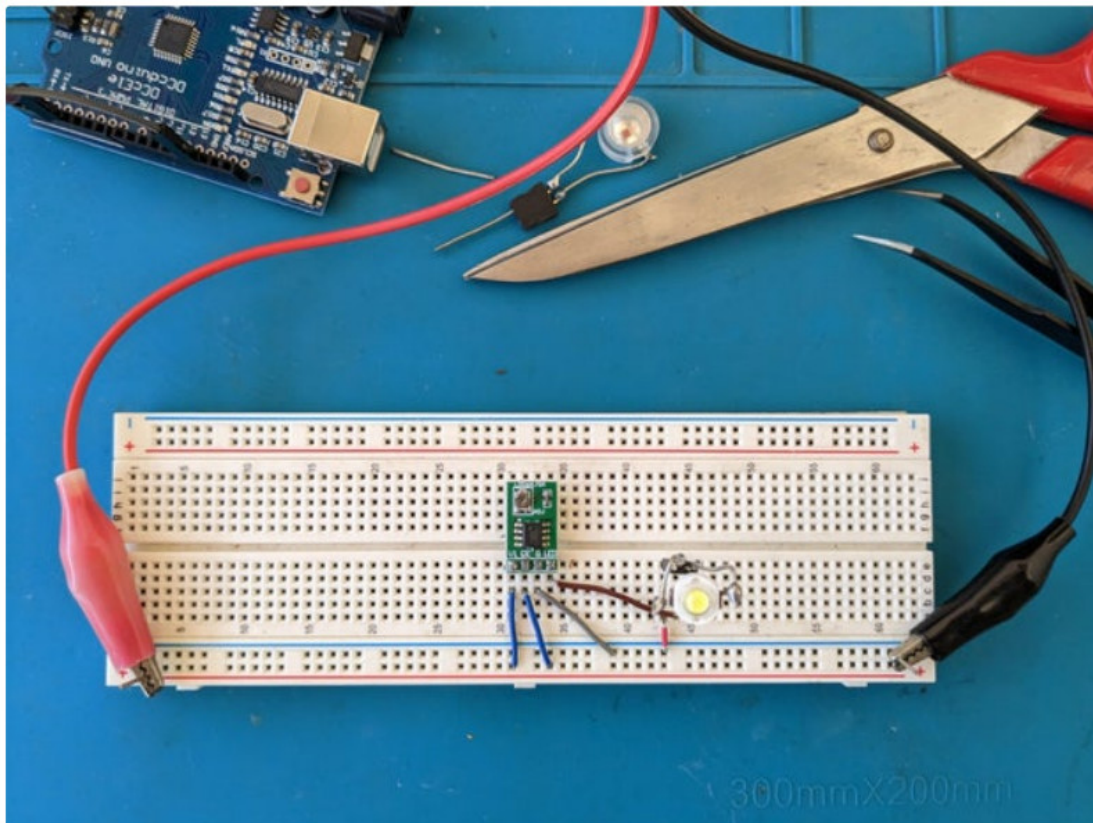

### Step 3: Drive the Led With a Microcontroller

To control the circuit with a microcontroller just connect the CE pin to the PWM pin of the microcontroller.

V1 >> blue >> power supply +

CE >> purple >> pwm pin

G >> gray >> ground

LED >> brown >> led +


Setting the duty cycle to 0 (0%) the LED will turn off. Setting the duty cycle to 255 (100%) the LED will light up at maximum power. With a few lines of code we can adjust the brightness of the LED.

In this section you can download a test code for Arduino, Esp32 and AtTiny85.



Arduino test code:

```
#define pinLed 3
#define led Off 0
#define led On 255 //255 is the maximum pwm value
int value = 0 ; //pwm value
void setup() {
  pinMode(pinLed, OUTPUT); //setto il pin pwm come uscita
}
void loop () {
  //blink
  analog Write(pinLed, led Off); // Turn off led
  delay(1000);
  // Wait a second
  analog Write(pinLed, led On); // Turn on led
  delay(1000);
  // Wait a second
  analog Write(pinLed, led Off); //...
  delay(1000);
  analog Write(pinLed, led On);
  delay(1000);
  //dim
  for (value = ledOn; value > ledOff; value --) { //decrease the light by decreasing "value"
    analog Write(pinLed, value);
    delay(20);
  }
  for (value = ledOff; value < ledOn; value ++ ) { //increase the light by increasing "value"
    analog Write(pinLed, value);
    delay(20);
  }
}
```

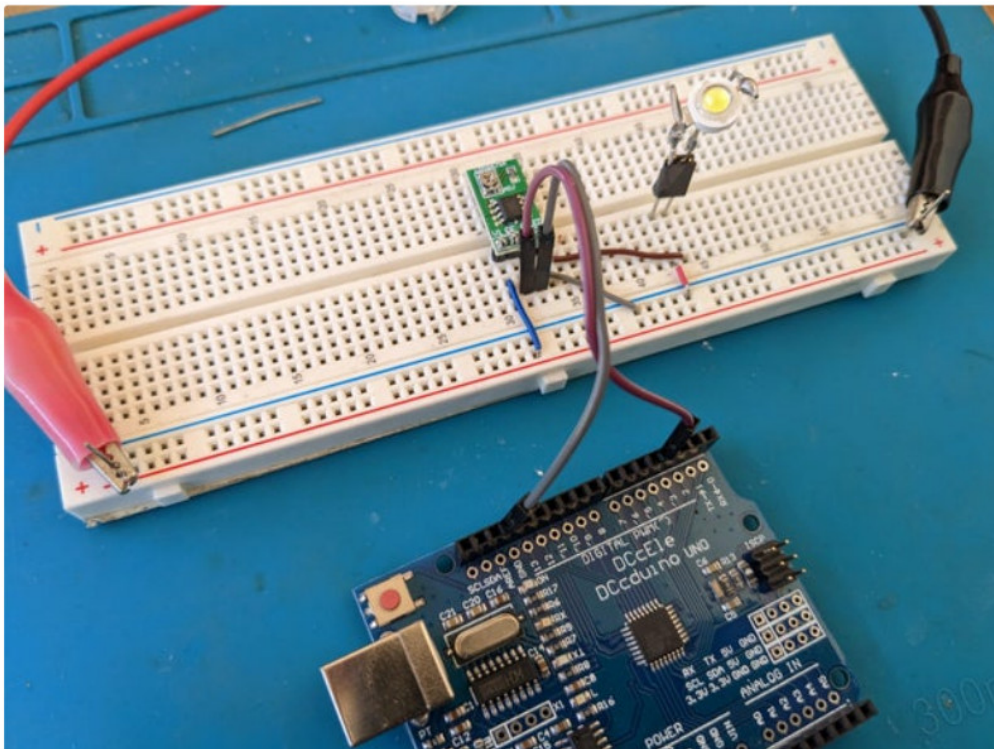[https://youtu.be/\\_6SwgEA3cuJg](https://youtu.be/_6SwgEA3cuJg)





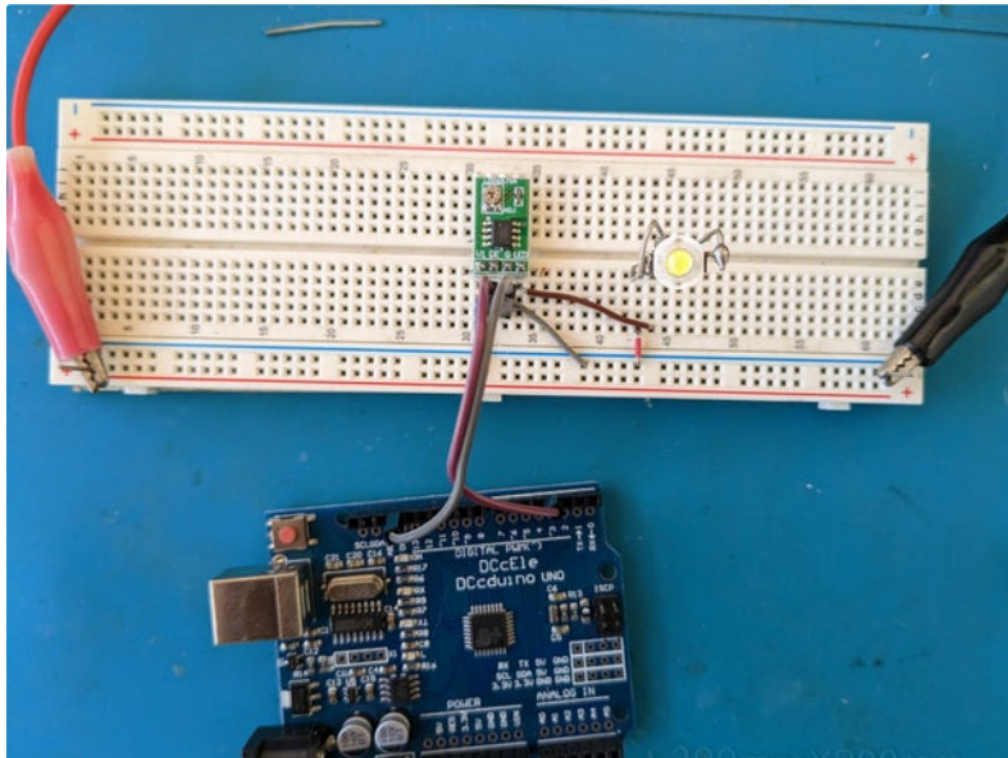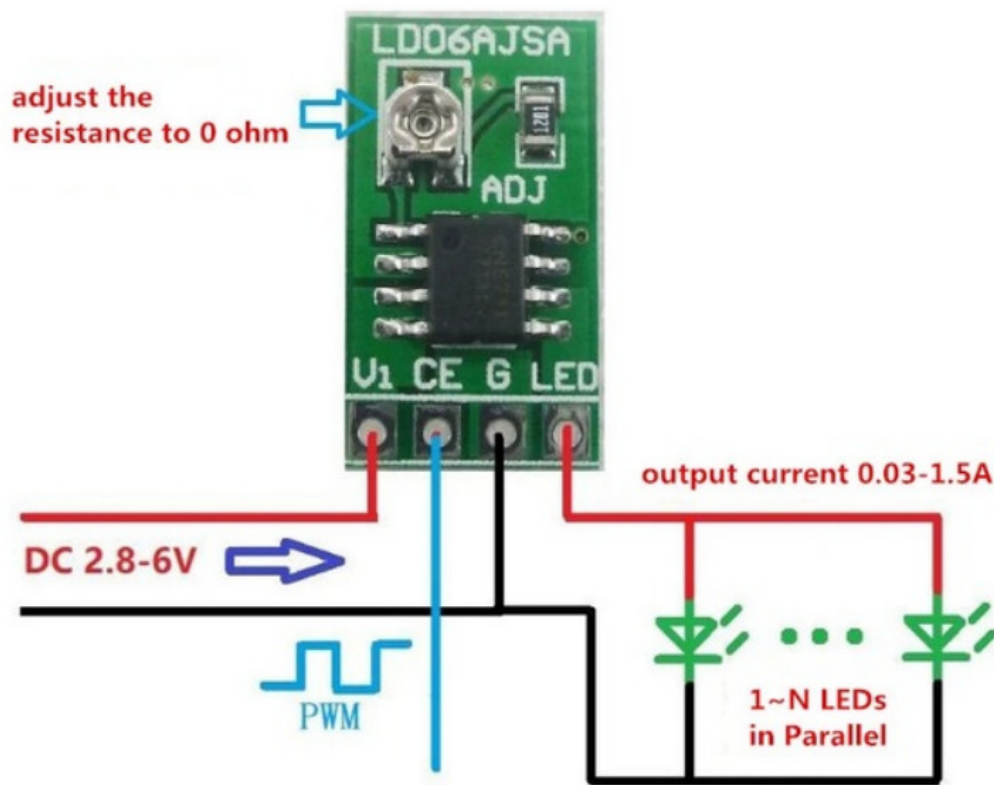



<https://www.instructables.com/FJV/WYFF/LDSTSONV/FJVVYFFLDSTSSNV.ino>  
<https://www.instructables.com/F4F/GUYU/LDSTS9NW/F4FGUYULDSTS9SNW.ino>  
<https://www.instructables.com/FXD/ZBY3/LDSTS9NX/FXDZBY3LDSTS9NX.ino>


Download  
 Download  
 Download
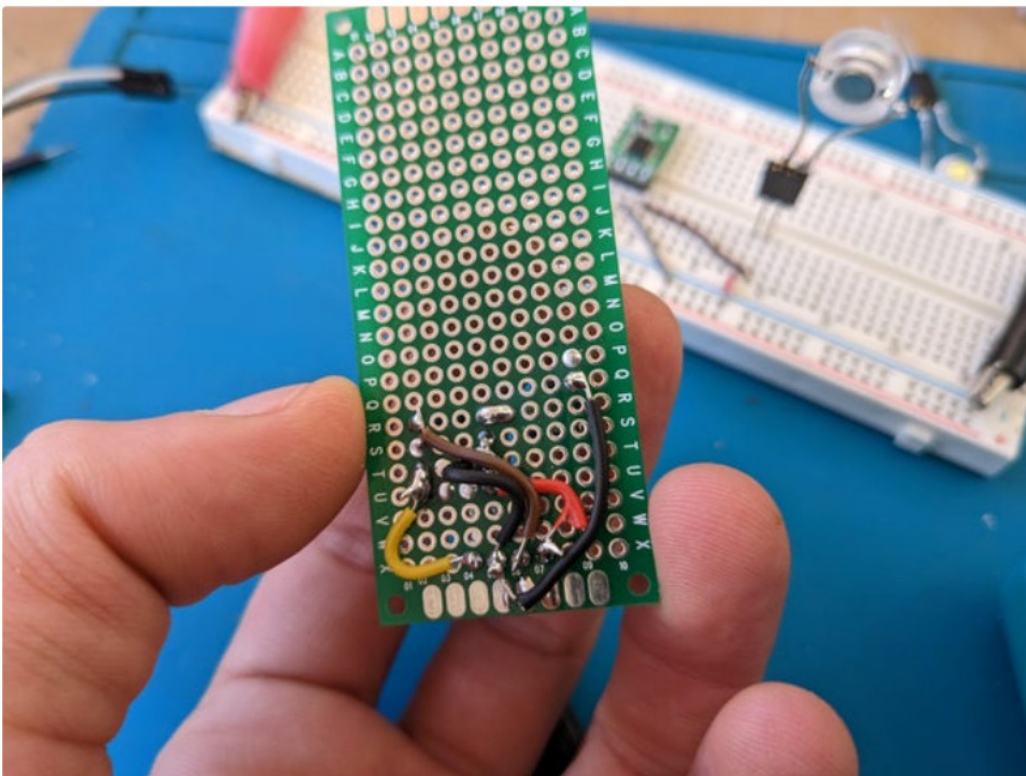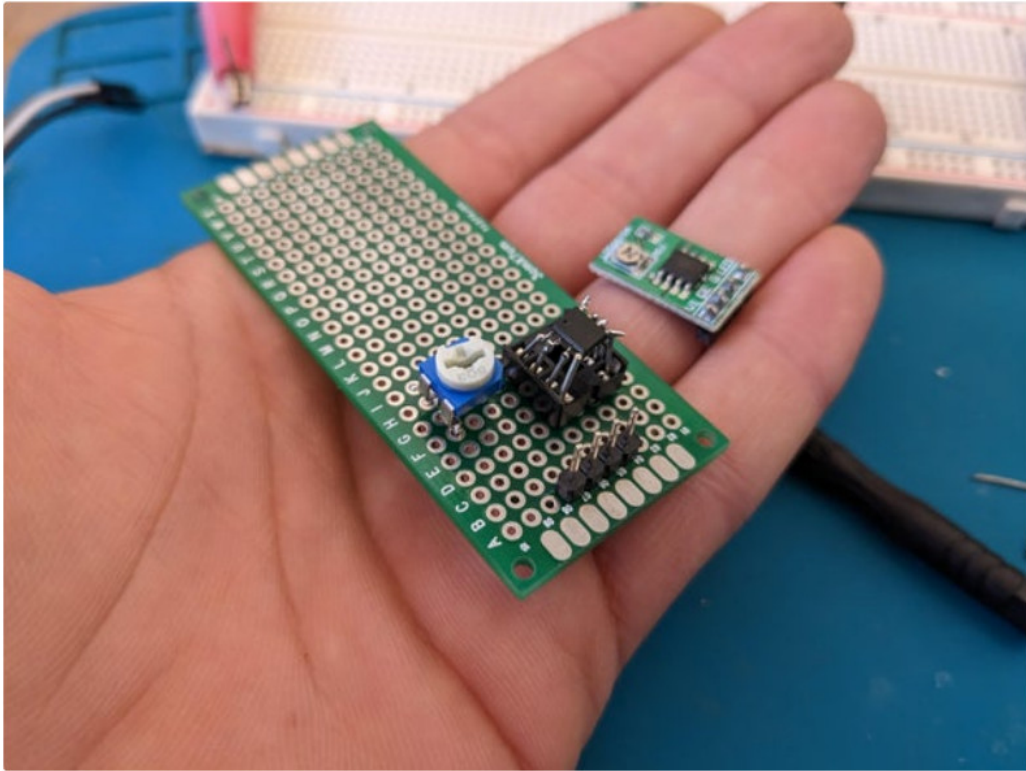
#### Step 4: Diy Version

I made a diy version of the module following the standard datasheet circuit.  
 I used a 50k potentiometer even though the datasheet says the “R-ISET’s maximum value is 30K ohm”.  
 As you can see the circuit is not very clean...  
 I should have used SOP8 to DIP8 pcb or SOP8 to DIP8 adapter for a more elegant circuit!

I hope to share a gerber file soon that you can use.



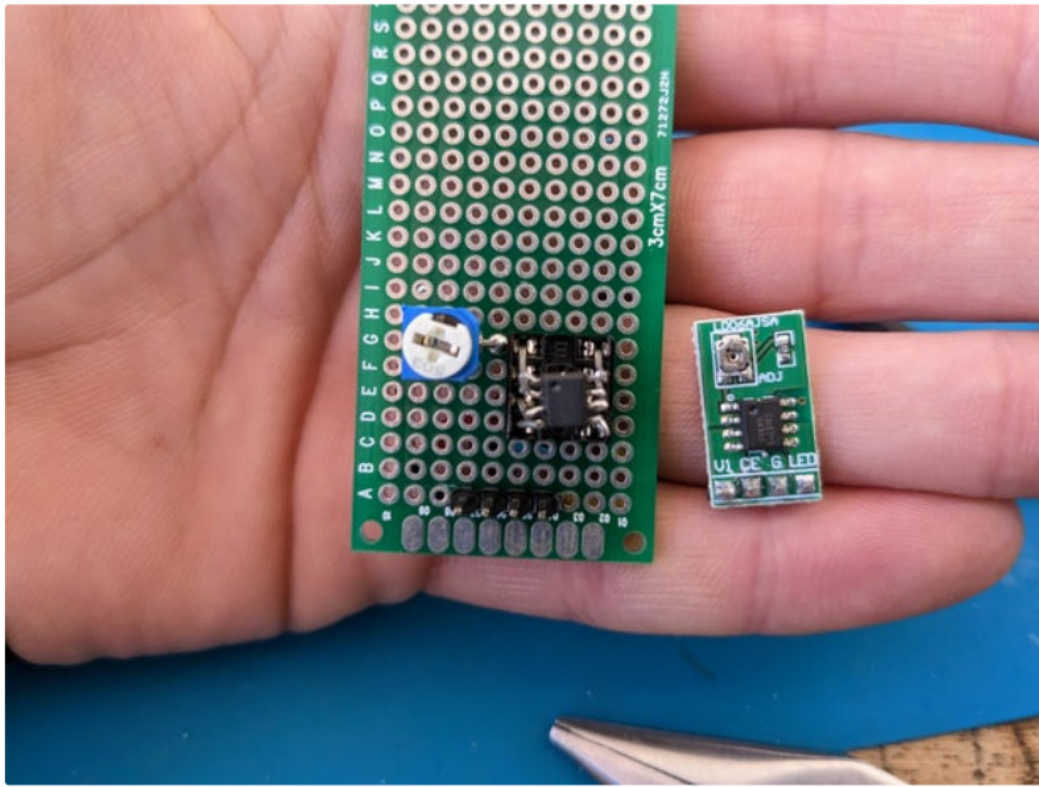

## Step 5: See You Soon!

Please leave me your impressions with a comment and report technical and grammatical errors! Support me and my projects at this link <https://allmylinks.com/dariocose>



Nice work!

I did see one technical grammar error that could cause some confusion. At the end of step 2 you say: "As we can see from the video, the circuit powers from 30mAh to more than 200mAh"

That should say "30 mA to 200 mA."

The term mAh means "milliamps times hours and is an energy measurement, not a current measurement. Fifteen milliamps for 2 hours or 5 milliamps for 6 hours are both 30 mAh.


Nicely written instruct able!

Thanks!



You are right! Thanks for your advice!


I correct immediately!

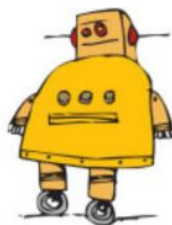










**instructables**

**Documents / Resources**



	<p><a href="#">instructables CN5711 Driving LED with Arduino or Potentiometer</a> [pdf] Instructions CN5711, CN5711 Driving LED with Arduino or Potentiometer, Driving LED with Arduino or Potentiometer</p>
--	--

## References

-  [Yours for the making - Instructables](#)
-  [How to Drive a Led With Arduino or Potentiometer \(CN5711\) : 5 Steps \(with Pictures\) - Instructables](#)
-  [Dariocose's Profile - Instructables](#)
-  [Dario Cose \(@dariocose\) | AllMyLinks](#)
-  [content.instructables.com/F4F/GUYU/LDSTS9NW/F4FGUYULDSTS9NW.ino](#)
-  [content.instructables.com/FJV/WYFF/LDSTS9NV/FJWYFFLDSTS9NV.ino](#)
-  [content.instructables.com/FXD/ZBY3/LDSTS9NX/FXDZBY3LDSTS9NX.ino](#)
-  [s.click.aliexpress.com/e/\\_Dem7d77](#)
-  [s.click.aliexpress.com/e/\\_DFI8pE1](#)

Manuals+,