

## **instructables Design a Functional ECG With Automated Plotting of the Biosignal Instructions**


[Home](#) » [instructables](#) » instructables **Design a Functional ECG With Automated Plotting of the Biosignal Instructions** 

## Contents

- 1 [instructables Design a Functional ECG With Automated Plotting of the Biosignal](#)
- 2 [Design a Functional ECG With Automated Plotting of the Biosignal](#)
- 3 [Documents / Resources](#)
  - 3.1 [References](#)
- 4 [Related Posts](#)


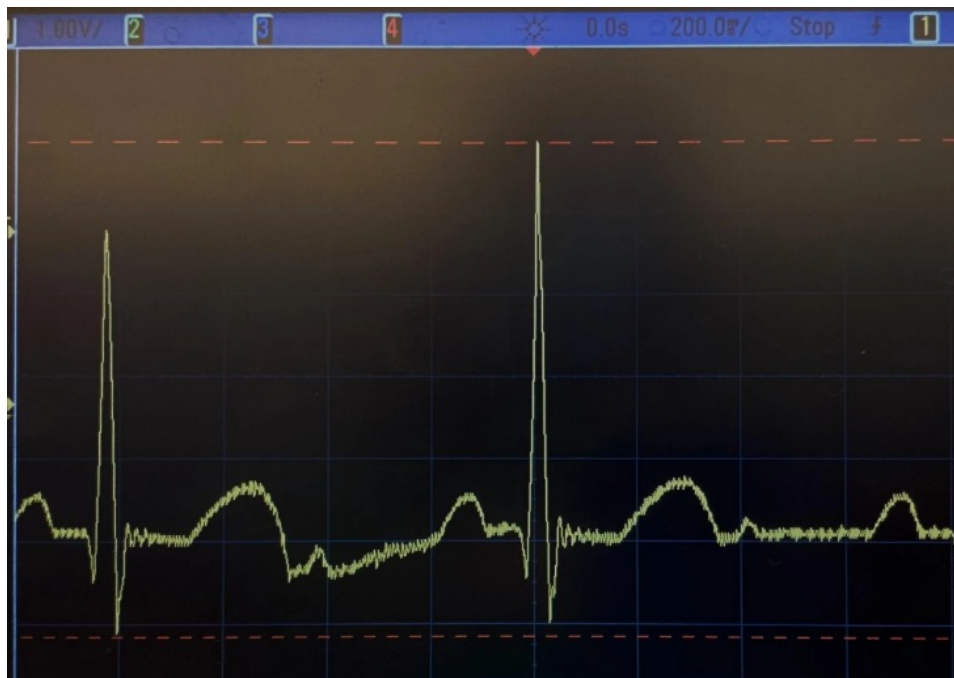
## instructables Design a Functional ECG With Automated Plotting of the Biosignal




## Design a Functional ECG With Automated Plotting of the Biosignal

This project combines everything learned this semester and applies it to one single task. Our task is to create a circuit that is able to be used as an electrocardiogram (ECG) by using an instrumentation amplifier, lowpass filter, and notch filter. An ECG uses electrodes placed on an individual to measure and display the heart activity. Calculations were made based on the average adult heart, and the original circuit schematics were created on LTSpice to verify gain and cutoff frequencies. The objectives of this design project are as follows:

1. Apply instrumentation skills learned in lab this semester
2. Design, build, and verify the functionality of a signal acquisition device
3. Validate the device on a human subject
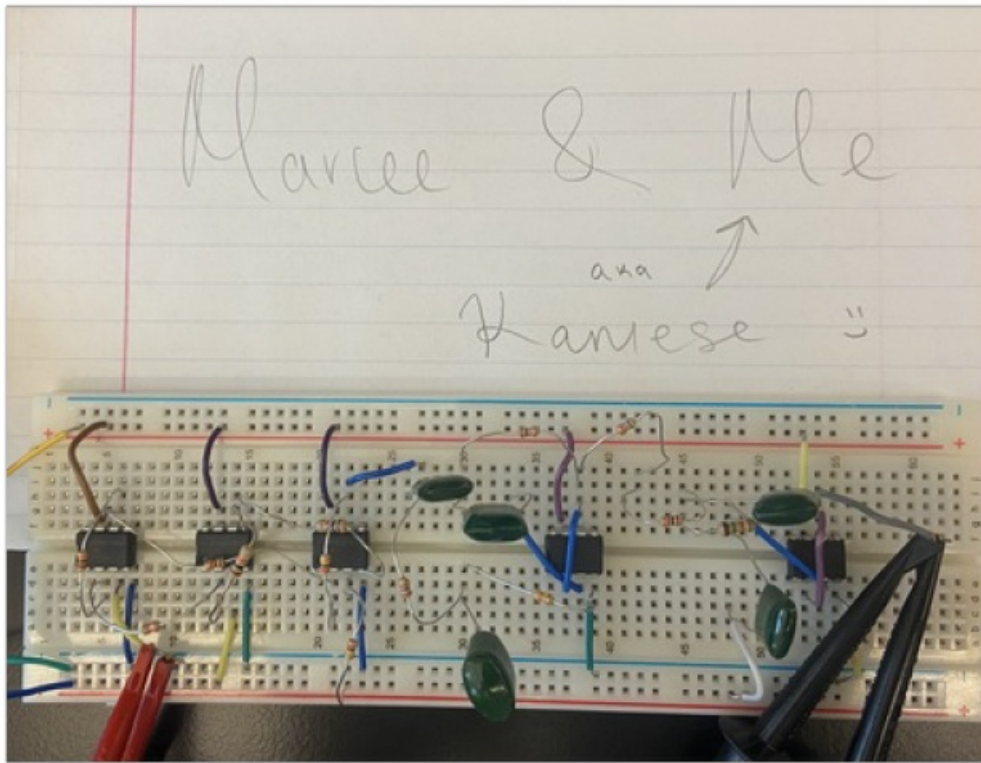
### Supplies:

- LTSpice simulator (or similar software) Breadboard
- Various resistors
- Various capacitors
- Opamps
- Electrode wires
- Input voltage source
- Device to measure output voltage (i.e. oscilloscope)



### Step 1: Make the Calculations for Each Circuit Component

The images above show the calculations for each circuit. Below, it explains more about the components and the calculations done.

#### Instrumentation Amplifier

An instrumentation amplifier, or IA, helps provide a large amount of gain for low-level signals. It helps increase the size of the signal so it's more visible and the waveform can be analyzed.

For calculations, we chose two random resistor values for R1 and R2, which are 5 kΩ and 10 kΩ, respectively. We also want the gain to be 1000 so the signal will be easier to analyze. The ratio for R3 and R4 are then solved for by the following equation:

$$V_{out} / (V_{in1} - V_{in2}) = [1 + (2 \cdot R_2 / R_1)] \cdot (R_4 / R_3) \rightarrow R_4 / R_3 = 1000 / [1 + 2 \cdot (10) / (5)] \rightarrow R_4 / R_3 = 200$$

We then used that ratio to decide what each resistor value will be. The values are as follows:

$$R_3 = 1 \text{ k}\Omega$$

#### Notch Filter

A notch filter attenuates signals within a narrow band of frequencies or removes a single frequency. The frequency we want to remove in this case is 60 Hz because most noise produced by electronic devices is at that frequency. A Q factor is the ratio of the center frequency to bandwidth, and it also helps describe the shape of the magnitude plot. A larger Q factor results in a narrower stop band. For calculations, we will be using a Q value of 8. We decided to choose capacitor values we had. So, C1 = C2 = 0.1 uF, and C2 = 0.2 uF.

The equations we will be using to calculate R1, R2, and R3 are as follows:

$$R_1 = 1 / (4 \cdot \pi \cdot Q \cdot f \cdot C_1) = 1 / (4 \cdot \pi \cdot 8 \cdot 60 \cdot 0.1 \text{E-}6) = 1.6 \text{ k}\Omega$$

$$R_2 = (2 \cdot Q) / (2 \cdot \pi \cdot f \cdot C_1) = (2 \cdot 8) / (2 \cdot \pi \cdot 60 \cdot 0.1 \text{E-}6) = 424 \text{ k}\Omega$$

$$R_3 = (R_1 \cdot R_2) / (R_1 + R_2) = (1.6 \cdot 424) / (1.6 + 424) = 1.6 \text{ k}\Omega$$

#### Lowpass Filter

A low pass filter attenuates high frequencies while allowing lower frequencies to pass through. The cutoff frequency will have value of 150 Hz because that is the correct ECG value for adults. Also, the gain (K value) will be 1, and constants a and b are 1.414214 and 1, respectively.

We chose C1 to equal 68 nF because we had that capacitor. To find C2 we used the following equation:

$$C_2 \geq (C_1^2 \cdot b) / [a^2 + 4 \cdot b \cdot (K-1)] = (68 \text{E-}9^2 \cdot 4 \cdot 1) / [1.414214^2 + 4 \cdot 1 \cdot (1-1)] \rightarrow C_2 \geq 1.36 \text{E-}7$$


Therefore, we chose C2 to equal 0.15 uF

To calculate the two resistor values, we had to use the following equations:


$$R_1 = 2 / (2 \cdot \pi \cdot f \cdot [a \cdot C_2 + \sqrt{a^2 + 4 \cdot b \cdot (K-1)}] \cdot C_2^2 - 4 \cdot b \cdot C_1 \cdot C_2) = 7.7 \text{ k}\Omega$$

$$R_2 = 1 / (b \cdot C_1 \cdot C_2 \cdot R_1 \cdot (2 \cdot \pi \cdot f)^2) = 14.4 \text{ k}\Omega$$

## Instrumentation Amplifier

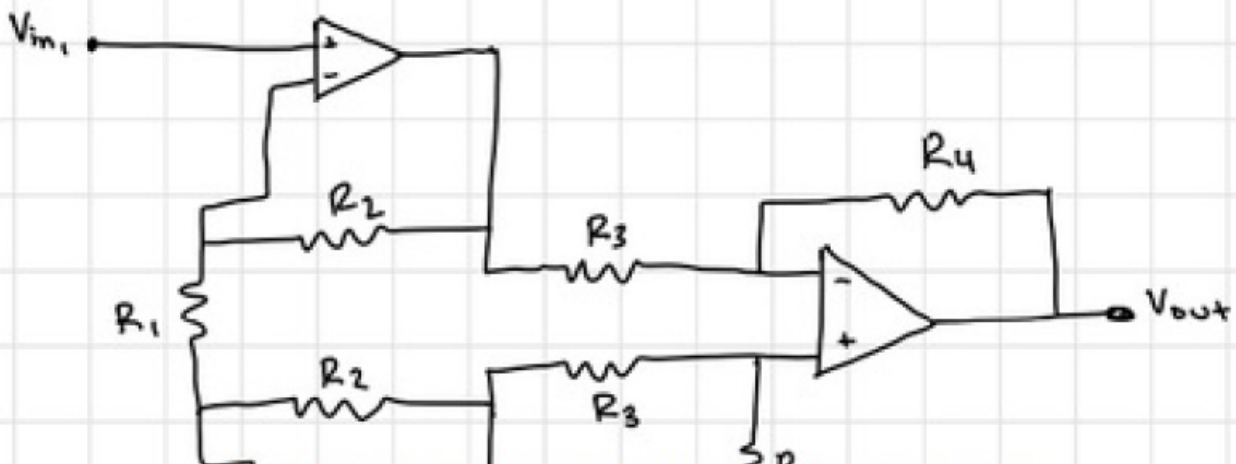

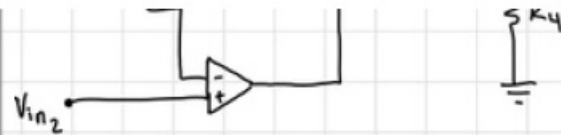Design a Functional ECG With Automated Plotting of the Biosignal: Page 3



$$R_1 = 5 \text{ k}\Omega$$

$$R_2 = 10 \text{ k}\Omega$$

$$\text{gain} = 1000$$


$$\frac{V_{out}}{V_{in2} - V_{in1}} = \text{gain} = \left(1 + \frac{2R_2}{R_1}\right) \left(\frac{R_4}{R_3}\right)$$

$$1000 = \left(1 + \frac{2(10)}{5}\right) \left(\frac{R_4}{R_3}\right)$$

$$\frac{R_4}{R_3} = 200 \rightarrow R_4 = 200 \text{ k}\Omega$$

$$R_3 = 1 \text{ k}\Omega$$

### Notch Filter

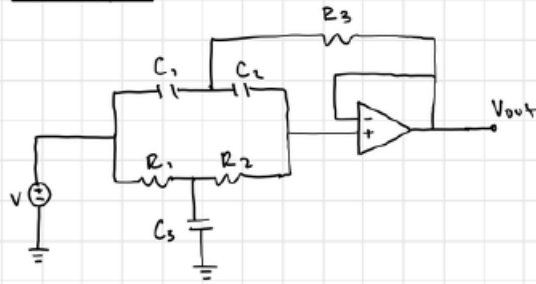

$$Q = 8$$

$$f_c = 60 \text{ Hz}$$

$$C_1 = C_2 = 0.1 \text{ mF}$$


$$C_3 = 0.2 \text{ mF}$$

$$R_1 = \frac{1}{4\pi f_c C_1 Q} = \frac{1}{4\pi (60)(0.1 \times 10^{-6})(8)} \rightarrow R_1 = 1.6 \text{ k}\Omega$$

$$R_2 = \frac{2Q}{2\pi f_c C_1} = \frac{8}{\pi (60)(0.1 \times 10^{-6})} \rightarrow R_2 = 424 \text{ k}\Omega$$

$$R_3 = \frac{R_1 R_2}{R_1 + R_2} = \frac{(1.6)(424)}{1.6 + 424} \rightarrow R_3 = 1.6 \text{ k}\Omega$$

### Low Pass

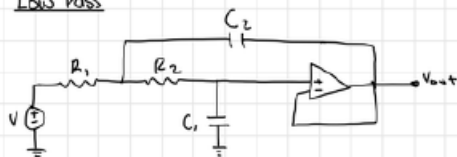

$$f_c = 150 \text{ Hz} \quad k = 1 \quad b = 1$$

$$C_1 = 68 \text{ nF} \quad a = 1.414214$$

$$C_2 \geq \frac{C_1 4b}{a^2 + 4b(k-1)}$$

$$C_1 \leq \frac{C_2 [a^2 + 4b(k-1)]}{4b}$$

$$68 \times 10^{-9} \leq \frac{C_2 [1.414214^2 + 4(1)(1-1)]}{4(1)} \rightarrow C_2 \geq 1.36 \times 10^{-7} \rightarrow C_2 = 0.15 \text{ mF}$$

$$R_1 = \frac{2}{2\pi f_c [aC_2 + \sqrt{[a^2 + 4b(k-1)]C_2^2 - 4bC_1C_2}]}$$

$$R_1 = \frac{2}{2\pi (150) [(1.414214)(0.15 \times 10^{-6}) + \sqrt{[1.414214^2 + 4(1)(1-1)](0.15 \times 10^{-6})^2 - 4(1)(68 \times 10^{-9})(0.15 \times 10^{-6})}]}$$

$$R_1 = 7.7 \text{ k}\Omega$$


$$R_2 = \frac{1}{bC_1C_2R_1(2\pi f_c)^2} = \frac{1}{(1)(68 \times 10^{-9})(0.15 \times 10^{-6})(7691)(2\pi \cdot 150)^2}$$

$$R_2 = 14.4 \text{ k}\Omega$$
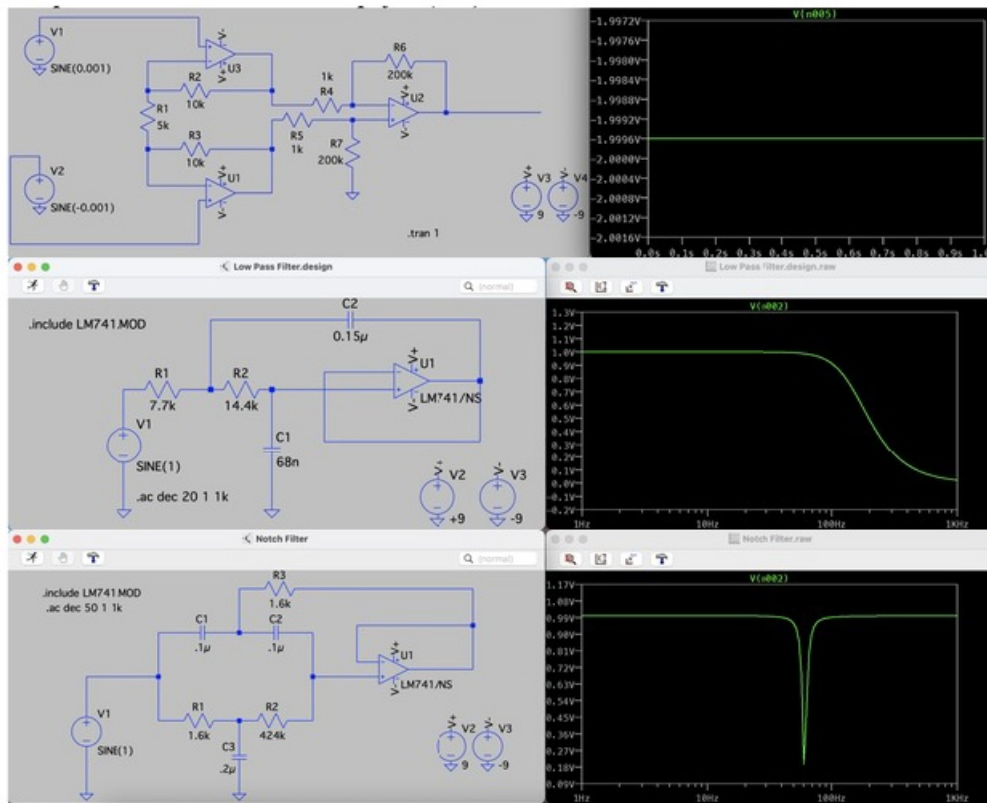
### Step 2: Create Schematics on LTSpice


All three components were created and ran individually on LTSpice with an AC sweep analysis. The values used are the ones we calculated in step 1.





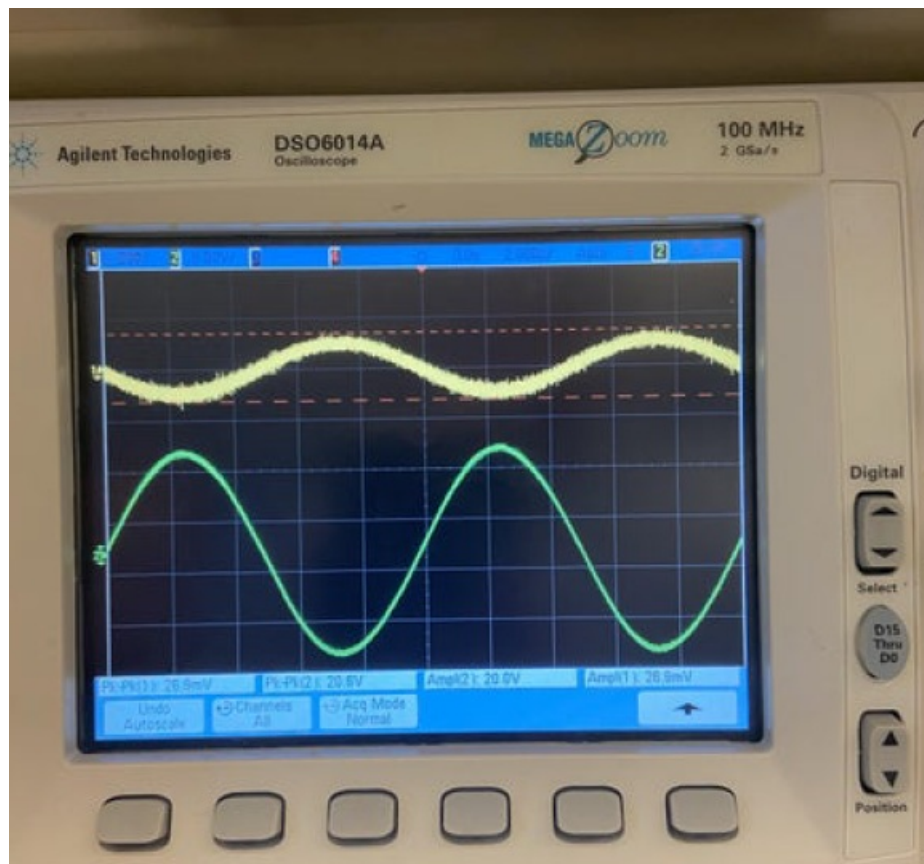
### Step 3: Build the Instrumentation Amplifier

We built the instrumentation amplifier on the breadboard by following the schematic on LTSpice. Once it was built, the input (yellow) and output (green) voltages were displayed. The green line only has a gain of 743.5X compared to the yellow line.





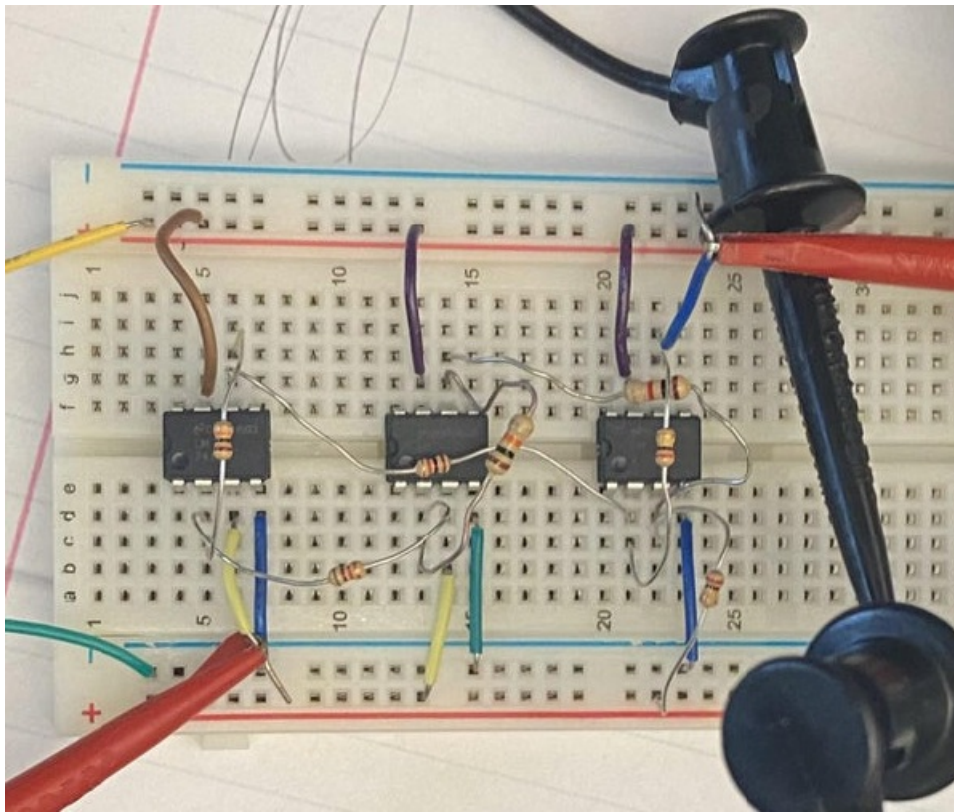

#### Step 4: Build the Notch Filter

Next, we built the notch filter on the breadboard based on the schematic made on LTSpice. It was built next to the IA circuit. We then recorded input and output voltage values at various frequencies to determine the magnitude. Then, we graphed magnitude vs. frequency on the plot to compare it to the LTSpice simulation. The only thing we changed was the values of C3 and R2 which are 0.22  $\mu$ F and 430 k $\Omega$ , respectively. Again, the frequency it is removing is 60 Hz.

Frequency (Hz)	Vin (V)	Vout (V)	Magnitude
10	10.13	10.19	1.005923
20	10.13	10.13	1
30	10.13	10.06	0.99308983
40	10.13	10.06	0.99308983
45	10.13	9.94	0.98124383
50	10.13	9.56	0.94373149
55	10.13	7.94	0.78381046
56	10.5	7.2	0.68571429
57	10.6	5.9	0.55660377
58	10.5	3.9	0.37142857
59	10.5	1.06	0.10095238
60	10.13	1.88	0.18558736
61	10.5	4.13	0.39333333
62	10.5	5.81	0.55333333
63	10.5	6.94	0.66095238
64	10.5	8	0.76190476
65	10.5	8.4	0.8
70	10.5	9.7	0.92380952
75	10.5	10	0.95238095
80	10.5	10	0.95238095

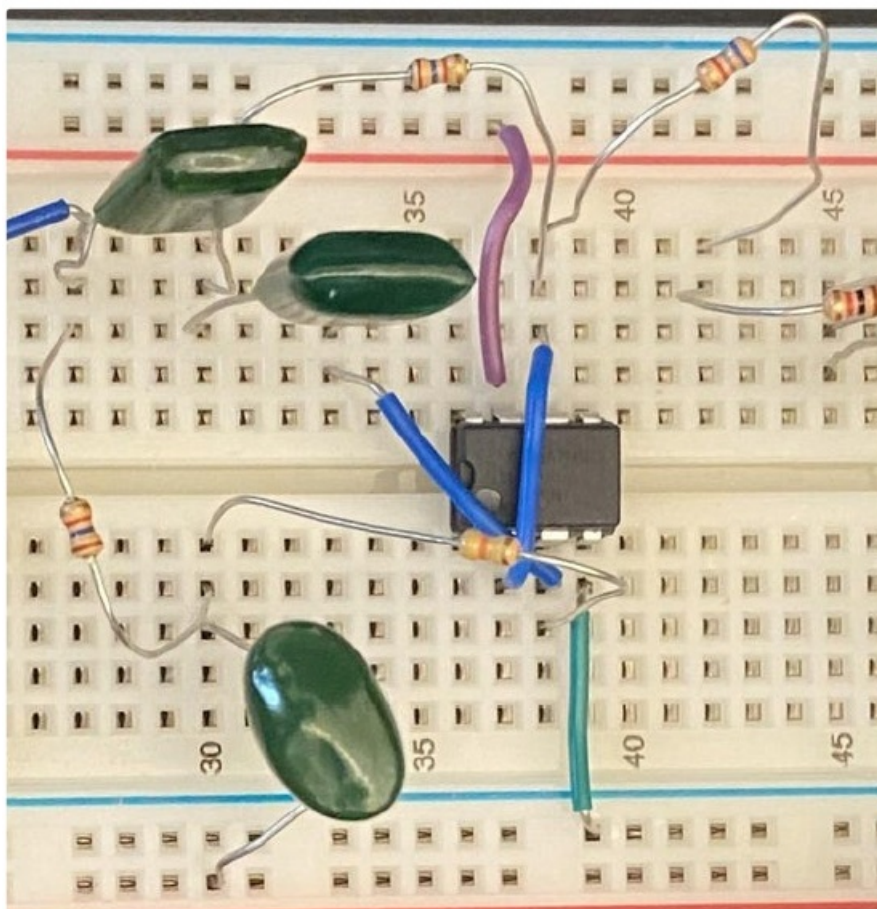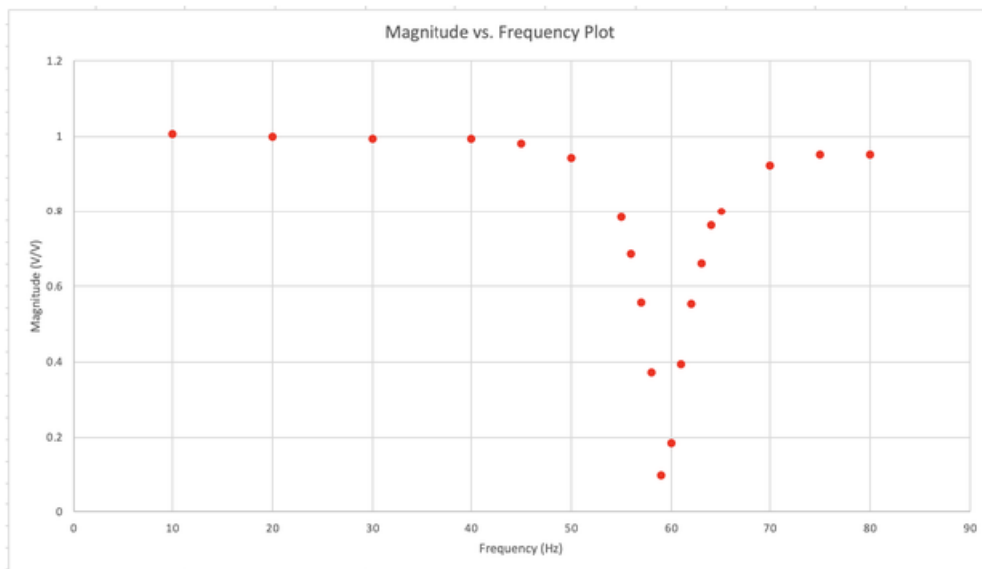


#### Step 5: Build the Lowpass Filter


We then built the low pass filter on the breadboard based on the schematic on LTSpice next to the notch filter. We then recorded the input and output voltages at various frequencies to determine the magnitude. Then, we plotted the magnitude and frequency to compare it to the LTSpice simulation. The only value we changed for this filter was C2 which is 0.15  $\mu\text{F}$ . The cutoff frequency we were verifying is 150 Hz.



Frequency (Hz)	Vin (V)	Vout (V)	Magnitude
30	10.5	10.5	1
40	10.5	10.3	0.98095238
50	10.5	10.2	0.97142857
60	10.5	10.2	0.97142857
70	10.5	10	0.95238095
80	10.5	9.8	0.93333333
90	10.5	9.7	0.92380952
100	10.5	9.4	0.8952381
110	10.3	8.9	0.86407767
120	10.3	8.4	0.81553398
125	10.5	8.3	0.79047619
130	10.5	8	0.76190476
135	10.3	7.8	0.75728155
140	10.3	7.5	0.72815534
145	10.3	7.2	0.69902913
150	10.3	7.2	0.69902913
155	10.5	6.9	0.65714286
160	10.3	6.6	0.6407767
165	10.3	6.3	0.61165049
170	10.3	6.3	0.61165049
175	10.3	5.9	0.57281553
180	10.3	5.8	0.5631068
190	10.3	5.3	0.51456311

200	10.3	4.75	0.46116505
-----	------	------	------------

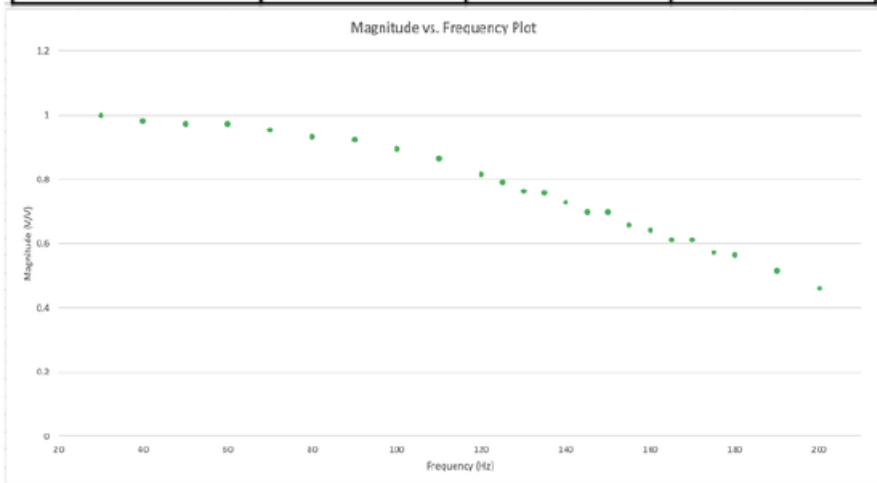


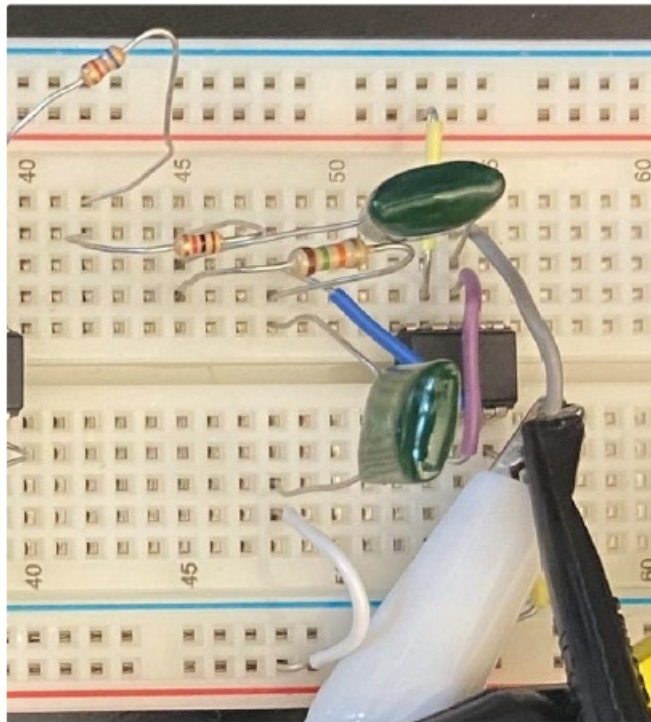

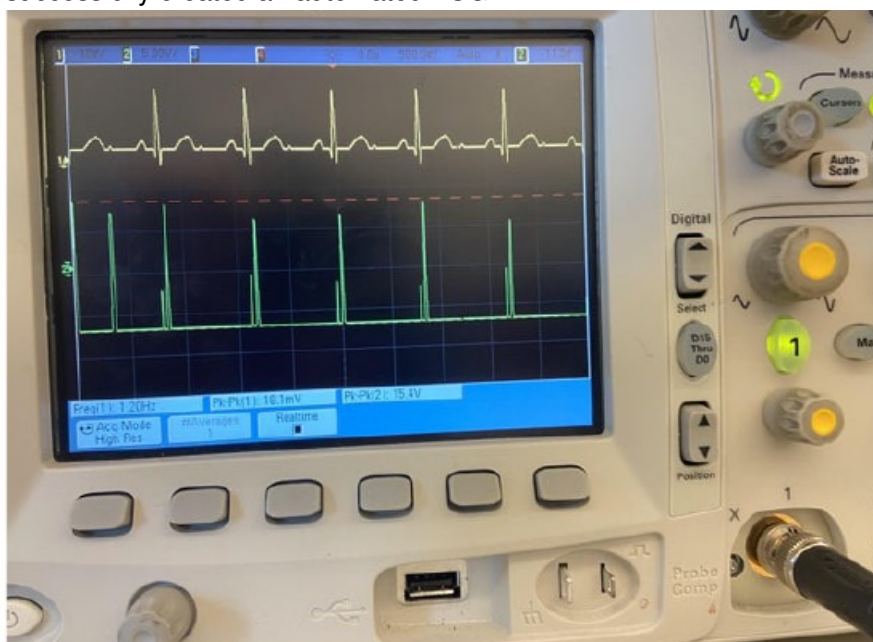
### Step 6: Test on a Human Subject


First, connect the three individual components of the circuit together. Then, test it with a simulated heart beat to ensure everything is working. Then, place the electrodes on the individual so the positive is on the right wrist, negative is on the left ankle, and the ground is on the right ankle. Once the individual is ready, connect a 9V battery to power the opamps and display the output signal. Note that the individual should remain very still for about 10 seconds to get an accurate reading.

Congrats, you have successfully created an automated ECG!



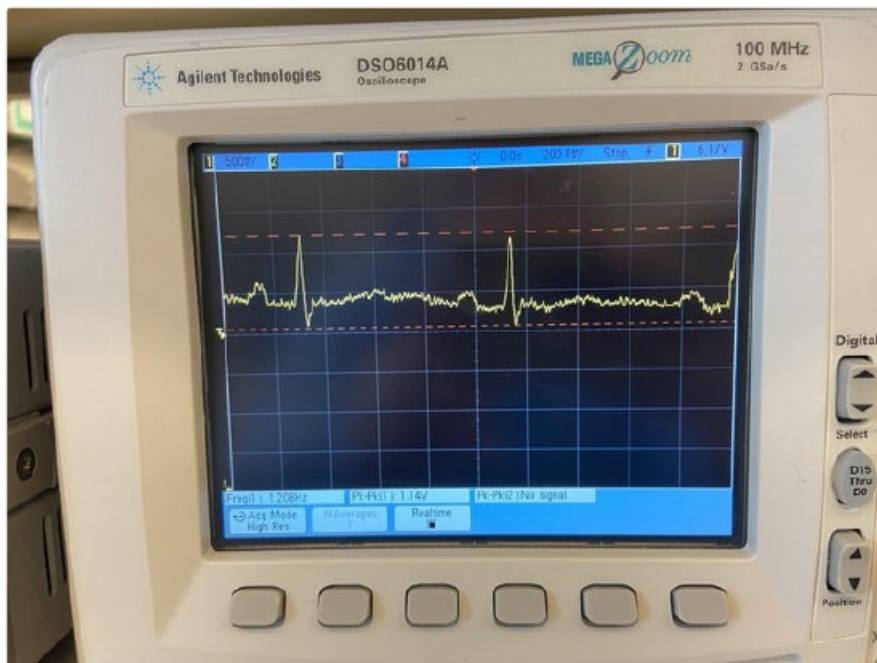

## Documents / Resources

	<p><a href="#">instructables Design a Functional ECG With Automated Plotting of the Biosignal</a> [pdf] Instructions</p> <p>Design a Functional ECG With Automated Plotting of the Biosignal, Design a Functional ECG, Functional ECG, Plotting of the Biosignal</p>
--	--

## References

- 🧑🏻 [Yours for the making - Instructables](#)

Manuals+