

AC393
Application Note
Board and Layout Design Guidelines for
SmartFusion2 SoC and IGLOO2 FPGAs



Power Matters.™

Microsemi Corporate Headquarters

One Enterprise, Aliso Viejo,
CA 92656 USA

Within the USA: +1 (800) 713-4113

Outside the USA: +1 (949) 380-6100

Fax: +1 (949) 215-4996

Email: sales.support@microsemi.com

www.microsemi.com

© 2018 Microsemi Corporation. All rights reserved. Microsemi and the Microsemi logo are trademarks of Microsemi Corporation. All other trademarks and service marks are the property of their respective owners.

Microsemi makes no warranty, representation, or guarantee regarding the information contained herein or the suitability of its products and services for any particular purpose, nor does Microsemi assume any liability whatsoever arising out of the application or use of any product or circuit. The products sold hereunder and any other products sold by Microsemi have been subject to limited testing and must not be used in conjunction with mission-critical equipment or applications. Any performance specifications are believed to be reliable but are not verified, and Buyer must conduct and complete all performance and other testing of the products, alone and together with, or installed in, any end-products. Buyer shall not rely on any data and performance specifications or parameters provided by Microsemi. It is the Buyer's responsibility to independently determine suitability of any products and to test and verify the same. The information provided by Microsemi hereunder is provided "as is, where is" and with all faults, and the entire risk associated with such information is entirely with the Buyer. Microsemi does not grant, explicitly or implicitly, to any party any patent rights, licenses, or any other IP rights, whether with regard to such information itself or anything described by such information. Information provided in this document is proprietary to Microsemi, and Microsemi reserves the right to make any changes to the information in this document or to any products and services at any time without notice.

About Microsemi

Microsemi Corporation (Nasdaq: MSCC) offers a comprehensive portfolio of semiconductor and system solutions for aerospace & defense, communications, data center and industrial markets. Products include high-performance and radiation-hardened analog mixed-signal integrated circuits, FPGAs, SoCs and ASICs; power management products; timing and synchronization devices and precise time solutions, setting the world's standard for time; voice processing devices; RF solutions; discrete components; enterprise storage and communication solutions, security technologies and scalable anti-tamper products; Ethernet solutions; Power-over-Ethernet ICs and midspans; as well as custom design capabilities and services. Microsemi is headquartered in Aliso Viejo, California, and has approximately 4,800 employees globally. Learn more at www.microsemi.com.

Contents

1	Revision History	1
1.1	Revision 14.0	1
1.2	Revision 13.0	1
1.3	Revision 12.0	1
1.4	Revision 11.0	1
1.5	Revision 10.0	2
1.6	Revision 9.0	2
1.7	Revision 8.0	2
1.8	Revision 7.0	2
1.9	Revision 6.0	2
1.10	Revision 5.0	3
1.11	Revision 4.0	3
1.12	Revision 3.0	3
1.13	Revision 2.0	3
1.14	Revision 1.0	3
1.15	Revision 0	3
2	Board Design Guidelines for SmartFusion2 SoC and IGLOO2 FPGAs	4
2.1	Design Considerations	4
2.2	Power Supplies	4
2.2.1	Power Supply Decoupling	6
2.2.2	Power Supply Sequencing	9
2.3	I/O Glitch	9
2.3.1	I/O Glitch During Power-Up	9
2.3.2	I/O Glitch During Power-Down	11
2.3.3	I/O Glitch in a Blank Device	12
2.3.4	Power Supply Flow	12
2.3.5	Unused Pin Configurations	13
2.4	Limiting Surge Current During Device Reset	17
2.5	Clocks	19
2.5.1	Main Crystal Oscillator	19
2.5.2	Auxiliary (RTC) Crystal Oscillator	21
2.6	Reset Circuit	21
2.7	Device Programming	23
2.7.1	JTAG Programming	23
2.7.2	SPI Master Programming	24
2.7.3	SPI Slave Programming	26
2.8	SerDes	26
2.8.1	PCI Express (PCIe)	27
2.8.2	AC Coupling	27
2.8.3	SerDes Reference Clock Requirements	28
2.8.4	PLL Filter	28
2.9	LPDDR, DDR2, and DDR3	28
2.9.1	MDDR/FDDR Impedance Calibration	29
2.9.2	VREF Power	30
2.9.3	VTT Power	30
2.9.4	LPDDR and DDR2 Design	30
2.9.5	DDR3 Guidelines	32
2.10	User I/O and Clock Pins	34

2.10.1	Internal Clamp Diode Circuitry	34
2.11	Obtaining a Two-Rail Design for Non-SerDes Applications	35
2.11.1	Operating Voltage Rails	35
2.12	Configuring Pins in Open Drain	36
2.13	Brownout Detection (BOD)	36
2.14	Simultaneous Switching Noise	37

3 Layout Guidelines for SmartFusion2- and IGLOO2-Based Board Design 38

3.1	Power Supply	38
3.2	Core Supply (VDD)	39
3.2.1	Component Placement	39
3.2.2	Plane Layout	40
3.2.3	Simulations	40
3.3	SerDes	41
3.3.1	Component Placement	41
3.3.2	Plane Layout	43
3.3.3	Simulations	44
3.4	DDR	46
3.4.1	Component Placement	46
3.4.2	Plane Layout	46
3.4.3	Simulations	48
3.5	PLL	50
3.5.1	Component Placement	50
3.5.2	Plane Layout	51
3.5.3	Simulations	51
3.6	I/O Power Supply	52
3.6.1	Component Placement	52
3.6.2	Plane Layout	52
3.6.3	Simulations	53
3.7	Programming Power Supply (VPP or VCCENV)	54
3.7.1	Component Placement	54
3.7.2	Plane Layout	54
3.7.3	Simulations	54
3.8	High-Speed Serial Link (SerDes)	55
3.8.1	Layout Considerations	55
3.8.2	Via	56
3.8.3	DC Blocking Capacitors	58
3.8.4	Connectors	58
3.9	Considerations for Simulation	59
3.9.1	Step 1: Gathering the Required Files	59
3.9.2	Step 2: Creating Simulation Topology	59
3.9.3	Step 3: Configuration of AMI Model	60
3.9.4	Step 4: Results	61
3.10	DDR3 Layout Guidelines	63
3.10.1	Placement	63
3.10.2	Routing	63
3.10.3	Simulation Considerations	65
3.11	References	68

4 Creating Schematic Symbols Using Cadence OrCAD Capture CIS for SmartFusion2 and IGLOO2 Designs 69

4.1	Creating Schematic Symbols using Pin Assignment Tables (PAT)	69
4.1.1	Preparing the PAT Layout File for Import into OrCAD Capture	69
4.1.2	Generating a OrCAD Capture Schematic Symbol	72

4.2	Creating Schematic Symbols with User Defined Pin Names	76
4.2.1	Exporting Pin Information from the Libero Design	76
4.2.2	Preparing the Pin List for Import into OrCAD Capture CIS	78
4.2.3	Generating a Capture Schematic Symbol	81
5	Board Design and Layout Checklist	82
5.1	Prerequisites	82
5.2	Design Checklist	82
5.3	Layout Checklist	89
6	Appendix: Special Layout Guidelines - Crystal Oscillator	90
7	Appendix: Stack-Up	91
8	Appendix: Dielectric Material	93
9	Appendix: Power Integrity Simulation Topology	94

Figures

Figure 1	Power Supplies	5
Figure 2	Impedance of Three Capacitors in Parallel	7
Figure 3	Example Power Supply Topology	13
Figure 4	Recommendations for Unused Pin Configurations	14
Figure 5	Crystal Oscillator	20
Figure 6	RC Time Constant	21
Figure 7	RC Oscillator	21
Figure 8	Reset Circuit	22
Figure 9	Without Reset Circuit	22
Figure 10	Fabric Logic Reset	22
Figure 11	JTAG Programming	24
Figure 12	SPI Master Mode Programming	25
Figure 13	SPI Slave Programming by External Microprocessor	26
Figure 14	SPI Slave Programming by External Programmer	26
Figure 15	SerDes Schematics	27
Figure 16	VREF Generation	30
Figure 17	LPDDR Interface	31
Figure 18	DDR2 Interface	32
Figure 19	8-Bit DDR3 Interface	33
Figure 20	16-Bit DDR3 Interface	33
Figure 21	Internal Clamp Diode Control Circuitry	34
Figure 22	Configuring Pins in Open Drain	36
Figure 23	BOD Circuit Implementation	37
Figure 24	Placement of Capacitors for VDD Plane	39
Figure 25	Capacitor Placement under BGA Vias	40
Figure 26	VDD Plane	40
Figure 27	Impedance Profile of VDD Plane with Respect to Frequency	41
Figure 28	Filter Circuit for SerDes PLL Power Supply	42
Figure 29	Component Between 1.2 K Resistor and K6 Pin	42
Figure 30	Layout for SERDES_x_VDD Plane	43
Figure 31	Layout of SERDES_x_VDDAIO Plane	43
Figure 32	Layout of SERDES_1_L01_VDDAPLL and SERDES_1_L01_REFRET	44
Figure 33	Impedance Profile of SERDES_x_VDD Plane Over Frequency Range	45
Figure 34	Impedance Profile of SERDES_x_VDDAIO Plane Over Frequency Range	45
Figure 35	Layout of VREF5	47
Figure 36	Layout of VDDIO0 Plane	47
Figure 37	Layout of VDDIO5 Plane	48
Figure 38	Impedance Profile of VDDIO0 Plane Over Frequency Range	49
Figure 39	Impedance Profile of VDDIO5 Plane Over Frequency Range	49
Figure 40	Filter Circuit for PLL	50
Figure 41	Placement of Capacitors for PLL filter Circuit	50
Figure 42	Routing for PLL Filter Circuit	51
Figure 43	PLL0VDDA Plane Impedance	52
Figure 44	Impedance Profile of VDDIO1 Plane Over Frequency Range	53
Figure 45	Impedance Profile of VDDIO2 Plane Over Frequency Range	53
Figure 46	Impedance Profile of VPP Plane Over Frequency Range	54
Figure 47	Skew Matching	55
Figure 48	Example of Asymmetric and Symmetric Differential Pairs Structure	55
Figure 49	Zig-Zag Routing	56
Figure 50	Ground Planes for Reference	56
Figure 51	Via Illustration	57
Figure 52	Non-Functional Pads of Via	57
Figure 53	Via-to-Via Pitch	58
Figure 54	GND Via or Return Via	58

Figure 55	Capacitor Pad Reference Plane	58
Figure 56	Typical Topology for SLA Simulation	60
Figure 57	Block Diagram of the 3-tap Feed Forward Equalizer	60
Figure 58	Continuous Time Linear Equalization Response	61
Figure 59	Expected Results from Simulations (Eye Diagram, Eye Contour, and Bath Tub Curve)	62
Figure 60	Eye Mask for PCIe 2.0	62
Figure 61	DDR3 Memories	63
Figure 62	TMATCH Signals (Example Layout)	65
Figure 63	DDR3 Simulation Topology	66
Figure 64	List of Reports Generated by Hyperlynx	67
Figure 65	Setup and Time Margins of DQ0	67
Figure 66	Setup and Time Margins for DQ and DQS Signals	68
Figure 67	Example PAT Spreadsheet - Initial view	69
Figure 68	Example PAT Spreadsheet - Editing Stage	70
Figure 69	Example PAT Spreadsheet - Final Stage	71
Figure 70	New Part Creation Spreadsheet Dialog	72
Figure 71	Example PAT Spreadsheet - Final Stage	73
Figure 72	New Part Creation Spreadsheet Dialog with Data	74
Figure 73	New Part created in the Library	74
Figure 74	Schematic Symbol - First Section	75
Figure 75	Package View of the Schematic Symbol	75
Figure 76	Modifying Port Names	76
Figure 77	I/O Constraints	76
Figure 78	I/O Editor	77
Figure 79	Exporting pin information from Libero	77
Figure 80	Importing Pin Names to the Spreadsheet	78
Figure 81	Importing Pin Names to the Spreadsheet—Step 1	78
Figure 82	Importing Pin Names to the Spreadsheet—Step 2	79
Figure 83	Importing Pin Names to the Spreadsheet—Final Step	79
Figure 84	Spreadsheet with the Pin Names Imported	80
Figure 85	Final Example Spreadsheet to be Imported into OrCAD Capture	81
Figure 86	Layout of the Crystal Oscillator	90
Figure 87	Schematics of Crystal Oscillator	90
Figure 88	Stack-up Used in Development Board	92
Figure 89	Fiberglass Weaving	93
Figure 90	Power Integrity Simulation Topology	94

Tables

Table 1	Device-Package Combinations Without SERDES_x_VDD Pin	6
Table 2	Power Supply Decoupling Capacitors	7
Table 3	Recommended Capacitors	8
Table 4	I/O Glitch during Power-up	10
Table 5	I/O Glitch During Power-Down	11
Table 6	Recommendation for Bank Supplies for FC1152, FG896, FG676, FCS536, FCV484 Packages	15
Table 7	Recommendation for Bank Supplies for FG484 Package	16
Table 8	Recommendation for Bank Supplies for VF400 and FCS325 Packages	16
Table 9	Recommendation for Bank Supplies for VF256 and TQ144 Packages	17
Table 10	Surge Current on VDD during DEVRST_N Assertion (No Decoupling Capacitors on Board)	18
Table 11	M2S090 and M2S150 Surge Current During DEVRST_N Assertion (With Decoupling Capacitors on Board)	18
Table 12	Surge Current on VDD During Digest Check Using System Services (No Decoupling Capacitors on Board)	19
Table 13	Clock Circuit	19
Table 14	Crystal Oscillator Output Frequency Range	20
Table 15	JTAG Pins	23
Table 16	Dedicated Pins	25
Table 17	LPDDR/DDR2/DDR3 Parameters	29
Table 18	Recommendations for Unused I/O and Clock Pins	34
Table 19	Operating Voltage Rails	35
Table 20	Truth Table	36
Table 21	Specifications of the Received Signal for PCIe	62
Table 22	Grouping of DDR3 Signals	63
Table 23	Design Checklist	82
Table 24	Layout Checklist	89

1 Revision History

The revision history describes the changes that were implemented in the document. The changes are listed by revision, starting with the current publication.

1.1 Revision 14.0

The following is a summary of changes made in revision 14.0 of this document.

- Information about I/O glitches during power-up, power-down, and on blank devices was updated. For more information, see [I/O Glitch](#), page 9.
- A figure was added to illustrate SPI master mode programming. For more information, see [SPI Master Programming](#), page 24.
- Information about simultaneous switching noise support was added. For more information, see [Simultaneous Switching Noise](#), page 37.
- The design checklist from *CL0034: SmartFusion2/IGLOO2 Hardware Board Design Checklist* was merged into this document.
- List of device-package combinations that do not have SERDES_x_VDD pins was added. For more information, see [Table 1](#), page 6.
- Design checklist was added in [Board Design and Layout Checklist](#), page 82.
- Information about the de-coupling capacitor and SmartFusion2/IGLOO2 placement was added in [Component Placement](#), page 39.
- Figures were updated in [LPDDR and DDR2 Design](#), page 30 and [DDR3 Guidelines](#), page 32.

1.2 Revision 13.0

The following is a summary of changes made in revision 13.0 of this document.

- Updated [Figure 4](#), page 14, [Figure 17](#), page 31, [Figure 18](#), page 32, [Figure 19](#), page 33, and [Figure 20](#), page 33.
- Updated [Table 6](#), page 15, [Table 7](#), page 16, [Table 8](#), page 16, [Table 9](#), page 17, and [Table 17](#), page 29.
- AC408: Creating Schematic Symbols using Cadence OrCAD Capture CIS for SmartFusion2 and IGLOO2 Designs is merged with this document.

1.3 Revision 12.0

The following is a summary of changes made in revision 12.0 of this document.

- Recommended bank supplies are updated for the FG484 package. See [Table 7](#), page 16.
- Recommended bank supplies are updated for VF400 and FCS325 Packages. See [Table 8](#), page 16.
- Recommended bank supplies are updated for VF256 and TQ144 Packages. See [Table 9](#), page 17.
- Added a note about DQ pins that all 4- and 8-bit pins are interchangeable in LPDDR, DDR2, and DDR3 memories. See [Figure 17](#), page 31.
- Added that the SERDES_x_L[01/23]_VDDAPLL pin supports only 2.5 V, and removed 1.2 V references from all occurrences. For more information, see [Figure 1](#), page 5 and [Table 19](#), page 35.
- AC394: Layout Guidelines for SmartFusion2- and IGLOO2-Based Board Design was added as a part of Board Design guidelines itself.

1.4 Revision 11.0

The following is a summary of changes made in revision 11.0 of this document.

- The filter circuit for SERDES_x_VDD was removed. Even if it was used in the board design previously, it does not affect the functionality of the board. See [Figure 1](#), page 5.
- Information about VDDI2 was updated. See [Table 8](#), page 16 and [Table 9](#), page 17.
- Information about reset circuit was updated. see [Reset Circuit](#), page 21.
- Changed the document to the new template.

1.5 Revision 10.0

The following is a summary of the changes made in revision 10.0 of this document.

- Updated [Power Supplies](#), page 4 (SAR 77745 and SAR 79670).
- Updated [Table 6](#), page 15 (SAR 78887).
- Updated [SPI Master Programming](#), page 24 (SAR 75910).
- Updated [SerDes](#), page 26 (SAR 78504).
- Updated [User I/O and Clock Pins](#), page 34 (SAR 61314).

1.6 Revision 9.0

The following is a summary of the changes made in revision 9.0 of this document.

- Updated [Figure 1](#), page 5 (SAR 72533).
- Added CCC_PLL_VDDA and MSS_xDDR_PLL_VDDA details under [Power Supplies](#), page 4 (SAR 72533).
- Deleted the RC Values for Filter Circuitry table (SAR 72533).
- Added the M2S060T/M2GL060T device column in [Table 9](#), page 17 (SAR 70484).

1.7 Revision 8.0

The following is a summary of the changes made in revision 8.0 of this document.

- Updated [Figure 1](#), page 5 (SAR 66682).
- Updated the RC Values for Filter Circuitry table (SAR 66682 and SAR 65367).
- Updated [Table 6](#), page 15 (SAR 70545).
- Updated [Table 9](#), page 17 (SAR 67599).
- Updated [Table 17](#), page 29 to replace pin SC_SPI_SS with SC_SPI_SDO.
- Updated [PLL Filter](#), page 28 (SAR 60798).
- Updated [Figure 17](#), page 31 (SAR 65438, SAR 69743 and SAR 69580).
- Updated [Figure 18](#), page 32 (SAR 65438).
- Updated [Figure 20](#), page 33 (SAR 65438).
- Added [Figure 21](#), page 34 (SAR 64377).

1.8 Revision 7.0

The following is a summary of the changes made in revision 7.0 of this document.

- Updated [Figure 1](#), page 5 and [Figure 4](#), page 14 (SAR 62858).
- Updated [Power Supply Sequencing](#), page 9 (SAR 64117).
- Updated [Power Supply Flow](#), page 12.
- Added [Table 9](#), page 17.
- Updated [Table 6](#), page 15, [Table 20](#), page 36, and [Table 13](#), page 19 (SAR 62858).
- Updated [Reset Circuit](#), page 21.
- Updated [AC Coupling](#), page 27.
- Updated [Figure 17](#), page 31, [Figure 18](#), page 32, [Figure 19](#), page 33, and [Figure 20](#), page 33 (SAR 65438).
- Replaced all instances of VQ144 with TQ144 Package.
- Removed all instances of and references to M2S100 and M2GL100 device (SAR 62858).

1.9 Revision 6.0

The following is a summary of the changes made in revision 6.0 of this document.

- Updated [Design Considerations](#), page 4 (SAR 58055).
- Updated [Power Supplies](#), page 4 and [Figure 1](#), page 5 (SAR 52580).
- Updated [Power Supply Sequencing](#), page 9 (SAR 59593 and SAR 57004).
- Updated [Figure 4](#), page 14 (SAR 52580).
- Added M2S090T/M2GL090T-FCS325 information for power supplies in [Table 6](#), page 15 (SAR 58241).
- Updated [Figure 2](#), page 7 (SAR 56291).
- Added a foot note to [Table 17](#), page 29 (SAR 59563).

- Updated [SerDes Reference Clock Requirements](#), page 28 (SAR 60213).
- Updated Table 14 (SAR 58085).
- Updated [Brownout Detection \(BOD\)](#), page 36 and [Figure 23](#), page 37 (SAR 56598).
- Updates made to maintain the style and consistency of the document.

1.10 Revision 5.0

The following is a summary of the changes made in revision 5.0 of this document.

- Updated [Power Supply Sequencing](#), page 9, [Figure 1](#), page 5, [Figure 4](#), page 14, and [Table 6](#), page 15 (SAR 52580).
- Updated main crystal oscillator pins naming convention (SAR 53177).
- Updated [Figure 1](#), page 5 (SAR 54177).
- Updated [Figure 1](#), page 5, [Figure 4](#), page 14, and [Table 20](#), page 36 (SAR 55659).
- Updated [Figure 1](#), page 5, and [Figure 4](#), page 14 (SAR 55705).
- Updated [Figure 17](#), page 31, [Figure 18](#), page 32, [Figure 19](#), page 33, and [Figure 20](#), page 33 (SAR 53161).
- Updated [Table 6](#), page 15 (SAR 53348).

1.11 Revision 4.0

The following is a summary of the changes made in revision 4.0 of this document.

- Corrected the ramp rate description to 50 us in the [Power Supply Sequencing](#), page 9 (SAR 50245) (SAR 50844).
- Updated [Figure 11](#), page 24. (SAR 50725).
- Added the Configuring Pins in Open Drain section.

1.12 Revision 3.0

The following is a summary of the changes made in revision 3.0 of this document.

- Updated the content for IGLOO2 devices (SAR 48630).
- Updated [Power Supply Sequencing](#), page 9.
- Updated [DDR3 Guidelines](#), page 32.
- Updated the Temperature Sensing section.

1.13 Revision 2.0

The following is a summary of the changes made in revision 2.0 of this document.

- Modified the SmartFusion2 Unused Pin Configurations section (SAR 47904).
- Updated [Table 19](#), page 35 (SAR 47548).
- Updated the Brownout Detection (BOD) section (SAR 47904).
- Added [Figure 23](#), page 37 (SAR 47904).

1.14 Revision 1.0

The following is a summary of the changes made in revision 1.0 of this document.

- Added the Power Supply Sequencing and Power-on Reset section (SAR 47223).
- Updated [Figure 4](#), page 14 (previously Figure 2) and added Figure 4 (SAR 47223).
- Updated [Table 6](#), page 15 and [Table 19](#), page 35, and added [Table 20](#), page 36 (SAR 47223).

1.15 Revision 0

Revision 0 was the first publication of this document.

2 Board Design Guidelines for SmartFusion2 SoC and IGLOO2 FPGAs

This application note provides board-level design guidelines for SmartFusion®2 and IGLOO®2 devices. This document can be used along with the [Layout Guidelines for SmartFusion2- and IGLOO2-Based Board Design](#), page 38 that describes the PCB design. These guidelines must be treated as a supplement to standard board-level design practices.

Good board design practices are required to obtain expected performance from both PCB and SmartFusion2/IGLOO2 devices. High quality and reliable results depend on minimizing noise levels, preserving signal integrity, meeting impedance and power requirements, and using appropriate SerDes protocols.

This document assumes that the reader has a good understanding of the SmartFusion2/IGLOO2 device, is experienced in digital and analog board design, and knows about the electrical characteristics of systems. Background information on the key theories and concepts of board-level design is available in *High Speed Digital Design: A Handbook of Black Magic*, and other industry literature.

2.1 Design Considerations

The SmartFusion2/IGLOO2 device supports various high-speed interfaces using both double data rate input/output (DDRIO) and SerDes I/O. DDRIO is a multi-standard I/O optimized for low-power DDR, DDR2, and DDR3 performance. SerDes I/O are dedicated to high-speed serial communication protocols. The SerDes I/O supports protocols such as PCI Express 2.0, 10 Gbps attachment unit interface (XAUI), serial gigabit media independent interface (SGMII), JESD204B, and user-defined high-speed serial protocol implementation in fabric.

Routing high-speed serial data over a PCB is a challenge as losses, dispersion, and crosstalk effects increase with speed. Channel losses and crosstalk decrease the signal-to-noise ratio and limit the data rate on the channel.


Subsequent sections discuss the following:

- Power supplies
- Limiting surge current during device reset
- Clocks
- Reset circuit
- JTAG
- Special pins
- Device programming
- SerDes
- LPDDR, DDR2, and DDR3
- User I/O and clock pins
- Achieving a two-rail design
- SerDes
- Brownout detection (BOD)

To verify the design, see the [CL0034: SmartFusion2/IGLOO2 Hardware Board Design Checklist](#).

2.2 Power Supplies

The following figure illustrates the typical power supply requirements, including PLL RC filter values, for SmartFusion2/IGLOO2 devices. For more information about decoupling capacitors associated with individual power supplies, see [Table 2](#), page 7.

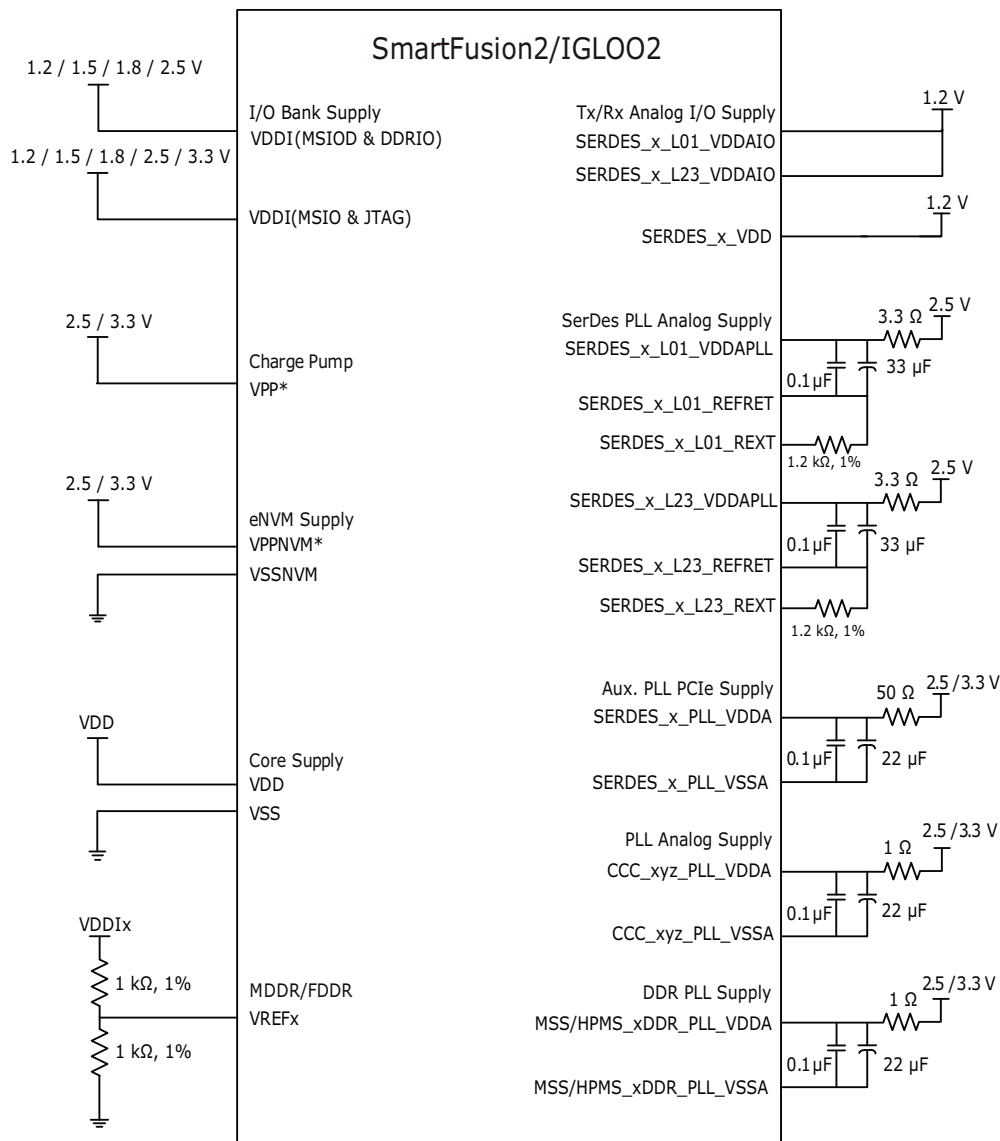Figure 1 • Power Supplies

Note: The power supply settings for all the PLLs (MDDR, FDDR, and CCC) must be the same in Libero SoC and on the board. The PLLs (MDDR, FDDR, CCC) can be connected to a 2.5 V or 3.3 V supply.

For M2S090T(S), M2GL090T(S), M2S150T(S), and M2GL150T(S) devices, the VPP and VPPNVM must be connected to a +3.3 V supply.

For the CCC_xyz_PLL supplies, xy refers to the location of the PLL in the device (NE/ NW/ SW) and z refers to the number associated with the PLL (0 or 1).

The PLL RC values shown in the figure are applicable to all variants of SmartFusion2/IGLOO2 devices.

For the device to operate successfully, power supplies must be free from unregulated spikes and the associated grounds must be free from noise. All overshoots and undershoots must be within the absolute maximum ratings provided in the [DS0128: IGLOO2 and SmartFusion2 Datasheet](#).

The various power supplies needed for IGLOO2 and SmartFusion2 FPGAs are as follows:

- VDD and VPP: The main power supplies for the device. These must be connected to the appropriate power rail based on the system requirements.
- VDDIx: I/O bank supplies for the device. For recommendations for unused I/O bank supplies, see [Table 6](#), page 15 and [Table 9](#), page 17.

- VPPNVM: eNVM supply for the device. This pin must be connected to the VPP supply.
- VREFx: Reference voltage for MDDR/FDDR signals, which is powered through the corresponding bank supply (VDDIx). Can be DNC or grounded (VSS) when unused.
- SERDES_x_VDD: The 1.2 V main power supply for the SerDes.SERDES_x_Lyz_VDDAIO: The +1.2 V SerDes PMA supply for Tx/Rx analog I/O. The SerDes VDDAIO must be powered up/down at the same voltage as the core VDD supply on the device.
- CCC_xyz_PLL_VDDA and MSS_xDDR_PLL_VDDA: If the associated PLL is used as a clock multiplier, these supplies must be connected over the RC filter circuitry between the common PLL supply and the corresponding on-board PLL return path. If the PLL is unused or used as a clock divider, these supplies can be connected directly to either 2.5 V or 3.3 V without filter circuitry.
- SERDES_x_Lyz_REFRET: This pin provides the internal PLL current return path for SERDES_x_Lyz_VDDAPLL. This pin must be connected to the corresponding SerDes VDDA PLL through an RC filter circuit, as shown in [Figure 1](#), page 5. For more information about unused pins, see [Figure 4](#), page 14.
- SERDES_x_PLL_VSSA: This pin provides the internal PLL current return path for SERDES_x_PLL_VDDA. This pin must be connected to the corresponding PLL_VDDA through an RC filter circuit, as shown in [Figure 1](#), page 5. For more information about unused pins, see [Figure 4](#), page 14. For more information about unused pins, see [Figure 4](#), page 14
- CCC_xyz_PLL_VSSA: This pin provides the internal PLL current return path for CCC_xyz_PLL_VDDA. This pin must be connected to the corresponding PLL_VDDA through an RC filter circuit, as shown in [Figure 1](#), page 5. For more information about unused pins, see [Figure 4](#), page 14.
- MSS/HPMS_xDDR_PLL_VSSA: This pin provides the internal PLL current return path for MSS/HPMS_xDDR_PLL_VDDA. This pin must be connected to the corresponding PLL_VDDA through an RC filter circuit, as shown in [Figure 1](#), page 5. For more information about unused pins, see [Figure 4](#), page 14.

For the device-package combinations listed in the following table, the SERDES_x_VDD pins are shorted with VDD pins inside the package substrate to free up the package pins.

Table 1 • Device-Package Combinations Without SERDES_x_VDD Pin

Device	Package
M2S025T, M2GL025T	FCS325
M2S050T(S), M2GL050T(S)	FCS325
M2S060T(S), M2GL060T(S)	FCS325
M2S90T(S), M2GL90T(S)	FCS325
M2S10T(S), M2GL010T(S)	VF256
M2S025TS, M2S025T, M2GL025TS, M2GL025T	VF256
M2S150T(S), M2GL150T(S)	FCV484
M2S150TS, M2S150T, M2GL150TS, M2GL150T	FCS536

For detailed pin descriptions, see [DS0115: SmartFusion2 Pin Descriptions Datasheet](#) or [DS0124: IGLOO2 Pin Descriptions Datasheet](#).

2.2.1 Power Supply Decoupling

To reduce any potential fluctuation on the power supply lines, decoupling capacitors, bypass capacitors, and other power supply filtering techniques must be used.


To save board space, fewer, larger-value bulk capacitors can be used instead of a large number of smaller capacitors. However, care must be taken to ensure that the electrical characteristics of the consolidated capacitors (ESR and ESL) match those of the parallel combination of the recommended capacitors.

Ceramic capacitors are preferred for high-frequency noise elimination and tantalum capacitors for low-frequency noise elimination.

- For values ranging from 1 nF to 100 μ F, use X7R or X5R (dielectric material) type capacitors.
- For values ranging from 100 μ F to 1000 μ F, use tantalum capacitors.

The following figure shows an impedance versus frequency graph for effective combinations of three values of capacitors. From the graph it is evident that impedance is less for wider frequency band when different capacitors are in parallel.

Figure 2 • Impedance of Three Capacitors in Parallel

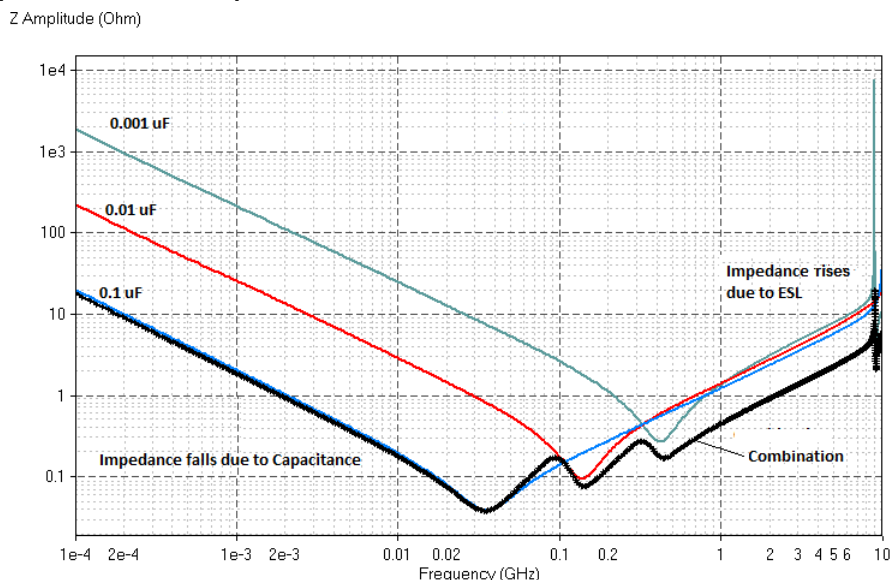

The following table lists the recommended number of PCB decoupling capacitors for an M2S050T/M2GL050T-FG896 device.

Table 2 • Power Supply Decoupling Capacitors

Pin Name	Number of Pins	Ceramic Caps				Tantalum Caps				
		0.01 μ F	0.1 μ F	10 μ F	33 μ F	22 μ F	47 μ F	100 μ F	220 μ F ¹	330 μ F
VDD	24	12	12					1	3	1
VDDI0	29	14	14				2			
VDDI1	4	2	2	1						
VDDI2	4	2	2	1						
VDDI3	5	2	3	1						
VDDI4	3	2	1	1						
VDDI5	29	14	14				2			
VDDI6	1	1		1						
VDDI7	6	3	3	1						
VDDI8	5	2	3	1						
VDDI9	1	1	1							
VPP	4	2	2	1						
VREF0	3	2	1	1						
VREF5	3	2	1	1						

Table 2 • Power Supply Decoupling Capacitors (continued)

Pin Name	Number of Pins	Ceramic Caps				Tantalum Caps				
		0.01 μ F	0.1 μ F	10 μ F	33 μ F	22 μ F	47 μ F	100 μ F	220 μ F ¹	330 μ F
VPPNVM	1	1		1						
SERDES_0_VDD	2	1	1	1 ²						
SERDES_1_VDD	2	1	1	1 ²						
SERDES_0_L01_VDDAIO	1	1 ²	1 ²	1 ³						
SERDES_0_L23_VDDAIO	1	1 ²	1 ²	1 ³						
SERDES_1_L01_VDDAIO	1	1 ²	1 ²	1 ³						
SERDES_1_L23_VDDAIO	1	1 ²	1 ²	1 ³						
CCC_NE0_PLL_VDDA	1		1			1				
CCC_NE1_PLL_VDDA	1		1			1				
CCC_NW0_PLL_VDDA	1		1			1				
CCC_NW1_PLL_VDDA	1		1			1				
CCC_SW0_PLL_VDDA	1		1			1				
CCC_SW1_PLL_VDDA	1		1			1				
MSS_FDDR_PLL_VDDA	1		1			1				
MSS_PLL_MDDR_VDDA	1		1			1				
PLL_SERDES_0_VDDA	1		1			1				
PLL_SERDES_1_VDDA	1		1			1				
SERDES_0_L01_VDDAPLL	1		1		1					
SERDES_0_L23_VDDAPLL	1		1		1					
SERDES_1_L01_VDDAPLL	1		1		1					
SERDES_1_L23_VDDAPLL	1		1		1					

1. 220 μ F is used to limit surge current for the VDD supply.
2. Single ceramic decoupling capacitor is required for both pins at the device.
3. Single ceramic decoupling capacitor is required for four pins at the device.

Decoupling capacitors other than those listed in the preceding table can be used if sized to meet or exceed the performance of the network given in this example. However, substitution requires analysis of the resulting power distribution system's impedance versus frequency to ensure that no resonant impedance spikes result. See [Figure 1](#), page 5 for power supply schematics design.

The following table lists the recommended decoupling capacitors for the SmartFusion2/IGLOO2 devices. For placement and routing details, see [Layout Guidelines for SmartFusion2- and IGLOO2-Based Board Design](#), page 38.

Table 3 • Recommended Capacitors

Part Number	Manufacturer	Description
GRM155R71C103KA01D	Murata	Ceramic 0.01 μ F, 16 V, 10%, X7R, 0402
GRM155R71C104KA88D	Murata	Ceramic 0.1 μ F, 16 V, 10%, X7R, 0402
GRM188R60J106ME47D	Murata	Ceramic 10 μ F, 6.3 V, X5R, 0603
T491B475M016AT	KEMET	Tantalum 4.7 μ F, 16 V, 20%, 1411
T491B226M016AT	KEMET	Tantalum 22 μ F, 16 V, 20%, 1411

Table 3 • Recommended Capacitors (continued)

Part Number	Manufacturer	Description
T491B476M010AT	KEMET	Tantalum 47 μ F, 10 V, 20%SMD
T520V107M010ATE050	KEMET	Tantalum 100 μ F, 10 V, 20%, 2917
TPSD337K010R0050	AVX	Tantalum 330 μ F, 10 V, 10%, 2917

2.2.2 Power Supply Sequencing

The SmartFusion2/IGLOO2 system controller performs systematic power-on reset (POR) whenever the device is powered on or reset. All the I/Os are held in a high-impedance state by the system controller until all power supplies are at their required levels and the system controller has completed the reset sequence.

VDD refers to the supply voltage to the SmartFusion2/IGLOO2 device core and VDDI refers to the supply voltage to the bank I/O buffers and I/O logic.

On detection of a power-up event, the POR circuit sends the power-on reset signal to the system controller and reset controller in the SmartFusion2/IGLOO2 device. The power-on reset circuitry in SmartFusion2/IGLOO2 devices require the VDD and VPP supplies to ramp monotonically from 0 V to the minimum recommended operating voltage within a predefined time. There is no sequencing requirement on VDD and VPP. Four ramp rate options are available during design generation: 50 μ s, 1 ms, 10 ms, and 100 ms. Each selection represents the maximum ramp rate to apply to VDD and VPP. The ramp rates can be configured by using the Libero software.

The SERDES_VDD pins are shorted to VDD on silicon die; therefore, Microsemi recommends using the same regulator to power up the VDD, SERDES_VDD and SERDES_VDDAIO pins. These three voltage supplies must be powered at the same voltage and must be ramped up and ramped down at the same time.

For information about the power-up to functional time sequence, see [DS0128: IGLOO2 and SmartFusion2 Datasheet](#).

2.3 I/O Glitch

Glitches were observed in SmartFusion2 and IGLOO2 devices during power-up and power-down cases in different scenarios. The following sections describe the glitch observations.

2.3.1 I/O Glitch During Power-Up

Table 4, page 10 lists the I/O glitch observations during power-up found during internal testing.

Table 4 • I/O Glitch during Power-up

Test Case	Output	Test Condition	Glitch observed (Yes or No)	Comments	Observation with 10 K Ω Pull-Down Resistor
Case 1	Output driving low	VPP and DEVRSTB are constant at 3.3V; VDD & VDDI are ramped up Simultaneously	Yes (less amplitude ~480mV)	-	No glitch observed
Case 2		VPP and DEVRSTB are ramped up; VDD and VDDI are constant at respective nominal voltages	Yes (less amplitude ~70mV)	From case 2 & 3 glitch(70mV) is mainly due to VPP	No glitch observed
Case 3		DEVRSTB is ramped up; VPP,VDD, and VDDI are constant at respective nominal voltages	Yes (less amplitude ~70mV)		
Case 4		VPP and DEVRSTB are constant 3.3V; VDD and VDDI are ramped up (VDD Leading VDDI)	Yes (less amplitude ~532mV)		No glitch observed
Case 5		VPP and DEVRSTB are constant 3.3V; VDD and VDDI are ramped up (VDD Lagging VDDI)	Yes (less amplitude ~448mV)		No glitch observed
Case 6		VPP, DEVRSTB, and VDDI are constant at respective nominal voltages; VDD is ramped up	Yes (less amplitude ~296mV with Bank4 and ~136mV with Bank0)	From this case glitch is mainly due to VDD ramp up. It is inconsistent	No glitch observed
Case 7		VPP, DEVRSTB, and VDD are constant at respective nominal voltages; VDDI is ramped up	Yes (less amplitude ~144mV)		No glitch observed
Case 8		VPP = 3.3V; DEVRSTB = 0V VDD and VDDI are ramped up simultaneously	Yes (less amplitude ~480mV)		No glitch observed

Table 4 • I/O Glitch during Power-up (continued)

Test Case	Output	Test Condition	Glitch observed (Yes or No)	Comments	Observation with 10 K Ω Pull-Down Resistor
Case 9	Output driving high	VPP and DEVRSTB are constant at 3.3V; VDD and VDDI are ramped up simultaneously	Yes (less amplitude ~560mV)		No glitch observed
Case 10		VPP, DEVRSTB, and VDDI are constant at respective nominal voltages; VDD is ramped up	Yes (less amplitude ~296mV)		No glitch observed

Recommendation: Glitches were observed in all the power-up cases. In most cases, it was not a true glitch, but simply VDDI to pad capacitive source-drain coupling as the supply charges up. The glitch could not be avoided under any ramp case scenario. The Glitch occurred for a maximum duration of 500 μ s approximatively.

To remove the glitch, use an external 10 k Ω pull-down resistor.

2.3.2 I/O Glitch During Power-Down

The following table lists the I/O glitch observations during power-down found during internal testing.

Table 5 • I/O Glitch During Power-Down

Test Case	Output State	Test Condition	Glitch Observed	Comments
Case 1	Output driving low	VPP and DEVRSTB are constant 3.3V; VDD and VDDI are ramped down	No	-
Case 2		VPP and DEVRSTB are ramped down; VDD and VDDI are constant	Yes (glitch amplitude ~1.53V)	From case 2 & 3 glitch(2V) is mainly due to DEVRSTB
Case 3		DEVRSTB is ramped down; VPP, VDD, and VDDI are constant	Yes (glitch amplitude ~2.03V)	
Case 4	Output driving high	DEVRSTB is ramped up; VPP, VDD, and VDDI are constant	No	-
Case 5		DEVRSTB is ramped down; VPP, VDD, and VDDI are constant	No	-
Case 6	Output tri-stated	DEVRSTB is ramped up; VPP, VDD, and VDDI are constant	No	-
Case 7		DEVRSTB is ramped down; VPP, VDD, and VDDI are constant	Yes (glitch amplitude ~1.75V)	-

To minimize I/O glitch during power-down, any one of the following solutions can be used:

- The device must enter Flash*Freeze mode before a device reset asserted.
- In the power-down sequence, VDDI must be powered-down first and then the DEVRST_N must be asserted.
- An external pull-down resistor (for example 1K resistor) must be used for the I/O.
- Critical outputs must be driven high before the DEVRST_N assertion.

2.3.3 I/O Glitch in a Blank Device

I/O glitch was observed on bank 2 of a blank device before programming. On a blank device, the I/Os are placed in the Flash*Freeze state (tristate with weak pull-ups). When the programming starts, the I/Os transition to the boundary scan mode. On I/O bank 2, there is a race condition between exiting the Flash*Freeze mode and the entering boundary scan mode. During this transition, the outputs on bank 2 briefly drive high until the boundary scan mode is enabled. This transition results in an I/O glitch.

To prevent this glitch, use the JTAG command to adjust the I/O drive strength to zero before programming starts.

2.3.3.1 Application Impact Due to Glitch


Application Impact: There is no reliability impact because the duration of the I/O glitch does not exceed the datasheet overshoot specifications. The glitch amplitude tracks the VDDI bank voltage and rises slightly above the VDDI. For example, at 3.3 V of VDDI, the glitch rises above 3.3 V by approximately 0.3 V for 5 ns. The the glitch amplitude is directly proportional to the VDDI value.

Resolution: Regenerate the bitstream using Libero 11.8 SP1.

2.3.4 Power Supply Flow

SmartFusion2/IGLOO2 FPGA devices require multiple power supplies. [Figure 3](#), page 13 illustrates a topology for generating the required power supplies from a single 12 V source. This example power supply topology is based on SmartFusion2 M2S050T-FG896 device with two SerDes channels (SERDES0 and SERDES1) and a DDR3 interface.

Figure 3 • Example Power Supply Topology

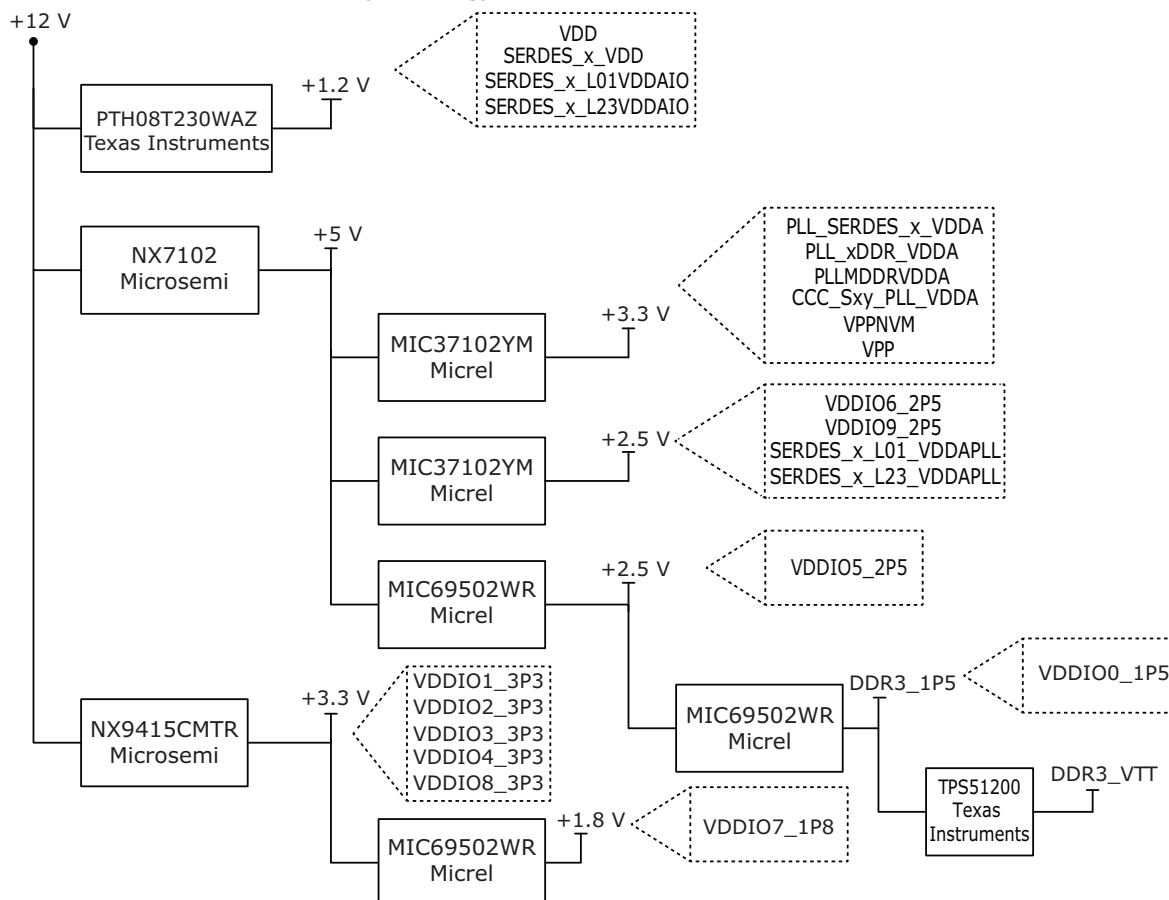

2.3.5 Unused Pin Configurations


In cases where certain interfaces are not used, the associated pins need to be configured properly. For example, the pins of an unused crystal oscillator can be left floating (DNC) and must not be grounded. If a PLL is not used or bypassed, and only the divider circuitry is used, then the PLL's pins can be powered without RC filter circuitry.

For SmartFusion2/IGLOO2 devices with multiple SerDes blocks, designers should tie off unused SerDes blocks, as shown in [Figure 4](#), page 14.

For banks configured as LPDDR or single-ended I/O (and MDDR or FDDR functionalities are not being used), VREFx can be left floating (DNC) even though the corresponding bank supply is still powered.

To allow a SmartFusion2/IGLOO2 device to exit from reset, some of the bank supplies (VDDIx) must always be powered, even if associated bank I/O are unused (as shown in [Table 6](#), page 15 and [Table 9](#), page 17).

For details on bank locations for all the devices, see [DS0115: SmartFusion2 Pin Descriptions Datasheet](#) or [DS0124: IGLOO2 Pin Descriptions Datasheet](#).

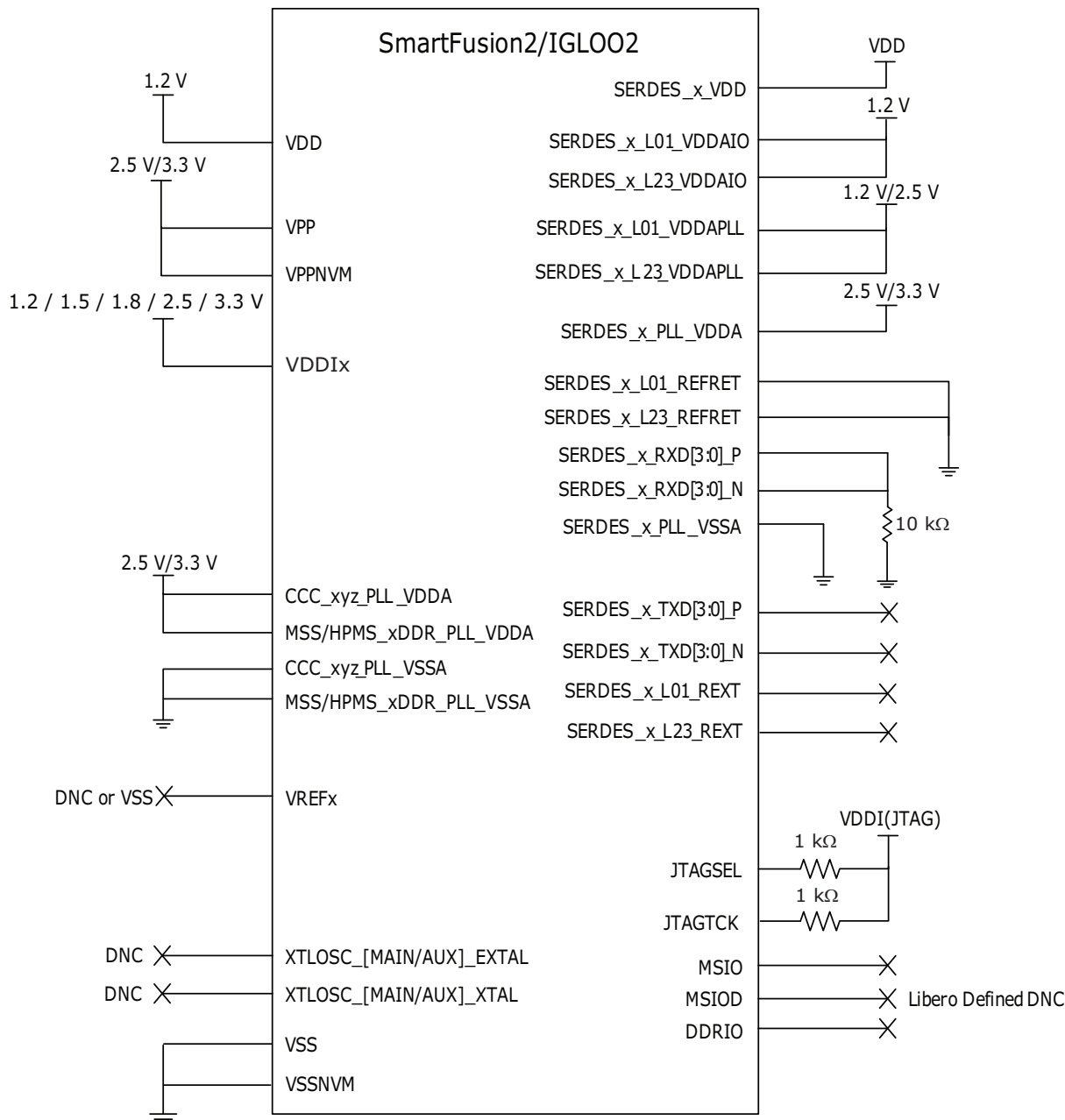Figure 4 • Recommendations for Unused Pin Configurations

Note: For M2S090T(S), M2GL090T(S), M2S150T(S), and M2GL150T(S) devices, the VPP and VPPNVM must be connected to a +3.3 V supply.

Note: SERDES_RXD pin connections are changed to VSS through a 10 kΩ resistor to reduce the latch-up risk. This change does not effect the old board design functionality.

For recommendations on unused VDDI supplies, see the following tables.

SmartFusion2/IGLOO2 devices have multiple bank supplies. In cases where specific banks are not used, Microsemi recommends connecting them as listed in the following tables.

If there is no recommendation provided for a device-bank supply combination, it means the bank is not pinned out.

Table 6 • Recommendation for Bank Supplies for FC1152, FG896, FG676, FCS536, FCV484 Packages¹

Bank	FC1152	FG896	FG676		FCS536	FCV484
Supply Names	M2S150T/ M2GL050T	M2S050T/ M2GL050T	M2S090T/ M2GL090T	M2S060T/ M2GL060T	M2S150T/ M2GL150T	M2S150T/ M2GL150
VDDI0	Connect to VSS through a 10 kΩ resistor					–
VDDI1	Connect to VSS through a 10 kΩ resistor	Must connect to VDDI1	Connect to VSS through a 10 kΩ resistor			
VDDI2	Connect to VSS through a 10 kΩ resistor	Must connect to VDDI2	Must connect to VDDI2	Must connect to VDDI2	Connect to VSS through a 10 kΩ resistor	
VDDI3	Connect to VSS through a 10 kΩ resistor	Must connect to VDDI3	Must connect to VDDI3	Must connect to VDDI3	Connect to VSS through a 10 kΩ resistor	
VDDI4	Connect to VSS through a 10 kΩ resistor			Must connect to VDDI4	Connect to VSS through a 10 kΩ resistor	
VDDI5	Connect to VSS through a 10 kΩ resistor					
VDDI6	Must connect to VDDI6	Connect to VSS through a 10 kΩ resistor			Must connect to VDDI6	Must connect to VDDI6
VDDI7	Must connect to VDDI7	Connect to VSS through a 10 kΩ resistor			Must connect to VDDI7	Must connect to VDDI7
VDDI8	Connect to VSS through a 10 kΩ resistor					–
VDDI9	Connect to VSS through a 10 kΩ resistor	–	Connect to VSS through a 10 kΩ resistor			
VDDI10	Connect to VSS through a 10 kΩ resistor	–	–	–	Connect to VSS through a 10 kΩ resistor	
VDDI11	Connect to VSS through a 10 kΩ resistor	–	–	–	Connect to VSS through a 10 kΩ resistor	
VDDI12	Connect to VSS through a 10 kΩ resistor	–	–	–	Connect to VSS through a 10 kΩ resistor	
VDDI13	Connect to VSS through a 10 kΩ resistor	–	–	–	Connect to VSS through a 10 kΩ resistor	
VDDI14	Connect to VSS through a 10 kΩ resistor	–	–	–	Connect to VSS through a 10 kΩ resistor	
VDDI15	Connect to VSS through a 10 kΩ resistor	–	–	–	Connect to VSS through a 10 kΩ resistor	–
VDDI16	Connect to VSS through a 10 kΩ resistor	–	–	–	Connect to VSS through a 10 kΩ resistor	
VDDI17	Connect to VSS through a 10 kΩ resistor	–	–	–	Connect to VSS through a 10 kΩ resistor	
VDDI18	Connect to VSS through a 10 kΩ resistor	–	–	–	Connect to VSS through a 10 kΩ resistor	–

1. The unused VDDI# pins must be connected to VSS through a 10 KΩ resistor. The VDDI# pins can be grouped and connected to one 10 KΩ resistor or a 10 K Ω resistor can be used for each VDDI# bank, it completely depends on the board layout. For the previous design the unused VDDI# pins were DNC, and cannot create functionality issue. Microsemi recommends connecting to Ground to improve the board reliability.

Table 7 • Recommendation for Bank Supplies for FG484 Package¹

Bank Supply Names	FG484					
	M2S090T/ M2GL090T	M2S060T M2GL060T	M2S050T/ M2GL050T	M2S025T/ M2GL025T	M2S010T/ M2GL010T	M2S005/ M2GL005
VDDI0	–	–	Connect to VSS through a 10 kΩ resistor			
VDDI1	Connect to VSS through a 10 kΩ resistor		Must connect to VDDI1	Must connect to VDDI1	Must connect to VDDI1	Must connect to VDDI1
VDDI2	Must connect to VDDI2	Must connect to VDDI2	–	Must connect to VDDI2	Must connect to VDDI2	Must connect to VDDI2
VDDI3	Must connect to VDDI3	–	Must connect to VDDI3	Connect to VSS through a 10 kΩ resistor	Must connect to VDDI3	Connect to VSS through a 10 kΩ resistor
VDDI4	Connect to VSS through a 10 kΩ resistor	Must connect to VDDI4	Connect to VSS through a 10 kΩ resistor	Must connect to VDDI4	Connect to VSS through a 10 kΩ resistor	Must connect to VDDI4
VDDI5	Connect to VSS through a 10 kΩ resistor					
VDDI6	Connect to VSS through a 10 kΩ resistor					
VDDI7	Connect to VSS through a 10 kΩ resistor					–
VDDI8	Connect to VSS through a 10 kΩ resistor			–	–	–
VDDI9	–	Connect to VSS through a 10 kΩ resistor	–	–	–	–

1. The unused VDDI# pins must be connected to VSS through a 10 KΩ resistor. The VDDI# pins can be grouped and connected to one 10 KΩ resistor or a 10 K Ω resistor can be used for each VDDI# bank, it completely depends on the board layout. For the previous design the unused VDDI# pins were DNC, and cannot create functionality issue. Microsemi recommends connecting to Ground to improve the board reliability.

Table 8 • Recommendation for Bank Supplies for VF400 and FCS325 Packages¹

Bank Supply Names	VF400					FCS325			
	M2S060T/ M2GL060T	M2S050T/M 2GL050T	M2S025T/ M2GL025T	M2S010T/ M2GL010T	M2S005/ M2GL005	M2S090T/ M2GL090T	M2S060T/ M2GL060T	M2S050T/M 2GL050T	M2S025T/ M2GL025T
VDDI0	–	Connect to VSS through a 10 kΩ resistor				–	–	Connect to VSS through a 10 kΩ resistor	
VDDI1	Connect to VSS through a 10 kΩ resistor	Must connect to VDDI1	Must connect to VDDI1	Must connect to VDDI1	Must connect to VDDI1	Connect to VSS through a 10 kΩ resistor		Must connect to VDDI1	Must connect to VDDI1
VDDI2	Must connect to VDDI2	–	Must connect to VDDI2	Must connect to VDDI2	Must connect to VDDI2	Must connect to VDDI2	Must connect to VDDI2	Must connect to VDDI2	–
VDDI3	–	Must connect to VDDI3	Connect to VSS through a 10 kΩ resistor			Must connect to VDDI3	Must connect to VDDI3	Must connect to VDDI3	Connect to VSS through a 10 kΩ resistor
VDDI4	Must connect to VDDI4	Connect to VSS through a 10 kΩ resistor			Must connect to VDDI4	Connect to VSS through a 10 kΩ resistor	Must connect to VDDI4	Connect to VSS through a 10 kΩ resistor	Must connect to VDDI4
VDDI5	Connect to VSS through a 10 kΩ resistor								

Table 8 • Recommendation for Bank Supplies for VF400 and FCS325 Packages¹ (continued)

VDDI6	Connect to VSS through a 10 kΩ resistor							
VDDI7	Connect to VSS through a 10 kΩ resistor	–	–	–	–	–	Connect to VSS through a 10 kΩ resistor	–
VDDI8	Connect to VSS through a 10 kΩ resistor	–	–	–	–	–	Connect to VSS through a 10 kΩ resistor	–
VDDI9	Connect to VSS through a 10 kΩ resistor	–	–	–	–	–	Connect to VSS through a 10 kΩ resistor	–

1. The unused VDDI# pins must be connected to VSS through a 10 KΩ resistor. The VDDI# pins can be grouped and connected to one 10 KΩ resistor or a 10 K Ω resistor can be used for each VDDI# bank, it completely depends on the board layout. For the previous design the unused VDDI# pins were DNC, and cannot create functionality issue. Microsemi recommends connecting to Ground to improve the board reliability.

Table 9 • Recommendation for Bank Supplies for VF256 and TQ144 Packages¹

Bank Supply Names	VF256			TQ144	
	M2S025T/ M2GL025T	M2S010T/ M2GL010T	M2S005S/ M2GL005S	M2S010S/ M2GL010S	M2S005S/ M2GL005S
VDDI0	Connect to VSS through a 10 kΩ resistor				
VDDI1	Must connect to VDDI1	Must connect to VDDI1	Must connect to VDDI1	–	–
VDDI2	Must connect to VDDI2	Must connect to VDDI2	Must connect to VDDI2	Must connect to VDDI2	Must connect to VDDI2
VDDI3	Connect to VSS through a 10 kΩ resistor				
VDDI4	Must connect to VDDI4	Must connect to VDDI4	Must connect to VDDI4	Must connect to VDDI4	Must connect to VDDI4
VDDI5	Connect to VSS through a 10 kΩ resistor			–	Connect to VSS through a 10 kΩ resistor
VDDI6	Connect to VSS through a 10 kΩ resistor				
VDDI7	Connect to VSS through a 10 kΩ resistor	–	–	Connect to VSS through a 10 kΩ resistor	–

1. The unused VDDI# pins must be connected to VSS through a 10 KΩ resistor. The VDDI# pins can be grouped and connected to one 10 KΩ resistor or a 10 K Ω resistor can be used for each VDDI# bank, it completely depends on the board layout. For the previous design the unused VDDI# pins were DNC, and cannot create functionality issue. Microsemi recommends connecting to Ground to improve the board reliability.

2.4 Limiting Surge Current During Device Reset

After device power-up, if the application asserts the DEVRST_N pin and there are no decoupling capacitors on the board, additional surge current on VDD may be observed during assertion of DEVRST_N or during a digest check operation. This section describes how to minimize additional surge current during SmartFusion2/IGLOO2 device reset operation. This additional surge current does not occur during device power-up; it is applicable only when DEVRST_N is asserted.

SmartFusion2/IGLOO2 device reset can be activated either directly through an external DEVRST_N pin or indirectly through the tamper macro IP. When the device reset is asserted, the system controller immediately puts the FPGA core in inactive state. During this operation, depending on the board design layout and decoupling capacitors used, there may be additional surge current on the VDD power rail. The additional surge current has no effect on device reliability. This surge current is for a very short duration and is normally handled by bulk decoupling capacitors on the power plane in a typical system. In cases where Microsemi-recommended board design guidelines cannot be implemented for decoupling capacitors for VDD (due to limited board spacing or other reasons), higher-than-expected surge current may occur during device reset.

The following table provides characterized surge current data for VDD during DEVRST_N assertion. This data represents the worst-case condition with no decoupling capacitors on the board.

Table 10 • Surge Current on VDD during DEVRST_N Assertion (No Decoupling Capacitors on Board)

Device	Width of Surge at 50% of Pulse (μS)	Surge Current on VDD			Units
		0 °C to 85 °C	–40 °C to 100 °C	–55 °C to 125 °C	
M2S005/M2GL005	2	0.5	0.6	0.6	A
M2S010/M2GL010	3	0.9	0.9	0.9	A
M2S025/M2GL025	6	1.7	1.7	1.7	A
M2S050/M2GL050	12	3.2	3.2	3.2	A
M2S060/M2GL060	12	3.2	3.2	3.2	A
M2S090/M2GL090	22	4.4	4.6	4.6	A
M2S150/M2GL150	42	7.0	7.3	7.3	A

However, the surge current data in the preceding table does not represent a typical system. To illustrate this, surge current during device reset was measured at room temperature separately for the M2S090 security evaluation kit and the M2S150 advanced development kit. These kits have decoupling capacitors according to the Microsemi-recommended board design guidelines. The following table lists the surge currents observed on the M2S090 security evaluation kit and the M2S150 advanced development kit. The surge current values were found to be within acceptable limits.

Table 11 • M2S090 and M2S150 Surge Current During DEVRST_N Assertion (With Decoupling Capacitors on Board)

Kit	Width of Surge at 50% of Pulse	
	Surge Current	
M2S090 Security Evaluation Kit	5 μs	150 mA
M2S150 Advanced Development Kit	40 μs	1.5 A

The digest check system service performs on-chip NVM data integrity check on SmartFusion2 devices. The use of system services by digest check may cause additional surge current on VDD. For more information on digest check service, see the [UG0450: SmartFusion2 SoC and IGLOO2 FPGA System Controller User Guide](#).

The following table provides surge current data recorded for VDD when system services were being used by the digest check service. To limit surge current during digest check, follow the Microsemi-recommended board design guidelines.

Table 12 • Surge Current on VDD During Digest Check Using System Services (No Decoupling Capacitors on Board)

Device	Width of Surge at 50% of Pulse (μS)	Surge Current on VDD			Units
		0 °C to 85 °C	–40 °C to 100 °C	–55 °C to 125 °C	
M2S005/M2GL005	12	0.2	0.2	0.2	A
M2S010/M2GL010	12	0.5	0.5	0.5	A
M2S025/M2GL025	13	0.6	0.6	0.6	A
M2S050/M2GL050	13	0.9	0.9	0.9	A
M2S060/M2GL060	13	0.9	0.9	0.9	A
M2S090/M2GL090	20	1.0	1.0	1.0	A
M2S150/M2GL150	26	1.0	1.0	1.0	A

2.5 Clocks

SmartFusion2 devices have two on-chip RC oscillators and up to two crystal oscillators for generating clocks for the on-chip resources and logic in the FPGA fabric, as listed in the following table.

RC Oscillators:

- 1-MHz RC oscillator
- 50-MHz RC oscillator

Crystal Oscillators:

- Main crystal oscillator
- Auxiliary (RTC) crystal oscillator

All IGLOO2 devices and the M2S050 SmartFusion2 device only have a main crystal oscillator; they do not have an auxiliary (RTC) crystal oscillator.

Table 13 • Clock Circuit

Resource	SmartFusion2 SoC Part Number					IGLOO2 Part Number					
		M2S005	M2S010	M2S025	M2S050	M2S150	M2GL005	M2GL010	M2GL025	M2GL050	M2GL150
On-Chip Oscillators	RC Oscillators	2	2	2	2	2	2	2	2	2	2
	Crystal Oscillators	2	2	2	1	2	1	1	1	1	1

2.5.1 Main Crystal Oscillator

The main crystal oscillator works with an external crystal, ceramic resonator, or a resistor-capacitor network to generate a high-precision clock in the range of 32 kHz to 20 MHz and is connected via the pins XTLOSC_[MAIN/AUX]_EXTAL and XTLOSC_[MAIN/AUX]_XTAL.

The following table lists the output frequency range of the main crystal oscillator with different possible sources.


Table 14 • Crystal Oscillator Output Frequency Range

Source	Output Frequency Range
Crystal	32 kHz to 20 MHz
Ceramic resonator	500 kHz to 4 MHz
RC circuit	32 kHz to 4 MHz

The main crystal oscillator is operated in medium gain mode when a ceramic resonator is connected between the XTLOSC_[MAIN/AUX]_EXTAL and XTLOSC_[MAIN/AUX]_XTAL pins.

When a crystal is used, the load capacitance is determined by the external capacitors C_1 and C_2 , internal capacitance, and stray capacitance (C_S), as shown in the following figure.

Figure 5 • Crystal Oscillator

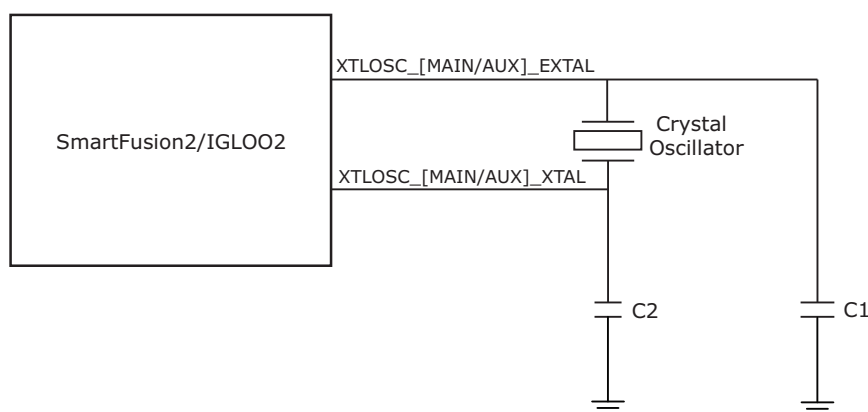

Typically, designers choose the values of capacitors C_1 and C_2 to match the crystal's capacitance C_L using the following equation:

$$C_L = \frac{C_1 \times C_2}{C_1 + C_2} + C_S$$

where:

C_L is the load capacitance provided in manufacturer datasheet.

C_S is stray capacitance on the PCB; this can be assumed to be in the range of 2 to 5 pF.

Usually C_1 and C_2 are selected such that they are equal.


Note: This equation is only a guideline, and selection of capacitors depends on design requirements such as cost, availability, frequency accuracy, PPM, and type of application.

Large values of C_1 and C_2 increase the frequency stability but decrease the loop gain and may cause oscillator startup problems. The basic rule of thumb is the values of C_1 and C_2 should be twice as that of C_L .


Suggested Crystal Oscillator

CRYSTAL 32.768 kHz 12.5 pF SMD	Citizen	CM519-32.768KEZF-UT
--------------------------------	---------	---------------------

The frequency generated by an RC network is determined by the RC time constant of the selected components, as shown in the following figure.

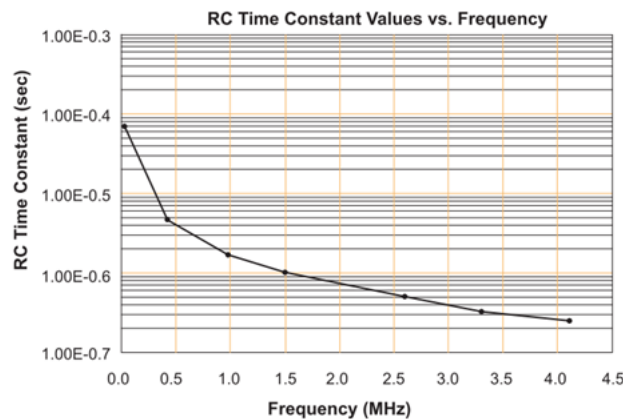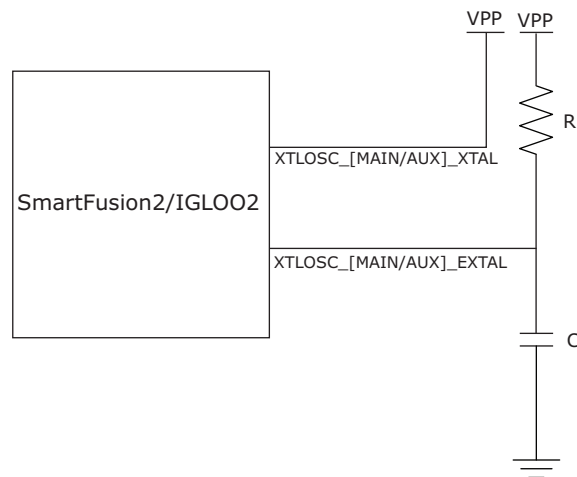Figure 6 • RC Time Constant

The R and C components are connected to the XTLOSC_[MAIN/AUX]_EXTAL pin, with the XTLOSC_[MAIN/AUX]_XTAL pin connected to the power pin VPP, as shown in the following figure.

Figure 7 • RC Oscillator

The operating mode of the main crystal oscillator is configured by the oscillator's macro available in Libero SoC.

2.5.2 Auxiliary (RTC) Crystal Oscillator

The SmartFusion2 devices, except M2S050, have an auxiliary crystal oscillator dedicated to real-time clocking as an alternative source for the 32 kHz clock. The RTC can take its 32 kHz clock source from the auxiliary crystal oscillator when the main crystal oscillator is being used.

Similar to the main crystal oscillator, the auxiliary crystal oscillator can work with an external crystal, ceramic resonator, or an RC circuit to generate a high-precision clock in the range of 32 kHz to 20 MHz. There are two I/O pads for connecting the external frequency source to the auxiliary crystal oscillator: XTLOSC_AUX_EXTAL and XTLOSC_AUX_XTAL. The output frequency range, operating modes, and characteristics for the auxiliary crystal oscillator are the same as those for the main crystal oscillator.

For detailed information, see the [UG0449: SmartFusion2 and IGLOO2 Clocking Resources User Guide](#).

Auxiliary (RTC) crystal oscillator is not available in the IGLOO2 device.

2.6 Reset Circuit


SmartFusion2/IGLOO2 devices have a dedicated asynchronous Schmitt-trigger reset input pin (DEVIRST_N) with a maximum slew rate not faster than 1 μ s. This active-low signal should be asserted only when the device is unresponsive due to some unforeseen circumstances. It is not recommended to

assert this pin during a programming (including eNVM) operation, as it may cause severe consequences including corruption of the device configuration. Asserting this signal tristates all user I/O and resets the system. Deasserting DEVRST_N enables the system controller to begin its startup sequence.

The following figure shows an example of a reset circuit using the Maxim DS1818 reset device, which maintains reset for 150 ms after the 3.3 V supply returns to an in-tolerance condition. Adding a capacitor to ground on DEVRST_N avoids high-frequency noise and unwanted glitches that could reset the device.


Note: Use DEVRST_N only for IAP or auto update. Do not use DEVRST_N for user logic reset.

Figure 8 • Reset Circuit

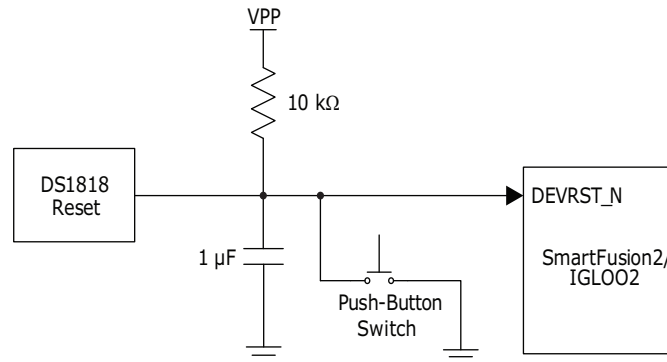


If the reset device is not used, DEVRST_N must be pulled up to VPP through a 10 kΩ resistor, as shown in the following figure.

Figure 9 • Without Reset Circuit

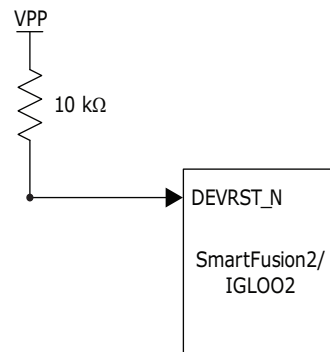

If the user logic needs to be reset, any FPGA I/O can be used as an asynchronous reset for the user logic, as shown in the following figure.

Figure 10 • Fabric Logic Reset

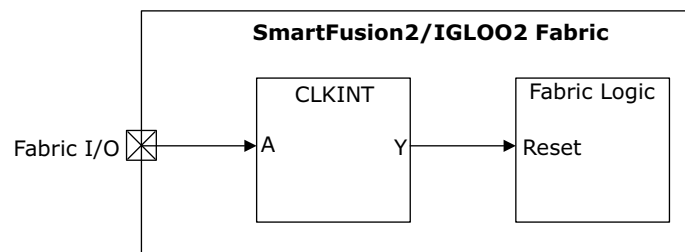

Use the fabric logic reset for CM3 Reset, fabric logic reset, MSS reset (including all peripherals), FDDR reset, SERDES reset. For more information about fabric reset, see the [MSS Reset Controller Configuration Guide](#).

2.7 Device Programming

The SmartFusion2/IGLOO2 device can be programmed via one of two dedicated interfaces: JTAG or SPI. These two interfaces support the following programming modes:

- Auto-programming (master) mode
- In-system programming:
 - JTAG programming mode
 - SPI Slave programming mode
- In-application update:
 - Cortex-M3 update mode (only for SmartFusion2 devices)
 - Auto update mode


For detailed information about programming the device, see the [UG0451: IGLOO2 and SmartFusion2 Programming User Guide](#).

2.7.1 JTAG Programming

The JTAG interface is used for device programming and testing or for debugging the Cortex-M3 firmware, as listed in the following table. These functions are enabled depending on the state of the JTAGSEL input. When the device reset is asserted, JTAG I/O are still enabled but cannot be used as the TAP controller is in reset. JTAG I/O are powered by VDDI in the I/O bank where they reside. JTAG pins must be connected as shown in the following figure.

Table 15 • JTAG Pins

Pin Names	Direction	Weak Pull-up	Description
JTAG_TMS	Input	Yes	JTAG test mode select.
JTAG_TRSTB	Input	Yes	JTAG test reset. Must be held low during device operation.
JTAG_TDI	Input	Yes	JTAG test data in.
JTAG_TCK	Input	No	JTAG test clock. Microsemi recommends that TCK be tied to VSS or VDDI through a resistor on the board when unused per IEEE 1532 requirements. This prevents totem-pole current on the input buffer.
JTAG_TDO	Output	No	JTAG test data out.
JTAGSEL	Input	Connect the JTAGSEL pin to an external pull-up resistor. The default configuration should enable the FPGA fabric TAP.	JTAG controller selection. Depending on the state of the JTAGSEL pin, an external JTAG controller connects to either the FPGA fabric TAP (high) or the Cortex-M3 JTAG debug interface (low). For SmartFusion2-based designs, this signal must be held high or low through jumper settings. For IGLOO2-based designs, this signal must be held high through a pull-up resistor.

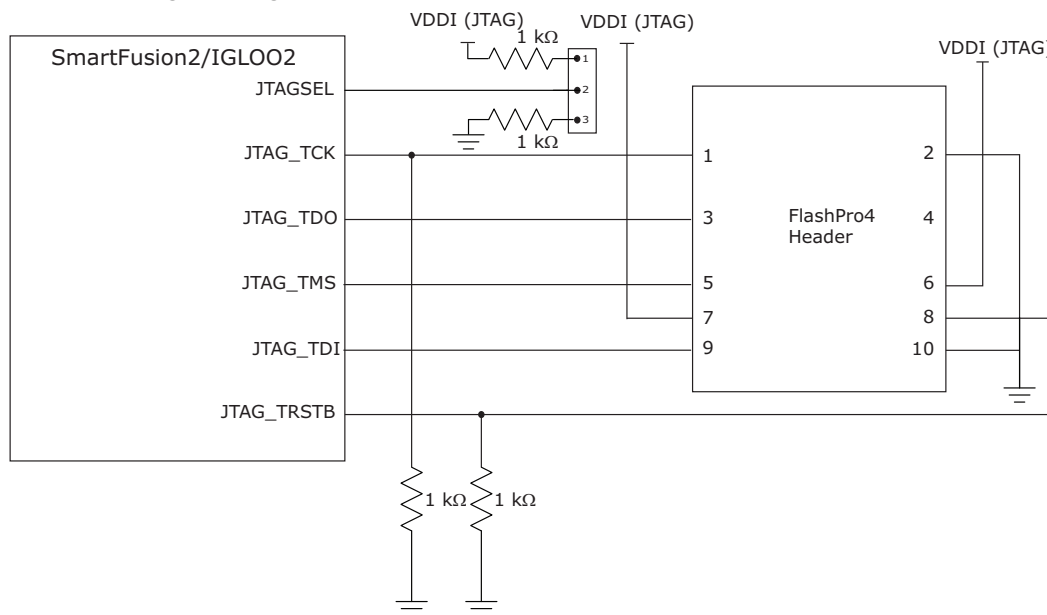
Figure 11 • JTAG Programming

2.7.2 SPI Master Programming

The SmartFusion2/IGLOO2 devices have dedicated pins for programming the device and probing the fabric I/O.

The embedded system controller contains a dedicated SPI block for programming, which can operate in master or slave mode. In master mode, the SmartFusion2/IGLOO2 device interfaces with the external SPI flash from which programming data is downloaded. In slave mode, the SPI block communicates with a remote device that initiates download of programming data to the device.

Figure 12, page 25 shows the board-level connectivity for SPI master mode programming in SmartFusion2 and IGLOO2 devices.

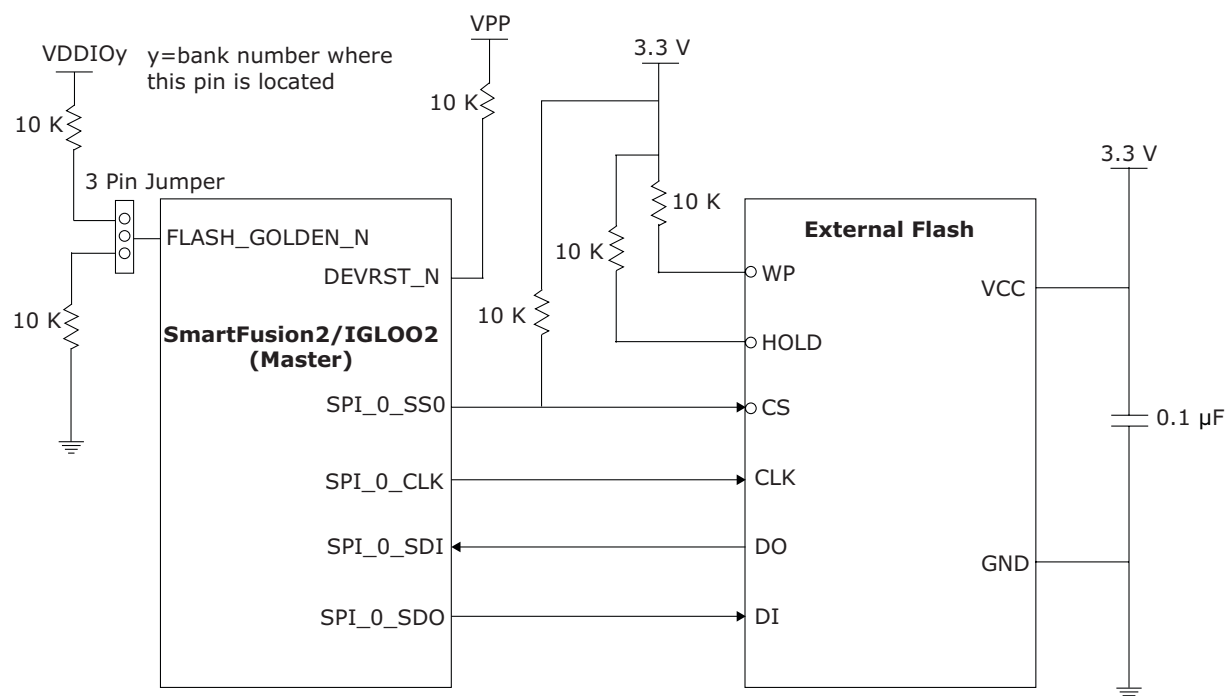Figure 12 • SPI Master Mode Programming

The following table lists the dedicated pins used for programming the device and probing the fabric I/O.

Table 16 • Dedicated Pins

Special Pins	Direction	Description
SPI_0_SDI	Input	Serial data input
SPI_0_SDO	Output	Serial data output
SPI_0_CLK	Output	Serial clock. It is a serial programmable bit rate clock out signal.
SPI_0_SSO ¹	Output	Slave select
FLASH_GOLDEN_N ¹	Input	If pulled low, the SPI_0 port is put into master mode, which indicates that the device is to be reprogrammed from an image in the external SPI flash attached to the SPI_0 interface.
NC		No connect. Indicates the pin is not connected to circuitry within the device. NC pins can be driven to any voltage or can be left floating with no effect on the operation of the device.
DNC		Do not connect. Must not be connected to any signals on the PCB. DNC pins must be left unconnected.
PROBE_A		The two live probe I/O pins are dual-purpose: - Live probe functionality - User I/O The unused live probe I/Os can be configured as weak pull-up resistors, and these pins can be connected to the 10 kΩ external resistor. The 10 kΩ external resistor power supply must be the same as the I/O bank power supply (VDDI).
PROBE_B		


1. Active Low Signal.

For more information about programming, see [UG0451: SmartFusion2 and IGLOO2 Programming User Guide](#).

2.7.3 SPI Slave Programming


The following figure shows the SmartFusion2/IGLOO2 SPI slave programming configuration when an external processor is the master.

Figure 13 • SPI Slave Programming by External Microprocessor

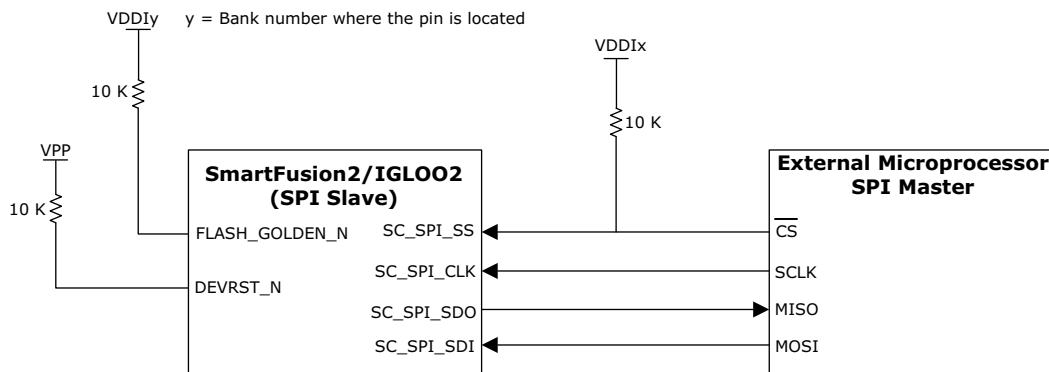

The following figure shows the SmartFusion2/IGLOO2 SPI slave programming configuration when an external programmer is the master.

Figure 14 • SPI Slave Programming by External Programmer

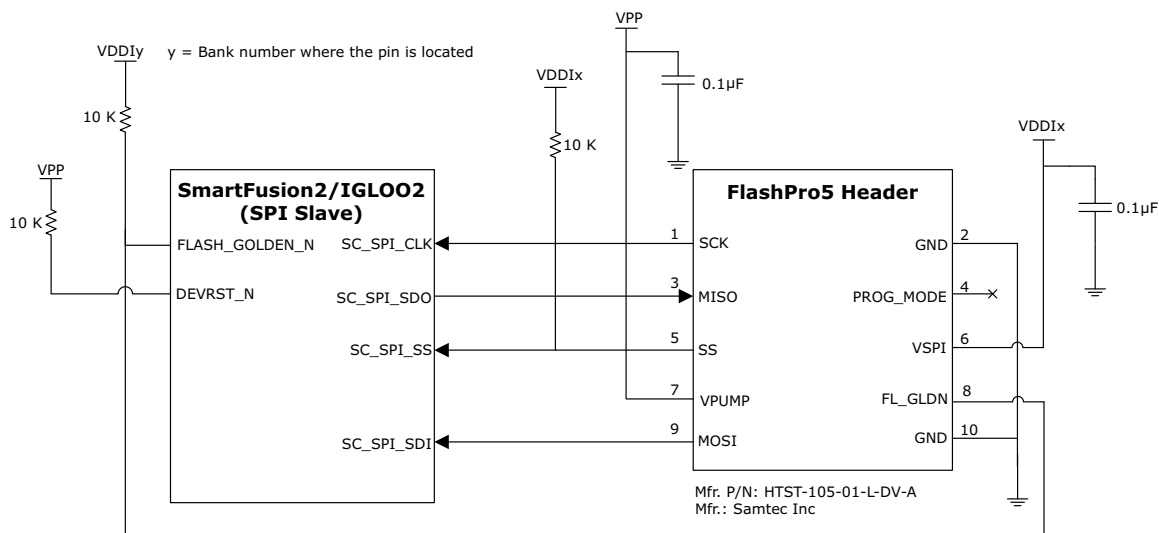


2.8 SerDes

SmartFusion2/IGLOO2 SerDes I/O reside in dedicated I/O banks. The number of SerDes I/O depends on the device size and pin count. For example, the M2S050T/M2GL050T device has two SerDes blocks (SERDES0 and SERDES1), which reside in bank 6 and bank 9 out of 10 I/O banks. The M2S010T/M2GL010T device has a single SerDes block (SERDES0), which resides in I/O bank 5.

2.8.1 PCI Express (PCIe)

PCIe is a point-to-point serial differential low-voltage interconnect supporting up to four channels. Each lane consists of two pairs of differential signals: a transmit pair, TXP/TXN, and receive pair, RXP/RXN. The following figure illustrates the connectivity between the SmartFusion2/IGLOO2 SerDes interface and the PCIe edge connector.

Figure 15 • SerDes Schematics

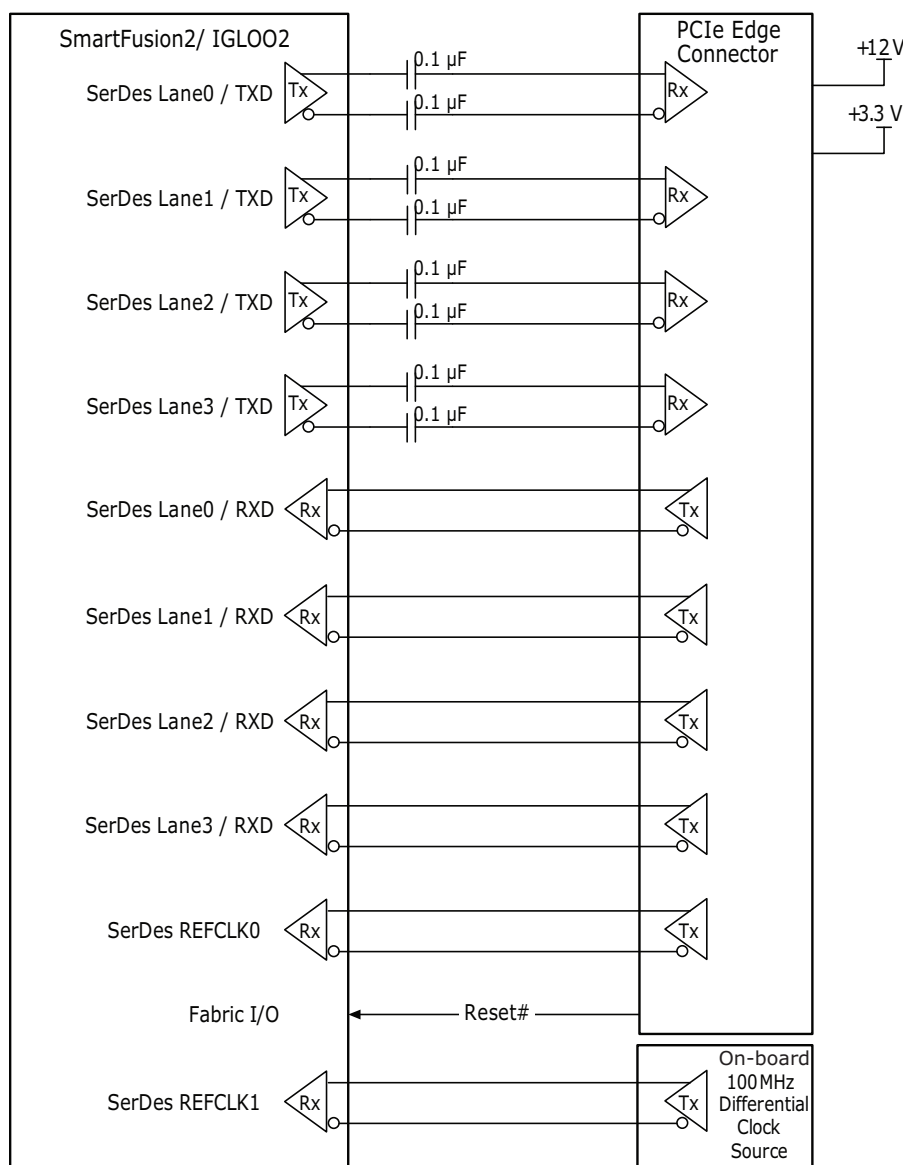

2.8.2 AC Coupling

Each transmit channel of a PCIe lane must be AC coupled to allow link detection. Capacitors used for AC coupling must be external to the device and large enough to avoid excessive low-frequency drops when the data signal contains a long string of consecutive identical bits.

For non-PCIe applications, the SmartFusion2/IGLOO2 device requires the receive inputs to be AC coupled to prevent common-mode mismatches between devices. Suitable values (for example, 0.1 μ F) for AC-coupling capacitors must be used to maximize link signal quality and must conform to [DS0128: IGLOO2 and SmartFusion2 Datasheet](#) electrical specifications.

2.8.3 SerDes Reference Clock Requirements

The selection of the reference clock source or clock oscillator is driven by many parameters such as frequency range, output voltage swing, jitter (deterministic, random, and peak-to-peak), rise and fall times, supply voltage and current, noise specification, duty cycle and duty cycle tolerance, and frequency stability.

For SerDes reference clock pins, the internal ODT option should be enabled, and therefore, external termination is not required.

Following are the requirements for the SerDes reference clock:

- Must be within the range of 100 MHz to 160 MHz.
- Must be within the tolerance range of the I/O standard.
- The input clock for PCIe is typically a 100 MHz reference clock provided by the host slot for an end point device through the PCIe connector of the motherboard. If two components connected through the PCIe bus use the same 100 MHz clock source, it is called common clock mode. In any other case, the PCIe device is in separated clock mode where one component either does not use a 100 MHz reference clock or uses a 100 MHz reference clock that does not have the same source and phase as the one used by the connected component.

See the PCI Express Base specification Rev 2.1 for detailed PHY specifications. Also see the PCIe Add-in Card Electro-Mechanical (CEM) specifications.

2.8.4 PLL Filter

To obtain a reasonable level of long-term jitter, it is vital to supply the PLL with analog-grade power. Typically, an RC or RLC filter is used, where C is composed of multiple devices to obtain a wide spectrum of noise absorption. Although the circuit is simple, its effectiveness depends on specific board layout requirements. See [Figure 1](#), page 5 for an illustration of a typical power supply connection.

- The DC series resistance of this filter should be limited. Microsemi recommends limiting the voltage drop across this device to less than 5% under worst-case conditions.
- Place a main ceramic or tantalum capacitor (see [Figure 1](#), page 5), in the filter design to obtain good low-frequency cut-off. At least one low equivalent series inductance (ESL) and low ESR capacitor in parallel (~0.1 μ F ceramic capacitor in 0402 package) enables the filter to maintain its attenuation through moderately high frequencies.
- The package ball grid array (BGA) pattern allows the placement of 0402 or 0201 components across the SERDES_x_Lyz_VDDAPLL and SERDES_x_Lyz_REFRET pins on the backside of the board.
- For the SerDes block, SERDES_x_Lyz_REFRET serves as the local on-chip ground return path for SERDES_x_Lyz_VDDAPLL. Therefore, the external board ground must not get shorted with SERDES_x_Lyz_REFRET under any circumstances.
- High-quality series inductors must not be used without a series resistor when there is a high-gain series resonator. In general, avoid using inductive chokes in any supply path unless care is taken to manage resonance.

See [Figure 1](#), page 5 for SerDes analog power connections. A high-precision 1.2 K Ω , 1% resistor in either a 0402 or 0201 package is required for the external reference resistor connected between SERDES_x_Lyz_REXT and SERDES_x_Lyz_REFRET.

2.9 LPDDR, DDR2, and DDR3

DDRIO is a multi-standard I/O buffer optimized for LPDDR, DDR2, and DDR3 performance.

SmartFusion2/IGLOO2 devices include two DDR subsystems: the fabric DDR controllers (FDDR) and microcontroller subsystem (MSS) DDR (MDDR) controllers. All DDRIO can be configured as differential I/O or two single-ended I/O. DDRIO can be connected to the respective DDR sub-system PHYs or can be used as user I/O.

For more information on FDDR and MDDR, see the [SmartFusion2 FPGA Fabric DDR Controller Configuration Guide](#) and [SmartFusion2 MSS DDR Controller Configuration Guide](#).

The following table lists the differences between LPDDR, DDR2, and DDR3.

Table 17 • LPDDR/DDR2/DDR3 Parameters

Parameter	LPDDR	DDR2	DDR3
VDDQ	1.8 V	1.8 V	1.5 V
VTT, VREF		0.9 V	0.75 V
Clock, address, and command (CAC) layout	Asymmetrical tree branch	Symmetrical tree branch	Daisy chained (fly-by)
Data strobe	Single-ended	Differential	Differential
ODT	None	Static	Dynamic
Match Addr/CMD/Ctrl to clock tightly	Yes	Yes	Yes
Match DQ/DM/DQS tightly	Yes	Yes	Yes
Match DQS to clock loosely	Yes	Yes	Not required
Interface	LVC MOS ₁₈ or SSTL18 for LPDDR1	SSTL ₁₈	SSTL ₁₅
Impedance Calibration	LVC MOS ₁₈ - Not required SSTL18 - Required	150_1%	240_1%

One major difference between DDR2 and DDR3 SDRAM is the use of data leveling. To improve signal integrity and support higher frequency operations, a fly-by termination scheme is used with the clocks, command, and address bus signals. Fly-by termination reduces simultaneous switching noise by deliberately causing flight-time skew between the data strobes at every DDR3 chip. Fly-by termination requires controllers to compensate for this skew by adjusting the timing per byte lane. To obtain length matching, short TMATCH_OUT to TMATCH_IN with the shortest loop.

For more information about DDR memories, refer to the following documents:

- JESD209B-JEDEC STANDARD—Low Power Double Data Rate (LPDDR) SDRAM Standard
- JESD79-2F-JEDEC STANDARD—DDR2 SDRAM Specification
- JESD79-3F-JEDEC STANDARD—DDR3 SDRAM Standard

2.9.1 MDDR/FDDR Impedance Calibration

The MDDR and FDDR have a DDRIO calibration block. DDRIO can use fixed impedance calibration for different drive strengths, and these values can be programmed using the Libero SoC software for the selected I/O standard.

Before initiating DDRIO impedance calibration, either of the following must be done:


- Power sequencing, where the DDRIO bank VDDI_x supply must be up and stable before VDD core supply.
- DDRIO re-calibration through the APB interface after DDRIO- VDDI_x and VDD are up and stable.

For more information on impedance calibration, see the [UG0445: SmartFusion2 SoC and IGLOO2 FPGA Fabric User Guide](#).

2.9.2 VREF Power

VREF is a low-power reference voltage equal to half of VDDQ. It must also be equal to $V_{TT} \pm 40$ mV. The following figure shows the VREF generation circuit.

Figure 16 • VREF Generation

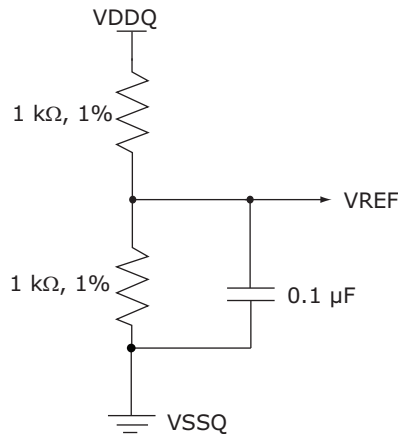

The following are the guidelines for connecting VREF power:

- For light loads (less than four DDR components), connect VDDQ to VSSQ through a simple resistor divider composed of two equivalent 1% 1 kΩ resistors (Figure 16, page 30).
- Generate a local VREF at every device, rather than generating a single VREF with one divider and routing it from the controller to the memory devices.
- Decouple at each device or connector to minimize noise.

Note: Use discrete resistors, not a resistor pack, to generate VREF.

2.9.3 VTT Power


VTT is memory bus termination voltage. To maintain noise margins, VTT must be equal to $V_{DDQ}/2$, with an accuracy of $\pm 3\%$. VTT terminates command and address signals to $V_{DDQ}/2$ using a parallel resistor (RT) tied to a low impedance source.

VTT is not used to terminate any DDR clock pairs. Rather, the xDDR_CLK and xDDR_CLK_N termination consists of a parallel 100-121 Ω resistor between the two lines.

- VTT islands require a 10μF capacitor.
- Since each data line is connected to VTT with relatively low impedance, this supply must be extremely stable. Any noise on this supply directly affects the data lines.
- Sufficient bulk and bypass capacitance must be provided to keep this supply at $V_{DDQ}/2$. VREF power should not be derived from VTT, but must be derived from VDDQ with a 1% or better resistor divider.

2.9.4 LPDDR and DDR2 Design


This document assumes that the designer is familiar with the specification and the basic electrical operation of the LPDDR/DDR2 interface. Data bus, data strobe, and data mask (byte enable) signals are point-to-point, whereas all other address, control, and clock signals are not point-to-point. Figure 17, page 31 and Figure 18, page 32 show the connectivity of the SmartFusion2/IGLOO2 LPDDR interface and a 32-bit DDR2 interface respectively.

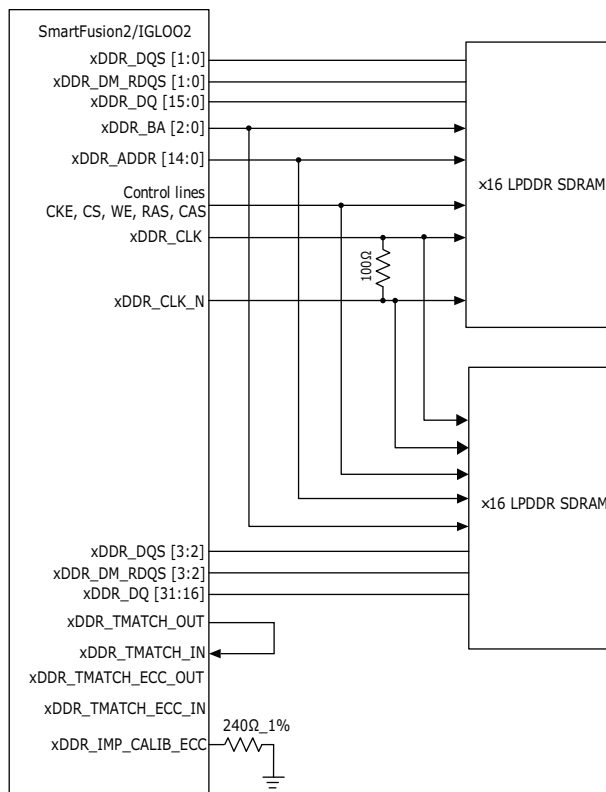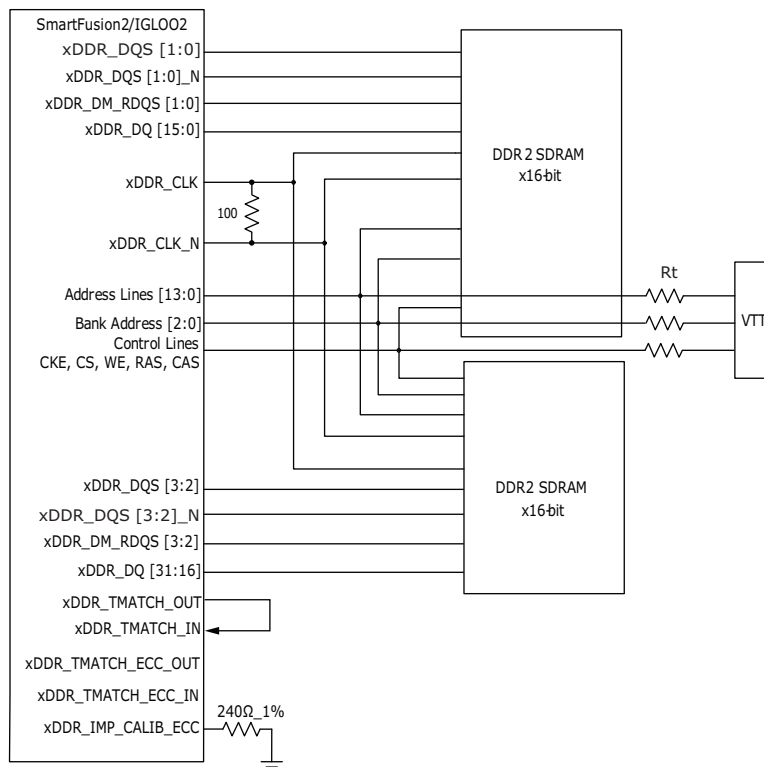Figure 17 • LPDDR Interface

Note: Impedance calibration is optional for LPDDR operating in LVCMOS mode and is required for LPDDR1 operating in SSTL18 mode.

Note: For a 4- or 8-bit DRAM, all DQ pins are interchangeable. All 4- and 8-bit DQ pins are interchangeable in LPDDR, DDR2, and DDR3 memories. For a 16-bit DRAM, DQ0 through DQ7 are interchangeable. Also, DQ8 through DQ15 are interchangeable. However, DQ0-7 pins or signals *must not* be interchanged with the DQ8-15 pins or signals.

Note: Short ECC_TMATCH_OUT and ECC_TMATCH_IN when using ECC bits.

Figure 18 • DDR2 Interface

With short traces, the address, control, and command signals may not require both parallel (RT) and series (RS) termination. In a worst-case scenario, a small series resistor (RS) of about 10 Ω or less is required. This series termination is not used for impedance matching, but for dampening the signals.

Note: To get length matching, short the TMATCH_OUT to TMATCH_IN with the shortest loop.



Note: Short ECC_TMATCH_OUT and ECC_TMATCH_IN when using ECC bits.

2.9.5 DDR3 Guidelines

The following are the guidelines for connecting to the DDR3 memory:

- DDR3 data nets have dynamic on-die termination (ODT) built into the controller and SDRAM. The configurations are 40 Ω, 60 Ω, and 140 Ω. VTT pull-up is not necessary.
- Characteristic impedance: Z_0 is typically 50 Ω, and Z_{diff} (differential) is 100 Ω.

DDR3 interfacing with SmartFusion2/IGLOO2 devices for 8-bit and 16-bit interfaces is shown in [Figure 19](#), page 33 and [Figure 20](#), page 33.

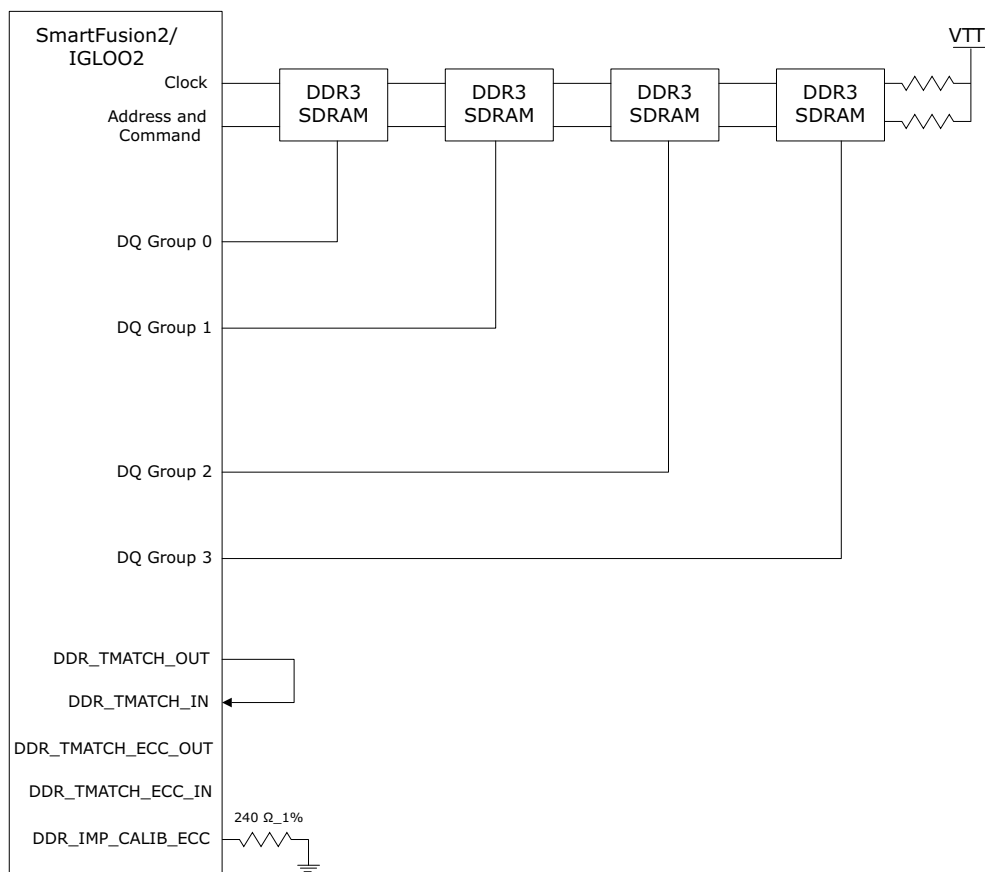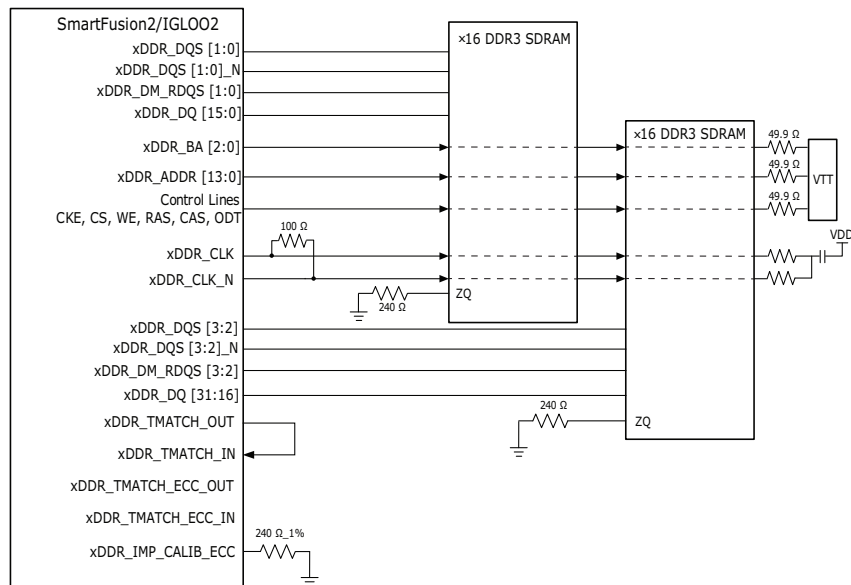Figure 19 • 8-Bit DDR3 Interface**Figure 20 • 16-Bit DDR3 Interface**

Note: Short ECC_TMATCH_OUT and ECC_TMATCH_IN when using ECC bits.

2.10 User I/O and Clock Pins

The following table lists recommendations for unused I/O and clock pins in a SmartFusion2/IGLOO2 device.

Table 18 • Recommendations for Unused I/O and Clock Pins


I/O	Unused Condition	Remarks
MSIO	Libero-Defined DNC ¹	Internal weak pull-up is available
MSIOD		
DDRIO		
Programming SPI pins		
Crystal oscillator pins	Must be left floating and must not connect to ground (VSS)	Internal weak nominal 50 k Ω pull-up to VPP

1. Libero configures unused user I/O (MSIO, MSIOD, and DDRIO) as: input buffer disabled, output buffer tristated with weak pull-up.

2.10.1 Internal Clamp Diode Circuitry

All user I/Os have an internal clamp diode control circuitry, as shown in the following figure. A pull-up clamp diode must not be present in the I/O circuitry if the hot-swap feature is used. The 3.3 V PCI standard requires a pull-up clamp diode and, therefore, cannot be selected if hot-swap capability is required.

Figure 21 • Internal Clamp Diode Control Circuitry

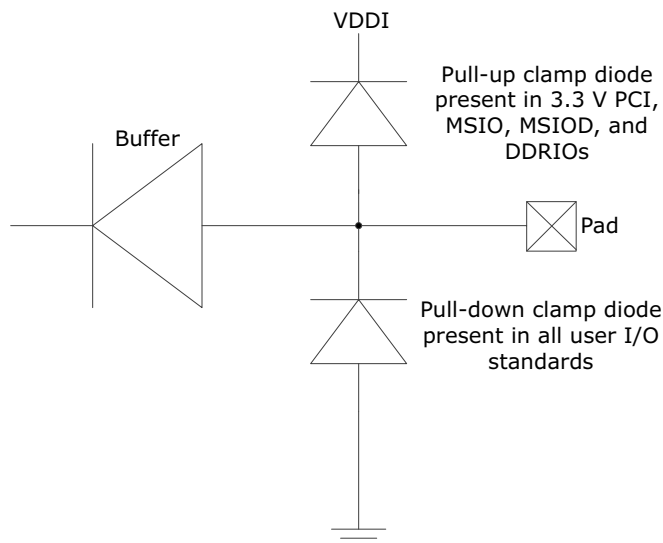

For more information about hot swapping and cold sparing applications, see the [AC396: SmartFusion2 and IGLOO2 in Hot Swapping and Cold Sparing Application Note](#).

2.11 Obtaining a Two-Rail Design for Non-SerDes Applications

SmartFusion2/IGLOO2 devices require multiple power supplies for functional operation, programming, and high-speed serial interfaces. It is possible to design an application with only two voltage rails using SmartFusion2/IGLOO2 devices.

I/O banks in SmartFusion2 and IGLOO2 devices support a wide range of I/O standards. I/O bank supplies can operate at +1.2 V, +1.5 V, +1.8 V, +2.5 V, or +3.3 V. To obtain a two-voltage-rail design, the core voltage should be connected to +1.2 V, and the mandatory I/O bank supplies and VPP supplies can be connected to +2.5 V or +3.3 V.

2.11.1 Operating Voltage Rails

SmartFusion2/IGLOO2 devices require +1.2 V for the core supply and either +2.5 V or +3.3 V for I/O and analog supplies. The following table lists operating voltage requirements for the devices.

Table 19 • Operating Voltage Rails

Pin Name	Description	Operating Voltage
VDD	DC core supply voltage.	+1.2 V
VDDIx ¹	I/O bank supply.	+1.2 V, +1.5 V, +1.8 V, +2.5 V, or +3.3 V
SERDES_x_VDD	PCIe/PCS supply.	+1.2 V
SERDES_x_L[01/23]_VDDAIO	Tx/Rx analog I/O voltage. Low-voltage power for lanes 0, 1, 2, and 3 of the SerDes interface.	+1.2 V
VPP ²	Power supply for charge pump.	+2.5 V or +3.3 V
VPPNVM ¹	Analog sense-circuit supply for the embedded non-volatile memory (eNVM).	+2.5 V or +3.3 V
CCC_xyz_PLL_VDDA	Analog power pad for CCC PLL.	+2.5 V or +3.3 V
MSS/HPMS_xDDR_PLL_VDDA	Analog power pad for xDDR PLL.	+2.5 V or +3.3 V
SERDES_x_PLL_VDDA	High supply voltage for SerDes PLL.	+2.5 V or +3.3 V
SERDES_x_L[01/23]_VDDAPLL	Analog power for SerDes PLL of lanes 0, 1, 2, and 3.	+2.5 V


1. The 3.3 V supply can be connected to MSIO VDDIx bank only.

2. For M2S090T(S), M2S150T(S) devices, VPP, and VPPNVM must be connected to +3.3 V.

2.12 Configuring Pins in Open Drain

To configure fabric pins in open-drain mode, the input port of the tristate buffer must be tied low, and the enable port of the buffer must be driven from the user logic via the fabric port, as shown in the following figure.

Figure 22 • Configuring Pins in Open Drain

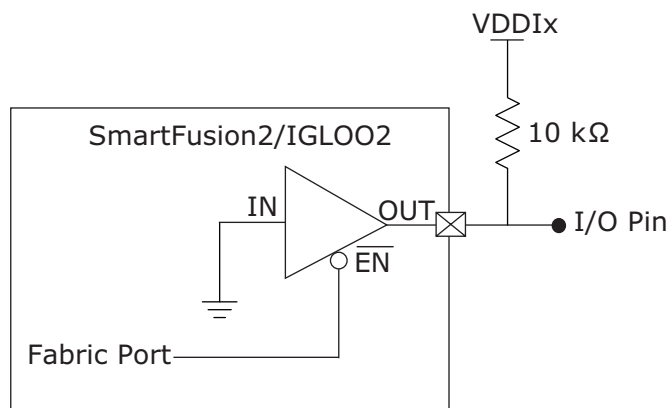

The following table lists the truth table for configuring pins in open-drain mode.

Table 20 • Truth Table

Buffer Enable Port	Buffer In Port	Buffer Out Port
0 (low)	0 (low)	0 (low)
1 (high)	0 (low)	VDDI _X

2.13 Brownout Detection (BOD)


SmartFusion2/IGLOO2 functionality is guaranteed only if VDD is above the recommended level specified in the datasheet. Brownout occurs when VDD drops below the minimum recommended operating voltage. As a result, it is not possible to ensure proper or predictable device operation. The design might continue to malfunction even after the supply is brought back to the recommended values, as parts of the device might have lost functionality during brownout. The VDD supply must be protected by a brownout detection circuit.

To recover from VDD brownout, the device must either be power-cycled, or an external brownout detection circuit must be used to reset the device for correct operation. The recommended guideline for the threshold voltage of brownout detection is mentioned in “Table 14” of [DS0128: IGLOO2 and SmartFusion2 Datasheet](#). The brownout detection circuit must be designed such that when the VDD falls below the recommended voltage mentioned in the datasheet, the device is held in power-down mode via the DEVRST_N pin.

Note: Brownout detection must be implemented through a standalone circuit or included as part of power management circuitry.

SmartFusion2/IGLOO2 devices do not have a built-in brownout detection circuitry, but an external brownout detection circuitry can be implemented as shown in the following figure.

Figure 23 • BOD Circuit Implementation

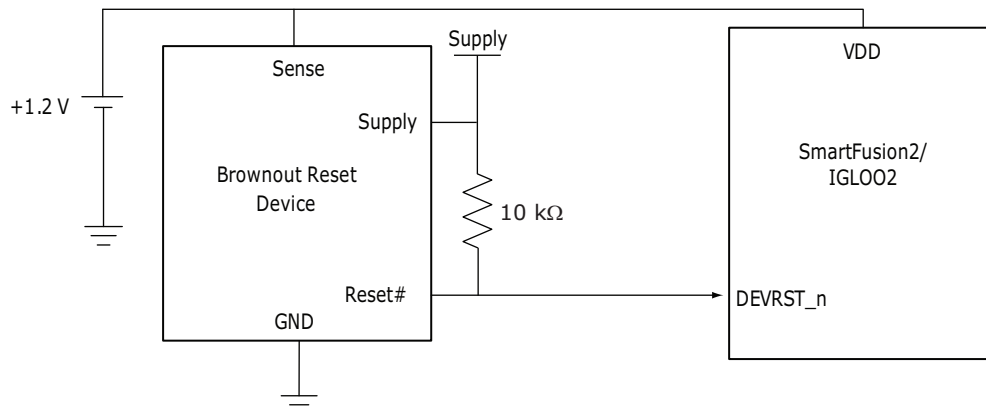

The BOD device must have an open-drain output to connect to VPP through a 10 kΩ resistor externally. During power-on, the brownout reset keeps the device powered down until the supply voltage reaches the threshold value. Thereafter, the brownout reset device monitors VDD and keeps RESET# output active as long as VDD remains below the threshold voltage. An internal timer delays the return of the output to the inactive state (high) to ensure proper system reset.

The delay time is in milliseconds and starts after VDD has risen above the threshold voltage. When the supply voltage drops below the threshold voltage, the output becomes active (low) again.

2.14 Simultaneous Switching Noise

When multiple output drivers switch simultaneously, they induce a voltage drop in the chip or package power distribution. The simultaneous switching momentarily raises the ground voltage within the device relative to the system ground. This apparent shift in the ground potential to a non-zero value is known as simultaneous switching noise (SSN) or, more commonly, ground bounce.

For SSO guidelines for SmartFusion2 and IGLOO2 I/Os, see [UG0445: SmartFusion2 SoC FPGA and IGLOO2 FPGA Fabric User Guide](#).

3 Layout Guidelines for SmartFusion2- and IGLOO2-Based Board Design

This chapter provides guidelines for the hardware board layout that incorporates SmartFusion2 SoC FPGA or IGLOO2 FPGA devices. Good board layout practices are required to achieve the expected performance from the printed circuit boards (PCB) and SmartFusion2/IGLOO2 devices. These are essential to achieve high quality and reliable results such as low-noise levels, signal integrity, impedance, and power requirements. The guidelines mentioned in this document act as a supplement to the standard board-level layout practices.

This chapter assumes that the users have a good understanding of the SmartFusion2/IGLOO2 chip, experience in digital and analog board layout, and knowledge of transmission line theory and signal integrity. For more information about the recommended guidelines for designing SmartFusion2/IGLOO2-based boards, see [Board Design Guidelines for SmartFusion2 SoC and IGLOO2 FPGAs](#), page 4.

Note: The target impedance calculated in this document is with respect to the development board. The simulations show the impedance that meets the target impedance of the development board. The target impedance depends on the logic implemented on SmartFusion2/IGLOO2; hence Microsemi recommends calculating the target impedance of the board.

3.1 Power Supply

In power supply design, it is important to know the target impedance of the power planes. The target impedance varies depending on the design. This helps in planning the requirement of the number of decoupling capacitors based on the target impedance. The number of decoupling capacitors varies based on the design.

Complex FPGA designs have increasing amounts of current transients switching across the power bus. Simultaneously switching outputs (SSO) contribute a major share of instantaneous current issues. Decoupling is necessary to prevent the instantaneous currents. Decoupling is only effective when inductance is minimized. Low inductance decoupling provides localized high frequency energy to decouple noise from the switching currents of the device power bus. This is most effective when capacitors are in close proximity to the device. Some of these high-frequency de-coupling capacitors must be placed directly under the FPGA or on single side. These capacitors must be placed close to the power and ground pins of the device and routed with thick trace.

To calculate the number of decoupling capacitors, it is important to know the target impedance of the power plane. Target impedance is calculated as follows:

$$Z_{\text{Max}} = \% \text{ Ripple} \times \frac{V_{\text{supply}}}{I_{\text{trans}}}$$

Where,

V_{supply}: Supply voltage of the power plane.

% Ripple: % of ripples allowed on the power plane; see [DS0128: IGLOO2 and SmartFusion2 Datasheet](#) for more information about ripple in Recommended Operating Conditions table.

I_{trans}: Transient current drawn on the power plane. Generally, the transient current is half of the maximum current. Maximum current is taken from the power calculator sheet.

Z_{max}: Target impedance of the plane.

Subsequent sections display simulation results based on target impedance calculated using preceding equation. Microsemi strongly recommends calculating the target impedance and performing simulations for the impedance profile of the power plane. These simulations help in optimizing the decoupling capacitors to reduce the production cost and have the optimal placement. The plane shapes given in this document are with reference to the [UG0557: SmartFusion2 SoC FPGA Advanced Development Kit User Guide](#). This may vary depending on the design. For simulation topology, see [Appendix: Power Integrity Simulation Topology](#), page 94.

SmartFusion2/IGLOO2 power supplies are classified as:

- Core power supply
- I/O power supply
- Serializer/deserializer (SerDes) power supply
- Double data rate (DDR) power supply
- Phase-locked loop (PLL) power supply


3.2 Core Supply (VDD)

The core power supply must have a low-noise and low-ripple voltages, as per datasheet. Proper care should be taken while designing the power supply (VDD) for core. Proper placement of decoupling capacitors and plane geometry greatly influences the power supply distribution going into SmartFusion2/IGLOO2 device.


3.2.1 Component Placement

- The bulk capacitors (330 μF and 100 μF) should be placed near by the SmartFusion2/IGLOO2 device.
- The bypass capacitors (47 μF and 22 μF) should be placed near or if possible, on the periphery of the device. The placement on the SmartFusion2 Development Kit board is shown in the following figure.

Figure 24 • Placement of Capacitors for VDD Plane

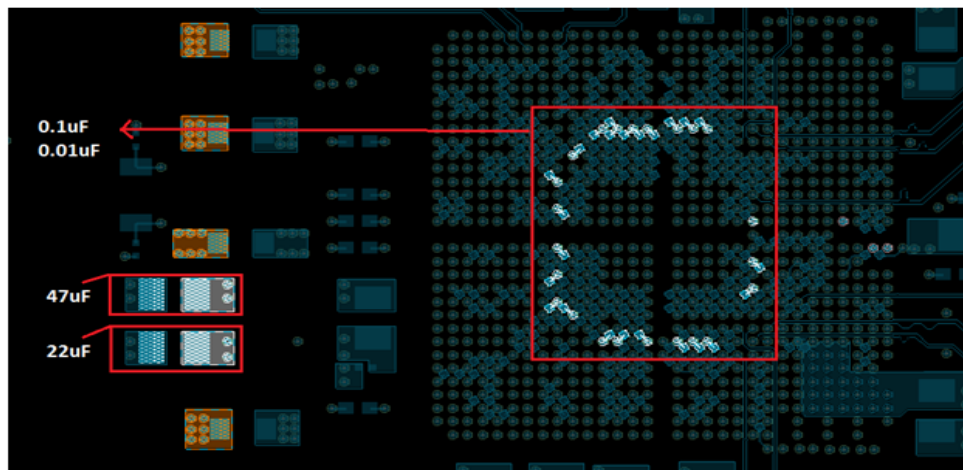


- All decoupling capacitors (0.1 μF and 0.01 μF) should be 0402 or of a smaller package size, as they are required to be mounted on the back side of the board. They should be fit between the adjacent vias of ball grid array (BGA) package pins. These decoupling capacitors are selected to have a low impedance over operating frequency and temperature range. Capacitor pad to via trace should be as small as possible. The following figure shows how these capacitors need to be mounted. Microsemi recommends keeping the capacitor pad directly on the corresponding vias. The capacitors should not share ground vias. Each decoupling capacitor should have its own via connection to the PCB ground plane.
- The De-coupling capacitor and the Smart Fusion2\IGOOOL2 device can be placed side by side. If placed side by side, route the power with thick traces. Microsemi does not guarantee on noise on power rails. User must run the power simulation.

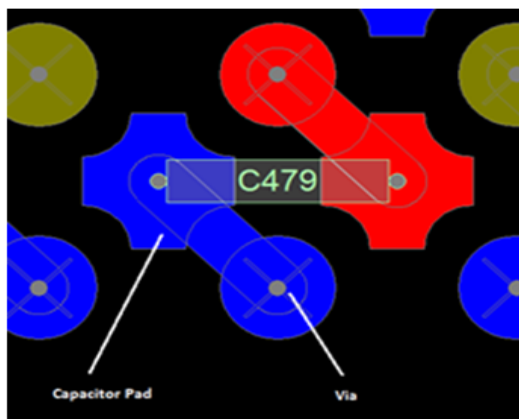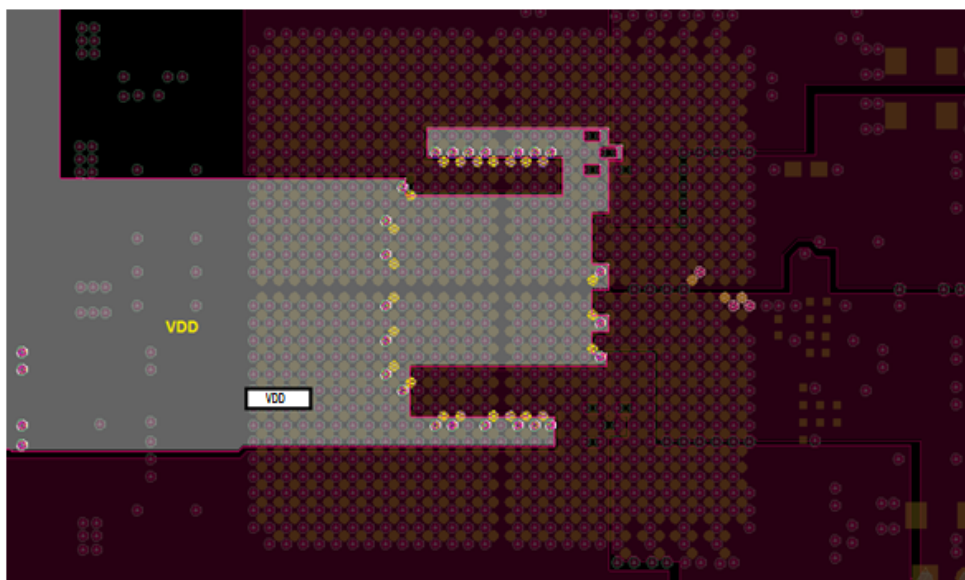Figure 25 • Capacitor Placement under BGA Vias

3.2.2 Plane Layout

Microsemi recommends using the VDD plane, as shown in the following figure.

Note: The plane can be routed in multiple ways. The goal is to have a dedicated and low-impedance plane.


Figure 26 • VDD Plane

3.2.3 Simulations

The effect of the decoupling capacitors can be visualized through the power integrity simulations. The target impedance of the VDD is calculated as 40 mΩ, based on the following values:

- $V_{SUPPLY} = 1.2\text{ V}$
- $I_{trans} = 1.5\text{ A}$
- Ripple = 5%

Figure 27, page 41 shows the impedance profile of the VDD plane of the SmartFusion2 Development Kit. It shows that the capacitors used are adequate to improve the impedance profile over the bandwidth. Good coupling between the planes can be achieved by having power and ground plane in adjacent layers. Once all the capacitors (0.1 μF and 0.01 μF) are placed, the impedance of the VDD plane impedance profile improves over the frequency range. The simulation results shown in this document are done in Sigrity PowerSI tool. For more information on how to do the simulation, see the *Sigrity PowerSI Tutorial*.

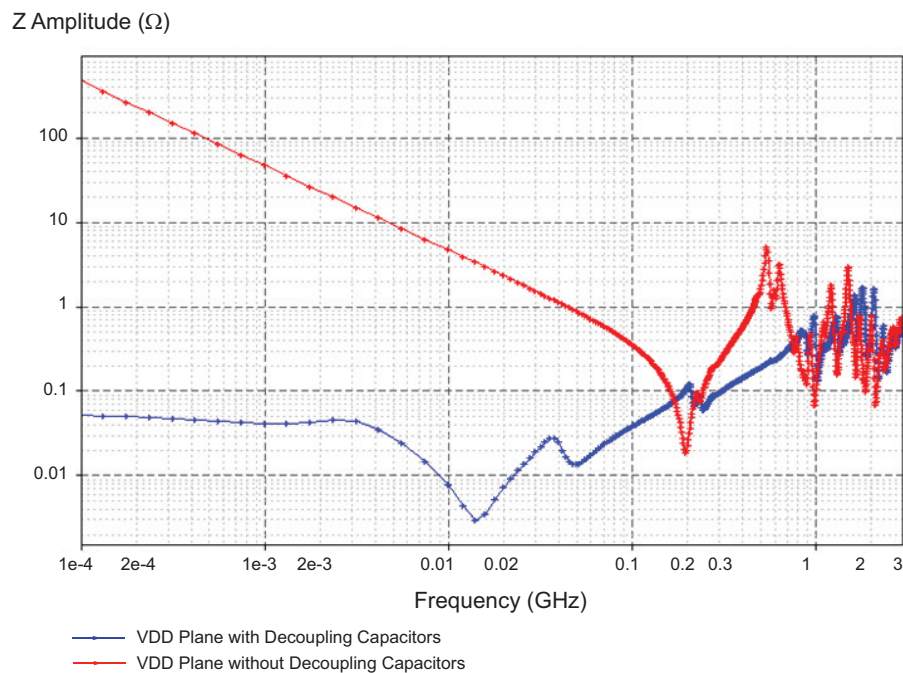Figure 27 • Impedance Profile of VDD Plane with Respect to Frequency

3.3 SerDes

PCB designers often overlook the requirement of isolating the noise generated by the digital components with the SerDes high-speed designs. It is necessary to provide a low-noise supply for the sensitive analog portions of the SerDes devices. Noise due to various power supply voltages can be coupled into the analog portion of the chip and may produce unwanted fluctuations in the sensitive stages of the device. The performance of SerDes highly depends on robust layout techniques. This section discusses the layout guidelines for power supply for the SerDes and the SerDes PLL.

3.3.1 Component Placement

3.3.1.1 Core Power (SERDES_x_VDD)

- All decoupling capacitors (0.1 μ F and 0.01 μ F) are placed on the pad adjacent to the BGA via of the corresponding pin, as shown in [Figure 25](#), page 40. The capacitor pad to via trace should be as small as possible. At least one 0.1 μ F and one 0.01 μ F capacitors should be placed for each SerDes bank.
- The bypass capacitor (10 μ F) should be placed at the edge of the integrated circuit (IC).


3.3.1.2 SerDes I/O Power (SERDES_x_VDDAIO)

- All decoupling capacitors (0.1 μ F and 0.01 μ F) are placed on the pad adjacent to the BGA via of the corresponding pin, as shown in [Figure 24](#), page 39. At least one of the capacitors (0.1 μ F and 0.01 μ F) should be placed for each SerDes bank. The capacitor pad to via trace should be as small as possible.
- The bypass capacitor (10 μ F) should be placed at the edge of the IC.

3.3.1.3 SerDes PLL

There are two power supply nodes required for SerDes. One is SERDES_x_VDDAPLL and another is SERDES_x_PLL_VDDA. Both of these supplies require separate filter circuits. Filter circuit for SERDES_x_VDDAPLL is shown in the following figure. A typical filter circuit for SERDES_x_PLL_VDDA is shown in the following figure.

Figure 28 • Filter Circuit for SerDes PLL Power Supply

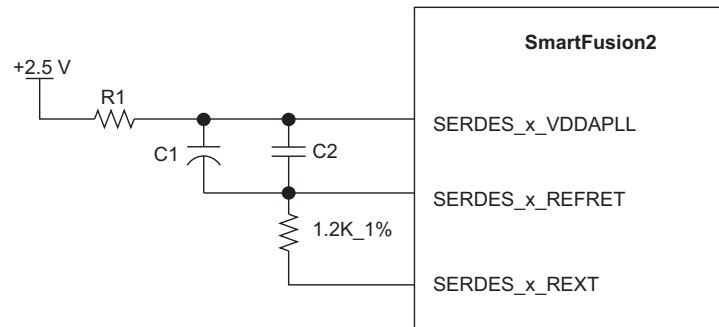

- C1 and R1 should be placed near the device.
- C2 should be placed under the BGA via. The capacitor pad to via trace should be as small as possible.
- Apart from this, a precision resistor (1.2 K) is placed between the SERDES_x_REXT and SERDES_x_REFRET pins. This resistor should be placed near the BGA via of SERDES_x_REXT pin. Any aggressive signal traces should be kept away from this resistor to avoid unwanted noise from coupling into this critical circuit. A sample placement is shown in the following figure.

Figure 29 • Component Between 1.2 K Resistor and K6 Pin




For more information about R1, C1, and C2, see [Board Design Guidelines for SmartFusion2 SoC and IGLOO2 FPGAs](#), page 4.

3.3.2 Plane Layout

3.3.2.1 SerDes Core Power (SERDES_x_VDD)

Even though SERDES0 and SERDES1 cores share the same power supply, separate planes must be made while connecting to corresponding SerDes blocks, as shown in the following figure. This reduces the noise coupling between SERDES0 and SERDES1 blocks.


Figure 30 • Layout for SERDES_x_VDD Plane

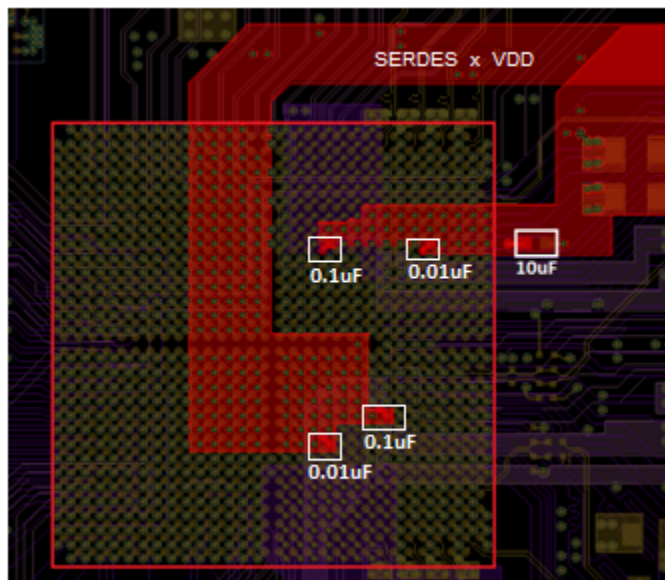

3.3.2.2 SerDes I/O Power (SERDES_x_VDDAIO)

- Even though SERDES0 and SERDES1 I/Os share the same power supply, make separate planes while connecting to the corresponding pins, as shown in the following figure. Each plane is separated as SERDES_0_L01_VDDAIO, SERDES_0_L23_VDDAIO, SERDES_1_L01_VDDAIO, and SERDES_1_L01_VDDAIO, as shown in the following figure. This reduces the noise coupling between the differential lanes.


Figure 31 • Layout of SERDES_x_VDDAIO Plane

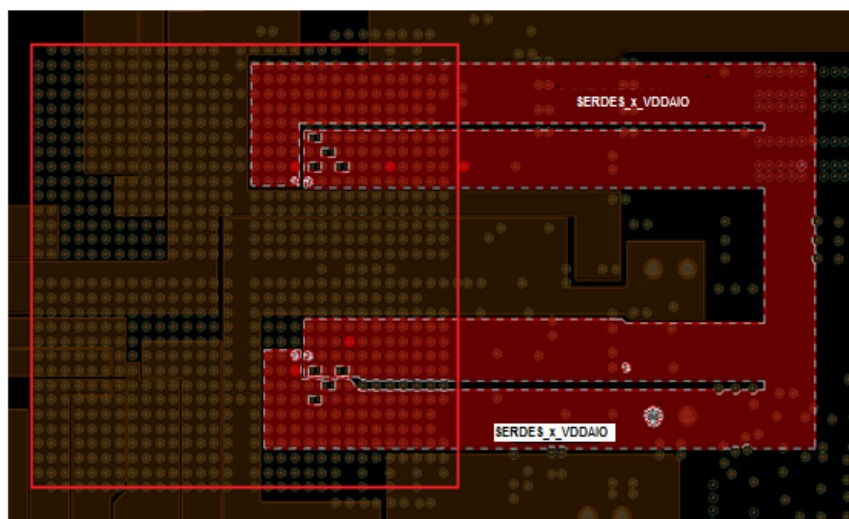

3.3.2.3 SerDes PLL

- Plane routing for SERDES_1_L01_VDDAPLL and SERDES_1_L01_REFRET is shown in the following figure.
- SERDES_1_L01_VDDAPLL and SERDES_1_L01_REFRET should not be routed as traces. A small trace width causes poor noise performance due to the high inductive behavior of the trace. Even though the current requirement is low, these supply traces should be routed as small planes, as shown in the following figure.
- The connections of 1.2 k Ω resistor and SERDES_1_L01_REXT of SmartFusion2/IGLOO2 should not be routed as a thick plane. It must be routed as a signal trace in-order to meet minimum capacitance requirement of the SERDES_1_L01_REXT pin. The length of the trace should be as short as possible. The following figure shows the sample layout.
- Same layout guidelines should be followed for the remaining SerDes PLL power supplies.

Figure 32 • Layout of SERDES_1_L01_VDDAPLL and SERDES_1_L01_REFRET

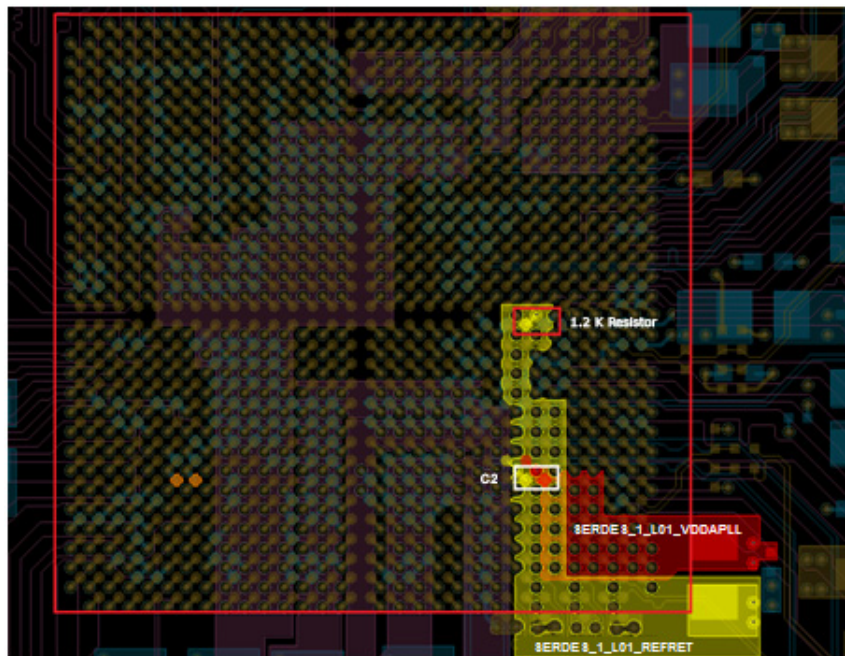


3.3.3 Simulations

3.3.3.1 SerDes Core Power (SERDES_x_VDD)

The target impedance of the SERDES_x_VDD pin is calculated as 300 m Ω , based on the following values (see [Power Supply](#), page 38):

- $V_{SUPPLY} = 1.2 \text{ V}$
- $I_{trans} = 200 \text{ mA}$
- Ripple = 5%

[Figure 33](#), page 45 shows the impedance of the plane (SERDES_x_VDD) improved by the decoupling capacitors. The impedance of the plane is kept under 0.2 Ω till 100 MHz.

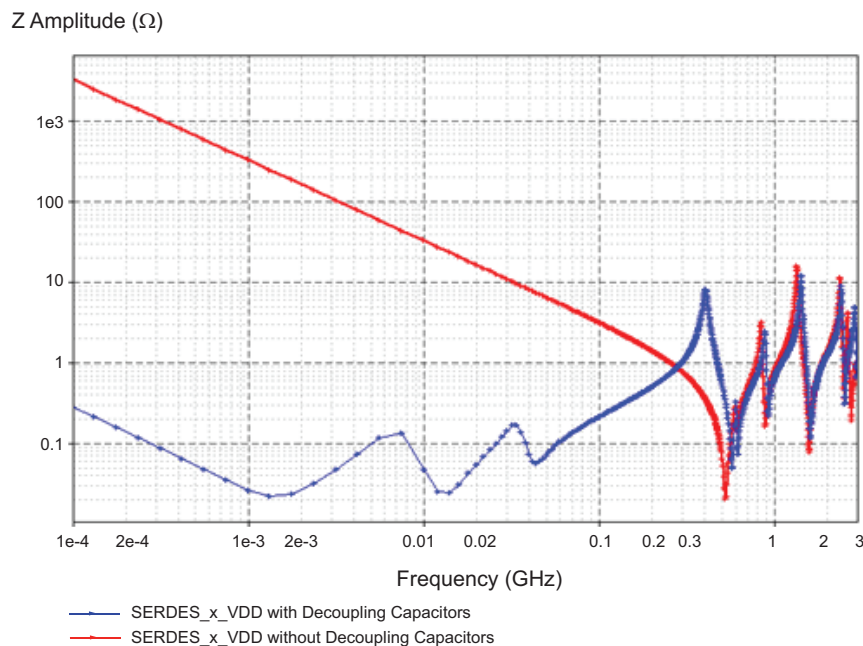
Figure 33 • Impedance Profile of SERDES_x_VDD Plane Over Frequency Range

3.3.3.2 SerDes I/O Power (SERDES_x_VDDAIO)

The target impedance of the SERDES_x_VDDAIO pin is calculated as 240 m Ω , based on the following values (see [Power Supply](#), page 38):

- $V_{\text{SUPPLY}} = 1.2\text{V}$
- $I_{\text{trans}} = 250\text{mA}$
- Ripple = 5%

The following figure shows the impedance of the plane (SERDES_x_VDDAIO) improved by the decoupling capacitors. The impedance of the plane is kept under 0.2 Ω till 100 MHz.

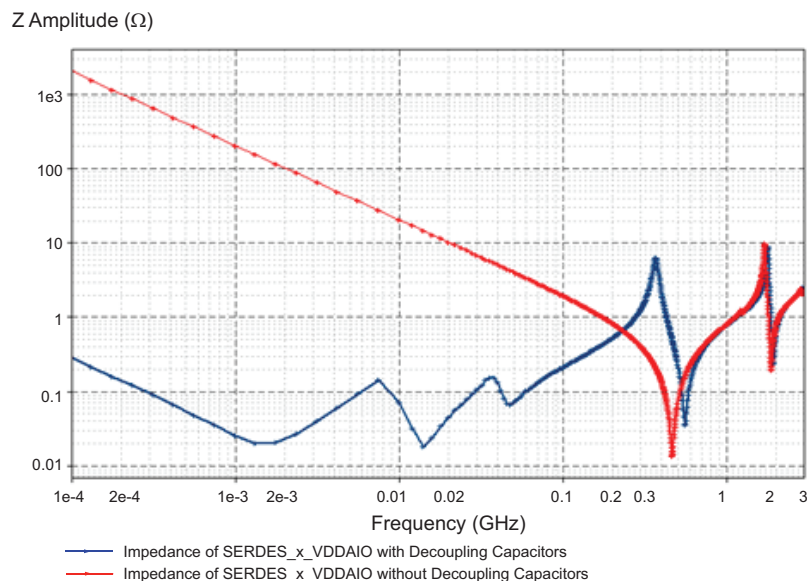Figure 34 • Impedance Profile of SERDES_x_VDDAIO Plane Over Frequency Range

3.4 DDR

Some of the variants support the fabric DDR (FDDR) and microcontroller subsystem DDR (MDDR) and some variants support only FDDR in SmartFusion2. Refer datasheet to see on which bank DDR is supported on each particular device. The layout guidelines of the respective VDDIO should be followed. Apart from that, it requires VREF voltage for an internal reference. Noise on VREF impacts the read performance of SmartFusion2/IGLOO2 devices. VREF lines should not be routed near the aggressive nets or switching power supplies. For more information about DDR memory layout guidelines, see the [Micron DDR3 Memory Layout Guidelines](#). The VDDIO guidelines should be followed for DDR bank VDDIO. This section explains the guidelines to be used for VREF.

3.4.1 Component Placement

3.4.1.1 VREF

- The bypass capacitor (10 μ F) should be placed near, or at the edge of the device if possible.
- All decoupling capacitors (0.1 μ F and 0.01 μ F) should be 0402 or of a smaller package size as they are required to be mounted on the reverse side of the board. They should be fit between the adjacent vias of the BGA package pins. These decoupling capacitors are selected to have a low impedance over the operating frequency and temperature range.
- The capacitor pad to via trace should be as small as possible. [Figure 24](#), page 39 shows how these capacitors are mounted. Microsemi recommends keeping the capacitor pad directly on the corresponding vias.

3.4.1.2 VDDIO

- The bypass capacitors (47 μ F and 22 μ F) should be placed near, or at the edge of the device if possible.
- All decoupling capacitors (0.1 μ F and 0.01 μ F) should be 0402 or of a smaller package size as they are required to be mounted on the reverse side of the board. They should be fit between the adjacent vias of the BGA package pins. These decoupling capacitors are selected to have a low impedance over the operating frequency and temperature range.
- The capacitor pad to via trace should be as small as possible. [Figure 24](#), page 39 shows how these capacitors are mounted. The capacitors can also be mounted directly on the pad available on the vias.


3.4.2 Plane Layout

3.4.2.1 VREF

Noise on VREF impacts the read performance of SmartFusion2/IGLOO2 devices. The VREF lines should be routed with no aggressive net or switching power supply nearby. Even the current is low, VREF should not be routed as trace as it is very susceptible to noise.

The following figure shows the VREF5 used for MDDR.

Figure 35 • Layout of VREF5

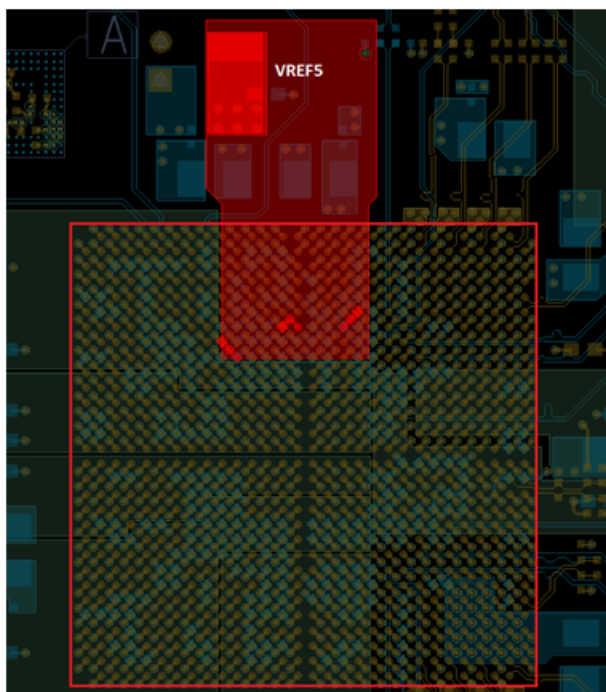

3.4.2.2 VDDIO

The shape of the plane does not have a specific requirement. The width of the plane should be sufficient to carry the required current. The following figures show the sample layout for VDDIO0 and VDDIO5 planes.

Figure 36 • Layout of VDDIO0 Plane

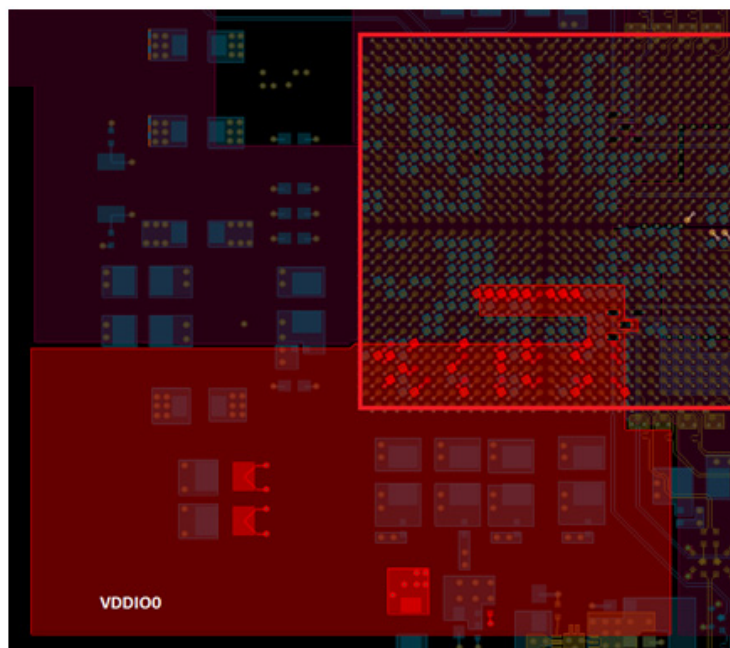
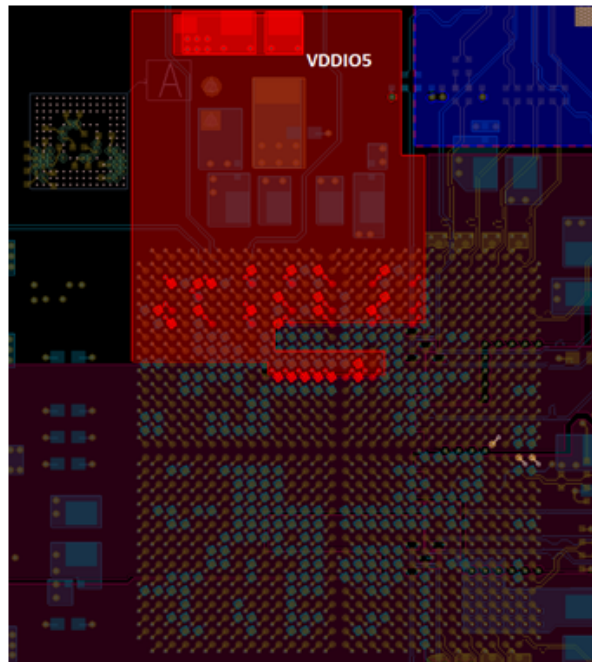




Figure 37 • Layout of VDDIO5 Plane

3.4.3 Simulations

The target impedance of the DDR VDDIO is calculated as 240 m Ω , based on the values (see [Power Supply](#), page 38):

- $V_{\text{SUPPLY}} = 1.5\text{V}$,
- $I_{\text{trans}} = 250\text{ mA}$
- Ripple = 5%

The impedance profile of the DDR VDDIO plane over frequency range is shown in the following figures. The impedance improves with the decoupling capacitors provided. The target impedance of 0.3 Ω has been achieved till 500 MHz.

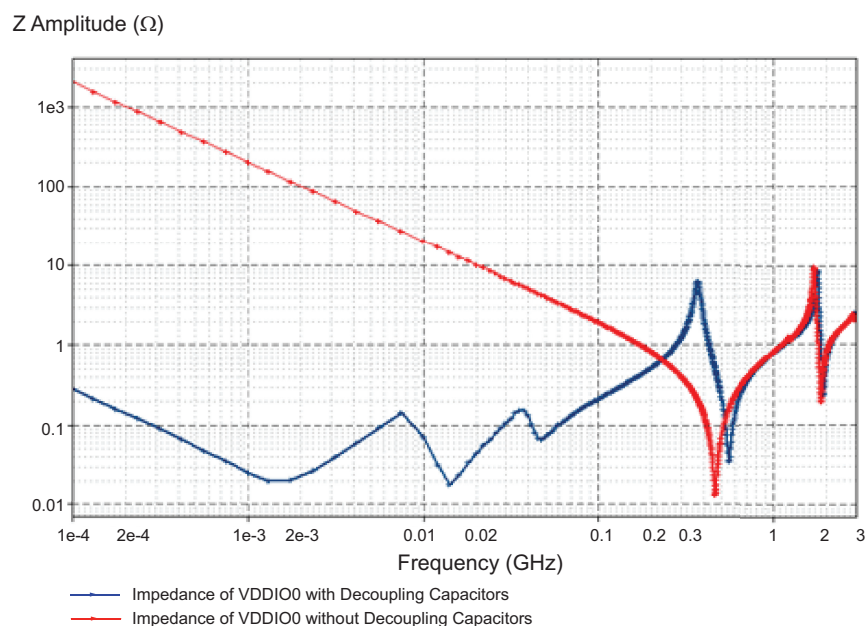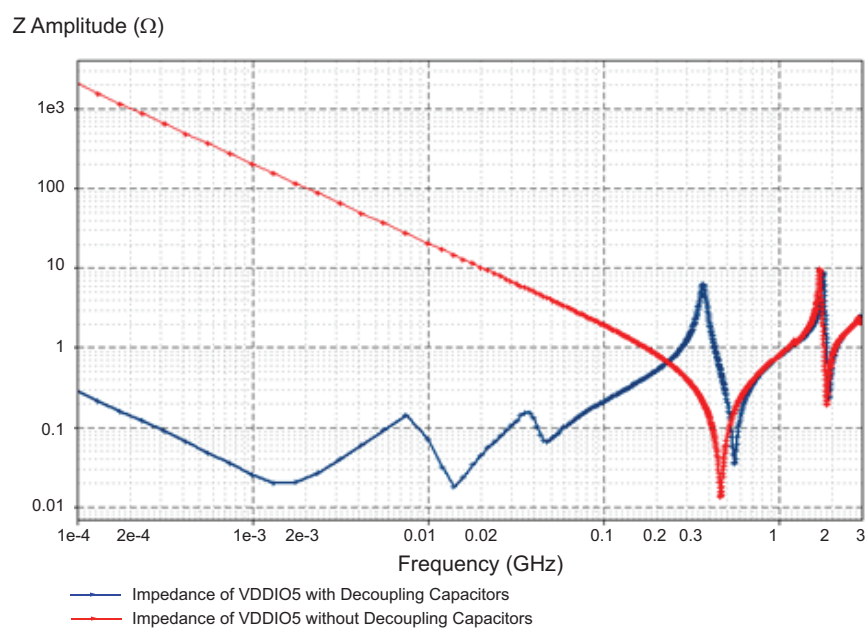
Figure 38 • Impedance Profile of VDDIO0 Plane Over Frequency Range**Figure 39 • Impedance Profile of VDDIO5 Plane Over Frequency Range**

3.5 PLL

To achieve a reasonable level of long term jitter, it is vital to deliver an analog grade power supply to the PLL. An R-C or R-L-C filter is used with the C being composed of multiple devices to achieve a wide spectrum of noise absorption. Even the circuit is simple, there are specific board layout requirements. Board layout around the high-frequency capacitor and the path to the pads are critical. It is vital that the quiet ground and power are treated like analog signals. The entire VDDPLL and PLLVSSA wiring path must not be coupled with any signal aggressors – especially, any high-swing and high-slew rate signals such as TTL, CMOS, or SSTL signals used in DDR buses, and so on.

The recommended circuit for the power supply filter is shown in the following figure.

Figure 40 • Filter Circuit for PLL

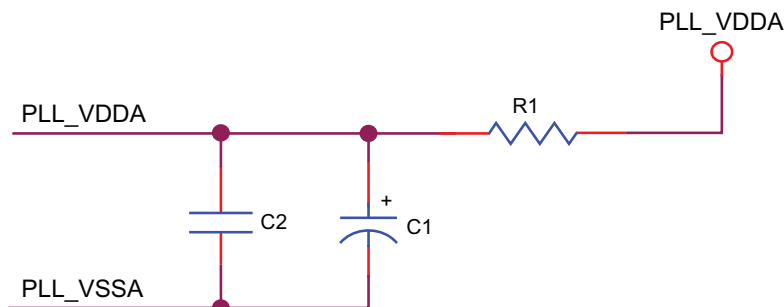


For more information about R1, C1, and C2, see [Board Design Guidelines for SmartFusion2 SoC and IGLOO2 FPGAs](#), page 4.

3.5.1 Component Placement

- The capacitor (C1) and series resistor (R1) should be placed near the device as close as possible to C2 device. A sample placement is shown in the following figure.
- The decoupling capacitor (C2) should be placed near the BGA via. The capacitor pad to via trace should be as small as possible. For more information about R1, C1, and C2, see [Board Design Guidelines for SmartFusion2 SoC and IGLOO2 FPGAs](#), page 4.


Figure 41 • Placement of Capacitors for PLL filter Circuit

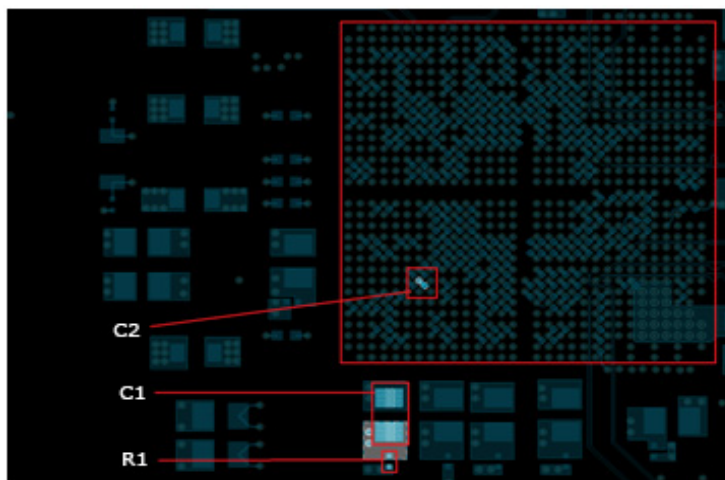

3.5.2 Plane Layout

- Plane routing for PLL0VDDA and PLL0VSSA is shown in the following figure. These are with respect to the schematic, as shown in [Figure 40](#), page 50.
- The capacitor (22 μ F) and series resistor should be placed near the device as close as possible to the 0.1 μ F cap. A sample placement is shown in the following figure.

Figure 42 • Routing for PLL Filter Circuit

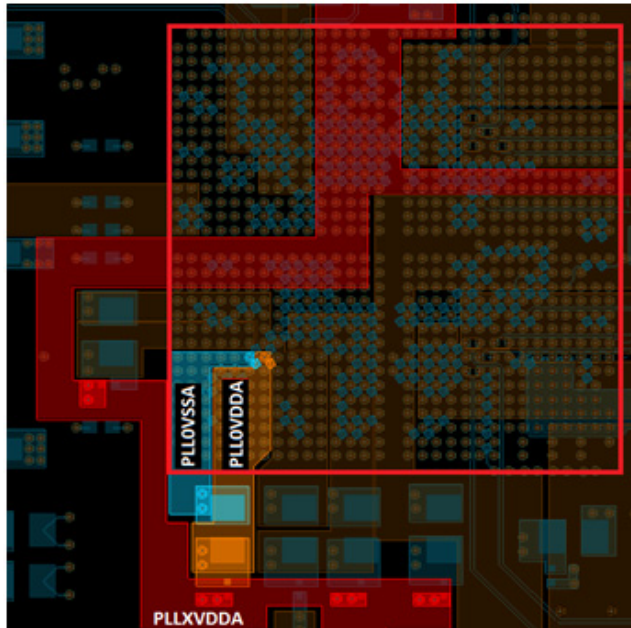


- PLL0VDDA and PLL0VSSA should not be routed with a small trace width as it increases the inductance resulting in ripples. These supply traces should be routed as plane (as shown in [Figure 42](#), page 51), even though the current requirements are small.
- Same layout guidelines should be followed for DDR PLL power supplies. For more information about PCIe PLL guidelines, see [SerDes](#), page 41.

3.5.3 Simulations

The target impedance of the PLL0VDDA plane is calculated as 16.5 Ω based on the values (see [Power Supply](#), page 38):

- $V_{\text{SUPPLY}} = 3.3 \text{ V}$
- $3.3 \text{ V}, I_{\text{trans}} = 10 \text{ mA}$
- Ripple = 5%

The impedance of the plane (Z) should be 16.5 Ω or less. For more information about ripples and its values, see [DS0128: IGLOO2 and SmartFusion2 Datasheet](#). Plane impedance with and without filter circuit is shown in [Figure 43](#), page 52.

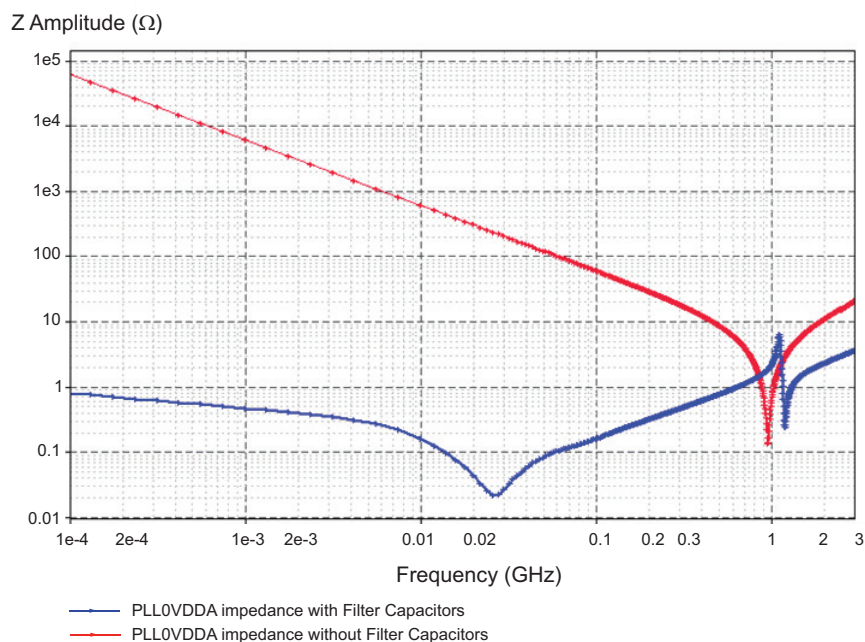Figure 43 • PLL0VDDA Plane Impedance

3.6 I/O Power Supply

3.6.1 Component Placement

- The bypass capacitors (47 μ F and 22 μ F) should be placed near, or if possible, at the edge of the device.
- All decoupling capacitors (0.1 μ F and 0.01 μ F) should be 0402 or of a smaller package size as they are required to be mounted under BGA package. They should be fit between the adjacent vias of BGA package pins. These decoupling capacitors are selected to have a low impedance over operating frequency and temperature range.

The capacitor pad to via trace should be as small as possible. [Figure 24](#), page 39 shows how these capacitors are mounted. The capacitors can also be mounted directly on the pad available on the vias. The decoupling capacitors should not be shared via connections.

3.6.2 Plane Layout

The shape of the plane does not have a specific requirement. The width of the plane should be sufficient enough to carry the required current.

3.6.3 Simulations

The target impedance of the VDDIO1 plane is calculated as 330 mΩ based on the following values (see [Power Supply](#), page 38):

- $V_{\text{SUPPLY}} = 3.3 \text{ V}$,
- $I_{\text{trans}} = 500 \text{ mA}$
- Ripple = 5%

The following figures show the impedance of the planes (VDDIO1 and VDDIO2). The impedance of the plane has been improved by decoupling capacitors and is kept under 0.2 Ω till 100 MHz.

Figure 44 • Impedance Profile of VDDIO1 Plane Over Frequency Range


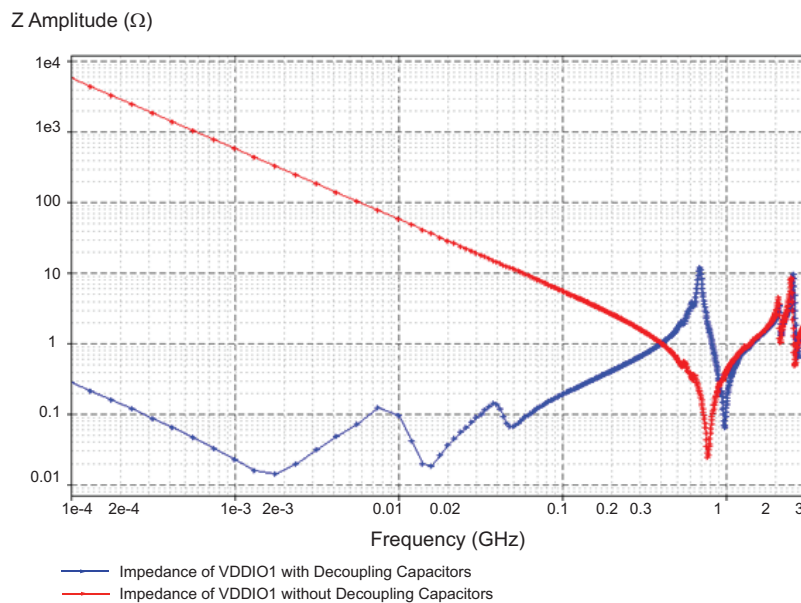


Figure 45 • Impedance Profile of VDDIO2 Plane Over Frequency Range

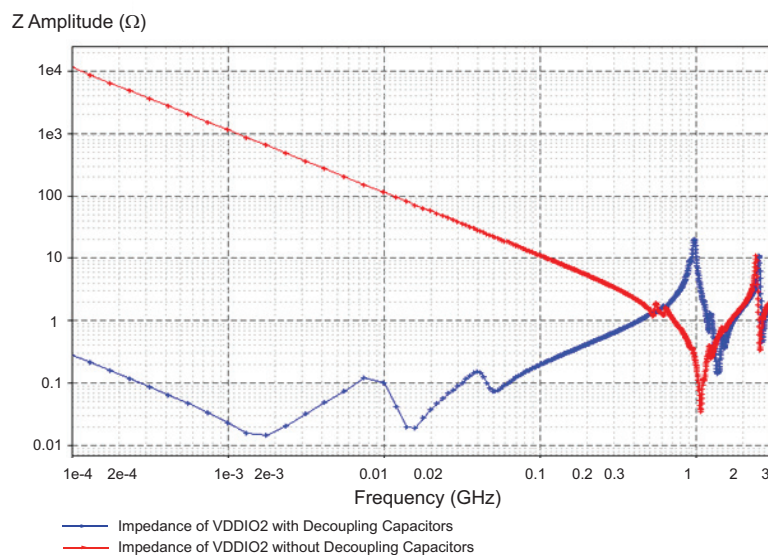

3.7 Programming Power Supply (VPP or VCCENVM)

VPP is used as an input for the internal charge pump that generates the required voltage to program flash. VCCENVM is an embedded non-volatile memory (eNVM) supply.

3.7.1 Component Placement

- The bypass capacitors (47 μ F and 22 μ F) should be placed near, or at the edge of the device if possible.
- All decoupling capacitors (0.1 μ F and 0.01 μ F) should be 0402 or of a smaller package size as they are required to be mounted on the reverse side of the board. They should be fit between the adjacent vias of BGA package pins. These decoupling capacitors are carefully selected to have low impedance over the operating frequency and temperature range.
- The capacitor pad to via trace should be as small as possible. [Figure 24](#), page 39 shows how these capacitors are mounted. The capacitor can also be mounted directly on the pad available on the vias.

3.7.2 Plane Layout

The shape of the plane does not have a specific requirement. The width of the plane should be sufficient enough to carry the required current.


3.7.3 Simulations

The target impedance of the VPP is calculated as 3.3 Ω , based on the values (see [Power Supply](#), page 38):

- $V_{SUPPLY} = 3.3$ V
- $I_{trans} = 50$ mA
- Ripple = 5%

The simulation result (as shown in the following figure) shows that it meets the required impedance levels.

Figure 46 • Impedance Profile of VPP Plane Over Frequency Range

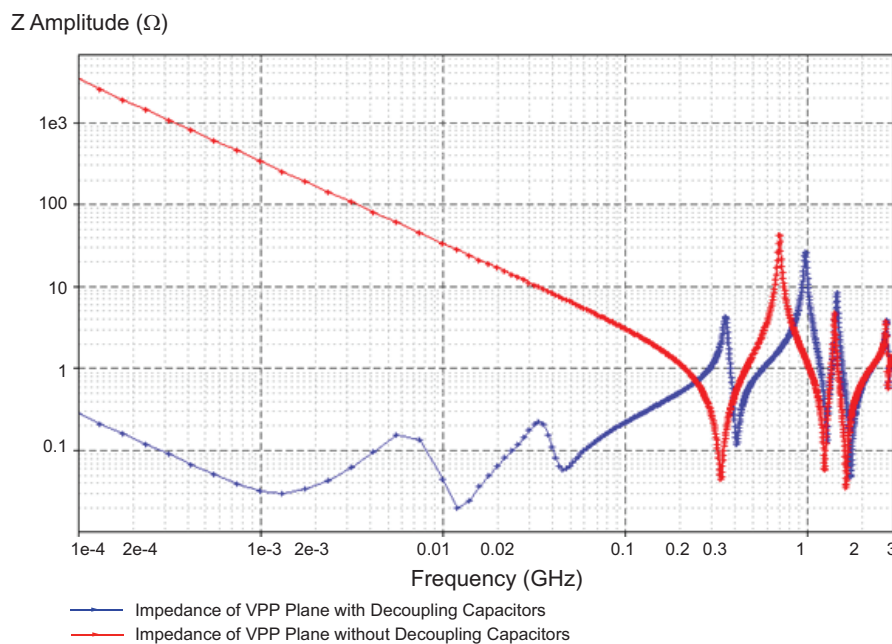

3.8 High-Speed Serial Link (SerDes)

3.8.1 Layout Considerations

3.8.1.1 Differential Traces


A well designed differential trace not must have the following qualities:

- Mismatch in impedance
- Insertion loss and return loss
- Skew within the differential traces

The following points need to be considered while routing the high-speed differential traces to meet the above qualities.


- The traces should be routed with tight length matching (skew) within the differential traces. Asymmetry in length causes conversion of differential signals in Common mode signals. The differential pair should be routed such that the skew within differential pairs is less than 5 mils. The length match should be used by matching techniques, as shown in the following figure.

Figure 47 • Skew Matching

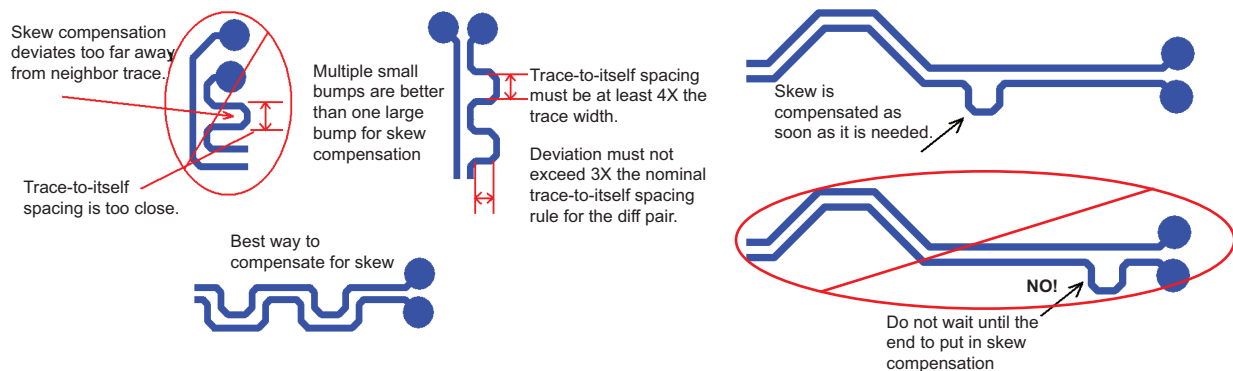

- The length of differential lanes should be matched within the TX and RX group. This is applicable only to specific protocols like XAUI and so on.
- Route differential pairs symmetrically into and out of structures, as shown in the following figure.


Figure 48 • Example of Asymmetric and Symmetric Differential Pairs Structure

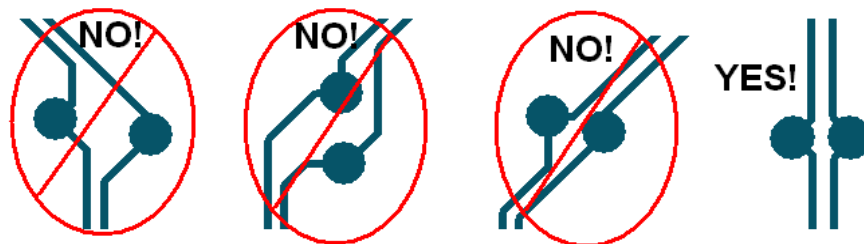

- Skin effect dominates as the speed increases. To reduce the skin effect, width of the trace has to be increased (loosely coupled differential traces). Increase in trace width causes increase in dielectric losses. To reduce the dielectric loss, use low Dissipation Factor (Df) PCB materials like Nelco 4000-13. This is approximately double the cost of FR4 PCB material, but can provide increased eye-opening performance when longer trace interconnections are required. Remember to maintain 100 Ω differential impedance. Need to consider this if the data rate is 5 Gbps and above.
- Far end cross talk is eliminated by using stripline routing. However, routing in stripline causes more dielectric loss and more variation in the impedance. Cross talk affects only when there is a high density routing. It is better to route as microstrip, if there is enough space between differential pairs (> 4 times the width of the conductor) to reduce dielectric loss. Simulations are recommended to see the best possible routing.


- 2116 or 2113 glass weaving PCB materials should be used to avoid the variations in the impedances. Zig-zag routing must be used instead of straight line routing to avoid glass weaving effect on impedance variations, as shown in the following figure. Instruct the fabrication vendor to use these PCB materials before manufacturing.

Figure 49 • Zig-Zag Routing

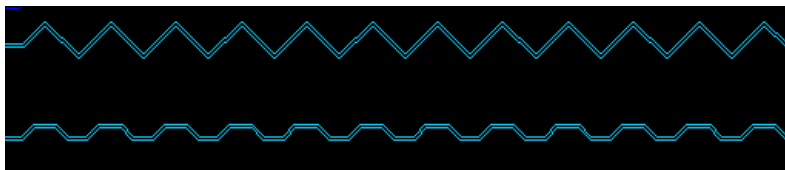


- These traces should be kept away from the aggressive nets or clock traces. For example, on M2S050T devices, the SerDes and DDR traces should not be adjacent to each other.
- Separation between the coupled differential trace pairs should be 1x. Spacing between channels should be > 3x separation. Trace stubs should be avoided. The stub length should not exceed 40 mils for 5 Gbps data rate.
- The trace lengths should be kept as small as possible.
- It is better to use low roughness, that is, smooth copper. As the speed increases insertion loss due to the copper, then roughness increases. The attenuation due to skin effect is increased proportional to the square root of frequency. The roughness causes this loss proportional to frequency. Microsemi recommends instructing the PCB fabrication house to use smooth copper, if the frequency exceeds 2 Gbps.
- Split reference planes should be avoided. Ground planes must be used for reference for all the SerDes lanes.

Figure 50 • Ground Planes for Reference

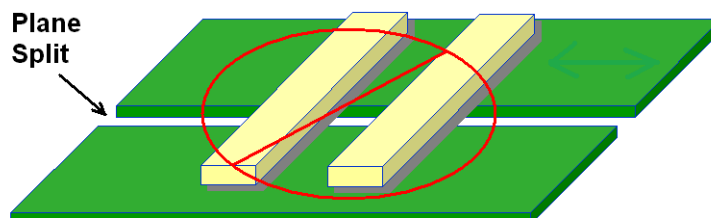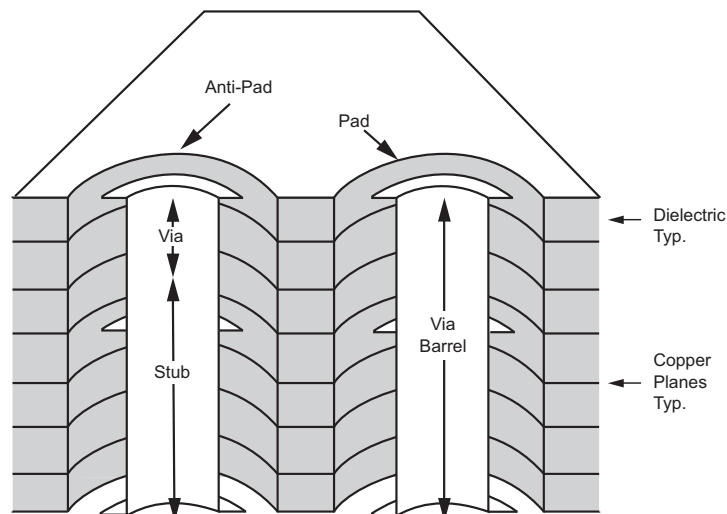


3.8.2 Via

- The target impedance of vias are designed by adjusting the pad clearance (anti-pad size). Field solver should be used to optimize the via according to the stack-up.


Figure 51 • Via Illustration¹

- Number of vias on different traces should be avoided or minimized. SerDes signals should be routed completely on a single layer with the exception of via transitions from component layer to the routing layer (3-via maximum).
- The length of via stub should be minimized by back drilling the vias, or by routing the signals from near top to near bottom layer, or else blind or buried vias can be used. Using blind-vias or back drilling is a good method to eliminate via stubs and reduce reflections.
- The stub length should be kept below 100 mils, if the data rate is 2.5 Gbps and 40 mils for 5 Gbps.
- If feasible, non-functional pads should be removed. Non-functional pads on via are the pads where no trace is connected. This reduces the via capacitance and stub effect of pads.

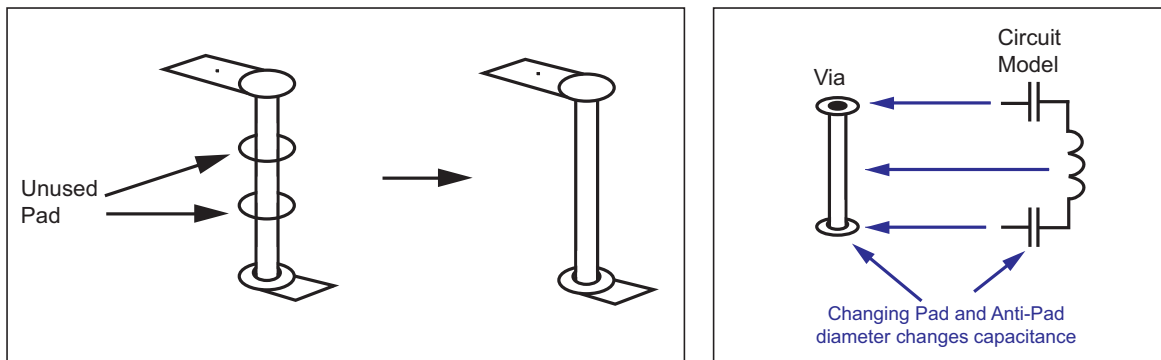
Figure 52 • Non-Functional Pads of Via

- The tight via to via pitch is practical to reduce the cross talk effect, as shown in the following figure.

1. Simonovich, E. Bogatin, Y. Cao, Method of Modeling Differential Vias, White Paper, Jan 2011

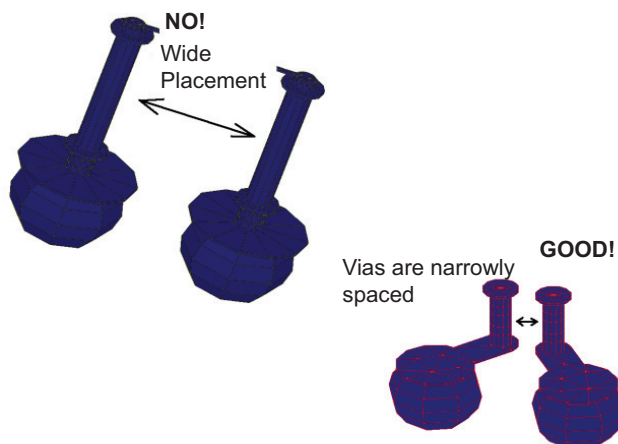
Figure 53 • Via-to-Via Pitch

- Symmetrical ground vias (return vias) should be used to reduce discontinuity for Common mode signal component, as shown in the following figure. Common mode of part of the signal requires continuous return path RX to TX and GND. Return vias help in maintaining the continuity.

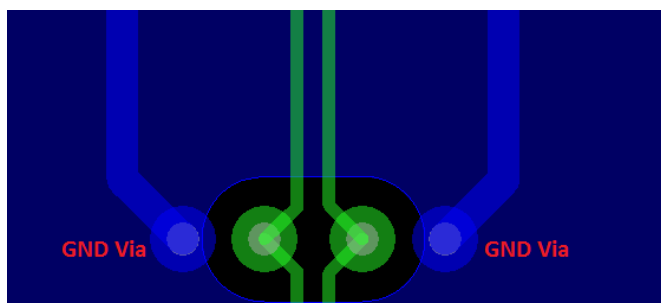Figure 54 • GND Via or Return Via

3.8.3 DC Blocking Capacitors

The plane underneath the pads of DC blocking capacitors should be removed (as shown in the following figure) to match the impedance of the pad to 50 Ω . This has to be done only on immediate reference plane, not on all planes.

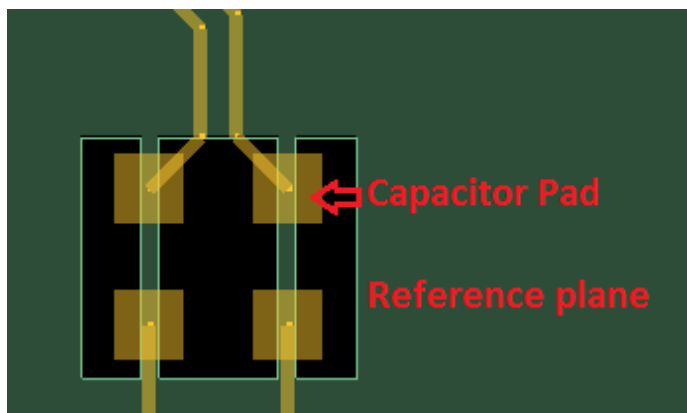Figure 55 • Capacitor Pad Reference Plane

3.8.4 Connectors

The plane keep-out clearance should be optimized from the pin to get 50 Ω impedance when through hole SMAs or connectors are used. This reduces the reflection loss.

3.9 Considerations for Simulation

Microsemi recommends simulations to confirm the quality of the received signal. The following files are required to simulate the serial channel:

- IBIS: AMI files for SmartFusion2/IGLOO2 and any other devices that are connected to SerDes
- Package: files (optional). S-parameter of package improves the accuracy instead of using package parameters in the IBIS file
- Board traces model file including via models
- Connector models, if required

The following steps describe how to run the serial channel simulations:

3.9.1 Step 1: Gathering the Required Files

3.9.1.1 IBIS-AMI Models

The IBIS-AMI models of SmartFusion2/IGLOO2 and the IBIS-AMI models of IC that will be interfaced with SmartFusion2/IGLOO2 can be downloaded from the Microsemi website:

- www.microsemi.com/soc/download/ibis/SmartFusion2.aspx
- www.microsemi.com/soc/download/ibis/IGLOO2.aspx

3.9.1.2 Package Models

The package models (S-parameter models) of SmartFusion2/IGLOO2 can be downloaded from the Microsemi website:

- www.microsemi.com/soc/download/ibis/SmartFusion2.aspx
- www.microsemi.com/soc/download/ibis/IGLOO2.aspx

Accuracy of simulation improves with S-parameter model of package file instead of using package models available in the IBIS file. If S-parameter models for package are used, the package details in IBIS should be commented.

3.9.1.3 PCB Trace Models

The PCB file should be converted into a compatible format of simulator software. For example, the .HYP file format of PCB is required to be simulated in Hyperlynx, and .SPD file format of PCB is required to be simulated in Sigrity. Once the PCB file is loaded in the simulation tool, the stack-up that matches the PCB stack-up should be checked. The dielectric constant, Dk and dissipation factor, and Df of PCB material should be defined. The tool extracts incorrect models, if the above points are not defined properly.

The SerDes traces should be identified and ports on both the sides of the traces need to be assigned. The S-parameter models of traces should be extracted. The following tools can be used to extract S-parameter models of PCB traces:

- Agilent's ADS
- Mentors Hyperlynx
- Sigrity's PowerSI

It is not mandatory to use the above mentioned tools, many other tools are available in the market which can extract S-parameter models.

3.9.2 Step 2: Creating Simulation Topology

The typical topology, as shown in the following figure, shows the blocks involved in the serial link analysis. These blocks are taken from the Sigrity tool. All simulations related to SerDes are done on Sigrity's SystemSI tool in this document. Topology is same in any tool. This can be done in any tool that supports the serial link analysis.


The typical topology for SLA simulation is done as following:

- AMI: AMI models of TX and RX
- TX_PRIMARY: IBIS model of TX I/O
- Pkg1 and Pkg2: Package model of TX and RX I/O

- PCB: S-parameter model of SmartFusion2 Development Kit SerDes Traces
- RX_PRIMARY: S-parameter model of either the connector or the IBIS model of the receiver IC device

Once all the model files are imported into the topology, the default configuration in the AMI model should be left to calculate the appropriate coefficients by the tool and then to run the simulations.

Figure 56 • Typical Topology for SLA Simulation

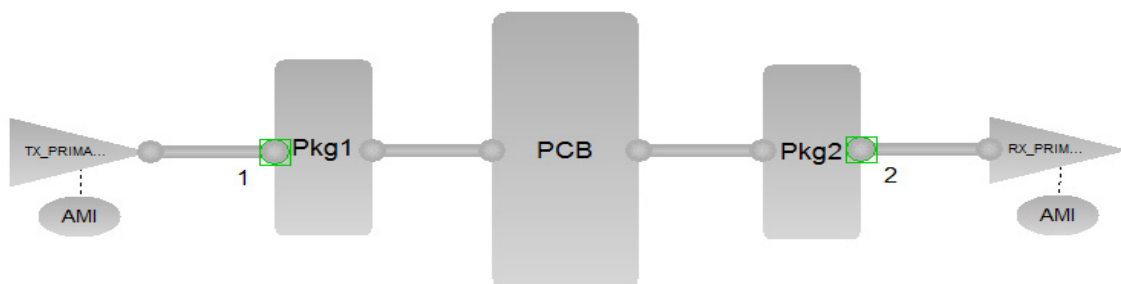


3.9.3 Step 3: Configuration of AMI Model

The following configurations on the AMI model are required before simulating the serial channel:

3.9.3.1 TX AMI Model

The following figure shows the block diagram of the 3-tap Feed Forward equalizer structure for TX. The output of the TX is given by the transfer function $t_{n-1} + t_n Z^{-1} + t_{n+1} Z^{-2}$. The TX output depends on the value of tap coefficients.

Figure 57 • Block Diagram of the 3-tap Feed Forward Equalizer

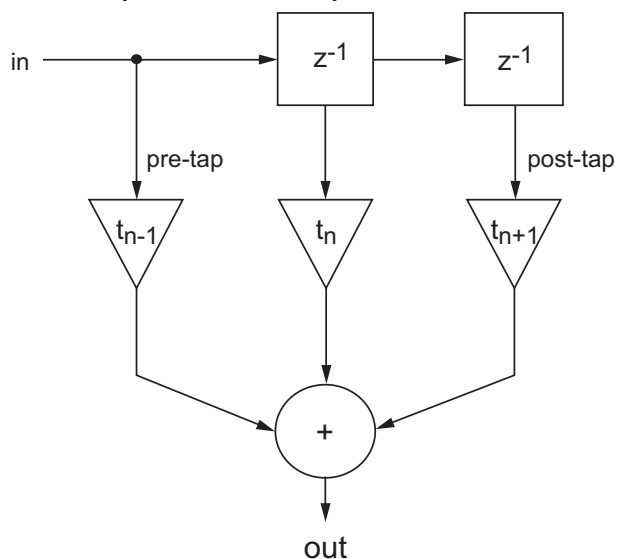

The following are the details of coefficients:

- **t0**: Pre-cursor tap setting. The range is from -0.4 to -0.01, default value is -0.01.
- **t1**: Main tap. The range is from 0.1 to 1, default value is 1.


- **t2:** Post-cursor tap. The range is from -0.5 to -0.01, default value is -0.01.
- **TapsFromFile:** Explicit feed forward equalizer (FFE) coefficients can be set through this file. If a file is used, it overrides the manual tap settings and automatic generation.
- **TapsToFile:** Output FFE tap coefficients to this file when automatic generation coefficients is used.

3.9.3.2 RX AMI Model

SerDes supports the programmable single pole continuous time linear equalization (CTLE) at the receiver. The linear equalization comprises of amplifying higher frequency components that have been more severely attenuated by the Interconnect, or attenuating the lower frequency components to a greater degree than the higher frequency components.

The low-frequency attenuation level and the low-frequency flat-band bandwidth are programmable, as shown in the following figure.

Figure 58 • Continuous Time Linear Equalization Response

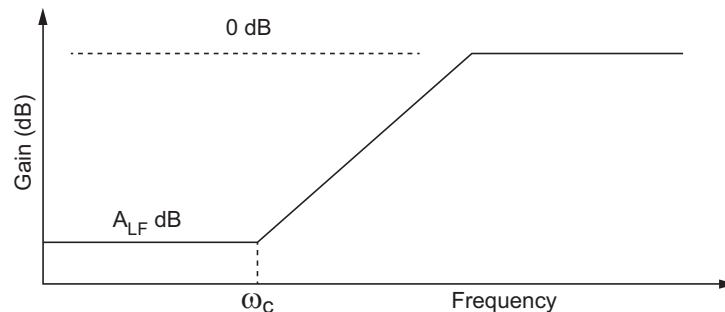

Both A_{LF} and ω_c (f_0) can be set to maximize the signal quality of the receiver for achieving the highest possible bit error rate (BER).

- A_{LF} : Low-frequency dB loss of the filter. The range is from 0 to 50, default value is 6.
- f_0 : High pass cut-off frequency. The range is from $1e^6$ to $5e^{10}$, default value is $1e^9$.

3.9.4 Step 4: Results


Qualification of simulation results is done based on the eye-height, eye-width, and BER curves. Check the eye-height and eye-width at target BER of $10e^{-12}$. These results are found in the report generated by the simulation tool. For example, the Sigrity tool gives the following information at RX:

At BER of $10e^{-12}$, running at 5 Gbps bit rate

- The eye-width is 0.68 UI (Unit Interval)
- The eye-height is 213 mV

This simulation is on the SmartFusion2 Development Kit using the Sigrit tool and the waveforms are shown in the following figure. The simulation result shows that it meets the PCIe 2.0 requirements.

Figure 59 • Expected Results from Simulations (Eye Diagram, Eye Contour, and Bath Tub Curve)

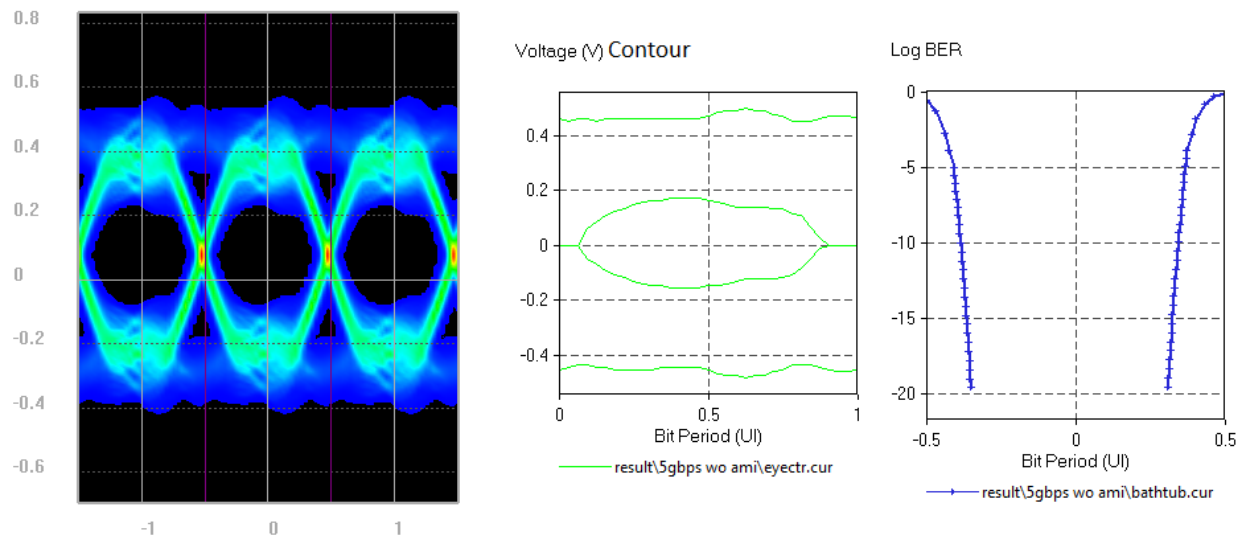

The following table lists the specifications of the received signal for PCIe.


Table 21 • Specifications of the Received Signal for PCIe

Bit Rate	Min Height of the Eye at RX	Min Width of the Eye at RX
2.5 Gbps	175 mV	0.6 UI
5 Gbps	120 mV	0.6 UI

For more information about PCIe 2.0 base specification, see www.pcisig.com/members/downloads/specifications/pciexpress/PCI_Express_Base_r2_1_04Mar09.pdf

To know whether or not the system is meeting the requirements, the eye mask can be imported. Specifications of eye mask depend on the application the system is using. For example, PCIe 1.0, PCIe 2.0, XAUI, and SGMII. A typical eye mask for PCIe 2.0 is shown in the following figure.

Figure 60 • Eye Mask for PCIe 2.0

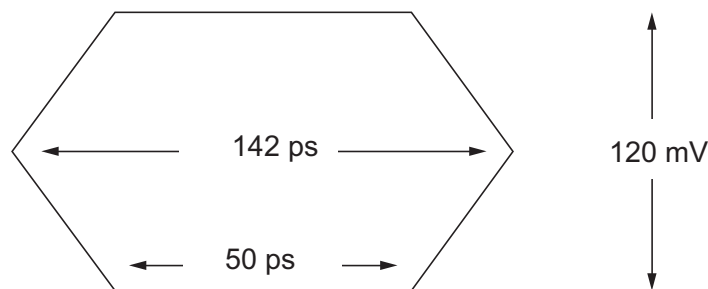

For more information about IBIS-AMI model, see [AC292- IBIS Models- Background and Usage Application Note](#).


3.10 DDR3 Layout Guidelines

3.10.1 Placement

It is required to ensure that the placement for the DDR3 memories looks like *L* (shape), where, memories are at the bottom of the *L* and controllers are on the top of the *L*. This gives enough space to route the DQ signals with less number of layers. This is not mandatory to follow the suggested placement.

However, the placement also depends on the board constraints. The maximum trace length of any signal in the placement should not be more than 7 inches.

Figure 61 • DDR3 Memories

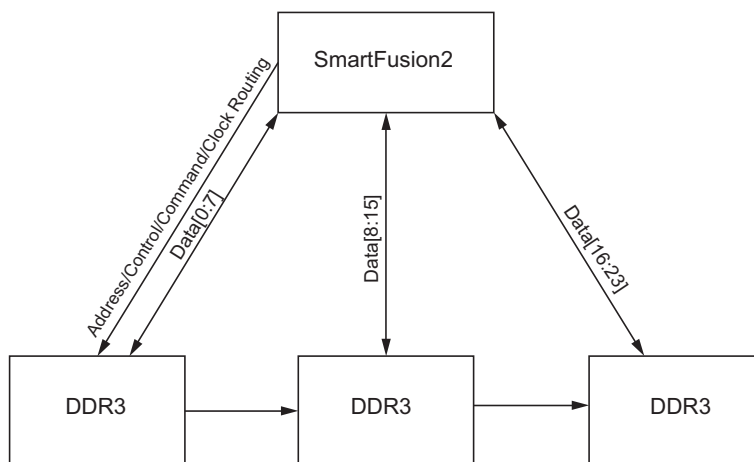

The termination resistors are not required for the DQ and DQS signals as these signals have on chip ODTs. The termination resistors are placed at the end of the address, command, control, and clock signals as these signals use fly-by topology. VTT plane/island is thick enough to handle the current required by termination resistors; at least 150 mil trace is required. The sense pin of VTT regulator should be connected at the center of the VTT island.

3.10.2 Routing

Reliability of DDR interface depends on the quality of the layout. There are many layout guidelines available from memory vendors. The following recommendations can also be used for routing the DDR3 signals. The following DDR3 signals are grouped:

- Data
- Address/Command
- Control
- Clocks
- Power

The following table lists the signals that come under a particular group:

Table 22 • Grouping of DDR3 Signals

Group	Signals
Data	DQ[0:7], DQ[8:15], DQ[16:23], DQ[24:31] and DQS[0:3], DM[0:3]
Address/Command	A[0:15], BA[0:2], RAS#, CAS#, and WE#
Control	CS#, CKE, and ODT
Clock	CK and CK#

3.10.2.1 Data Group Signal Routing

- The data signals should not be over the split planes.
- The reference plane for data signals should be GND plane and should be contiguous between memory and SmartFusion2/IGLOO2.
- Traces should not be routed at the edge of the reference plane and over via anti pads.
- When routing the data signals, the longest signals should be routed first, this allows to adjust the length for the short length signals, when routing data signals.
- Serpentine routing should be used to adjust the data group signals to meet this requirement.
- The DQS signal should be routed along with associated data byte lane on the same critical layer with the same via count. Using more than three vias in the connection between the FPGA controller and memory device should be avoided.
- The impedance for the data traces depends on the stack-up and the trace width. There are options to select the impedance based on the stack-up and trace width.
 - 40 Ω impedance, which requires wide traces (~7 to 8 mils). This gives the less cross talk and less spacing between the traces (~2x). Spacing between non-DDR signals and DDR signals should be ~4x.
 - 50 Ω impedance, which requires smaller trace width (~4 to 6mils). This requires more spacing between the traces (~3x). Spacing between non DDR signals and DDR signals should be ~4x.
- All data lanes should be matched to within 0.5 inch.
- Within the data lane, each trace should be matched to within ± 10 mils of its respective data strobe
- The DQS and DQS# need to be matched within +/- 5mils.
- Differential impedance should be between 75 to 100 Ω .
- Differential traces adjacent to noisy signals or clock chips should be avoided.
- Spacing between differential lines should be 5 to 8 mils.

3.10.2.2 Address, Control, Command, and Clock Routing

- These signals should be routed in the fly-by topology and terminated with appropriate termination resistor at the end of the signals. The resistor termination should not have a stub longer than 600 mil.
- The impedance for the trace depends on the stack-up and trace width. There are options to select the impedance based on the stack-up and trace width:
 - 40 Ω impedance, which requires wide traces (~7 to 8 mils). This gives the less cross talk and less spacing between the traces (~2x). Spacing between non DDR signals and DDR signals should be ~4x.
 - 50 Ω impedance, which requires smaller trace width (~4 to 6mils). This requires more spacing between the traces (~3x). Spacing between non DDR signals and DDR signals should be ~4w to avoid crosstalk issues.
 - Address and control signals can be referenced to a power plane if a ground plane is not available. The power plane should be related to the memory interface. However, a ground reference is preferred. Address and control signals should be kept on a different routing layer from DQ, DQS, and DM to isolate crosstalk between the signals.

3.10.2.3 Clock

- Clock signals are routed differentially, and the length matches between traces should be +/- 5 mils.
- It should be referenced to ground plane.
- The space between clock and other signals should be 25 mils.
- One clock signal is routed per rank of the DIMM, that is, one clock for single-ranked DIMM, two clock signals for the dual ranked DIMM. For non-DIMM systems, the differential terminations used by the CK/CK# pair must be located as close as possible to the memory.
- If more than one CS is used, the same clock to DQS skew should be applied to all CS.
- Address/control signals and the associated CK and CK# differential FPGA clock should be routed with trace matching ± 100 mil.

Note: The following guidelines are applicable for DDR2, DDR3, and LPDDR:


- Short the MDDR_TMATCH_0_IN and MDDR_TMATCH_0_OUT pins under BGA using short trace.
- Short the MDDR_TMATCH_1_IN and MDDR_TMATCH_1_OUT pins under BGA using short trace.
- Short the MDDR_TMATCH_ECC_IN and MDDR_TMATCH_ECC_OUT pins under BGA using short trace.
- Short the FDDR_TMATCH_0_IN and FDDR_TMATCH_0_OUT pins under BGA using short trace.
- Short the FDDR_TMATCH_1_IN and FDDR_TMATCH_1_OUT pins under BGA using short trace.
- Short the FDDR_TMATCH_ECC_IN and FDDR_TMATCH_ECC_OUT pins under BGA using short trace.

For more information about DDR2 and LPDDR memory layout guidelines, see the *Micron Memory Layout Guidelines* in the following documents, available on the *Micron website*:

- *TN-47-20: Hardware Tips for Point-to-Point System Design from Micron*
- *TN-46-19: Hardware Tips for Point-to-Point System Design from Micron*

The following figure shows an example layout.

Figure 62 • TMATCH Signals (Example Layout)

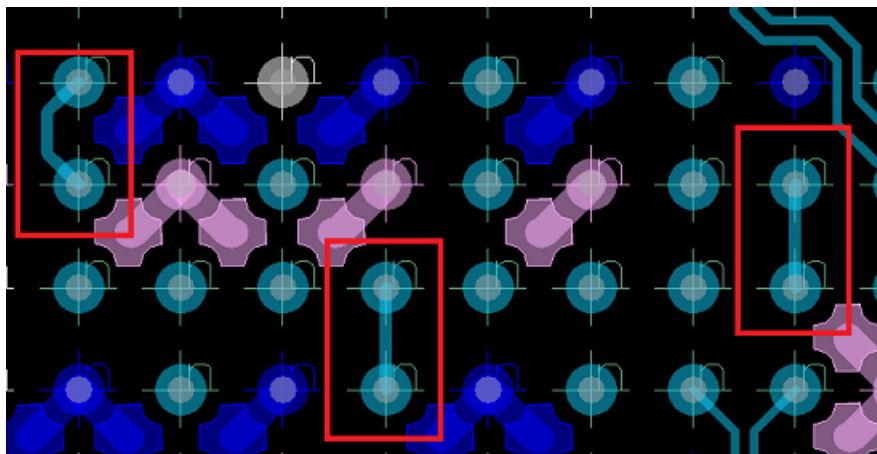

3.10.3 Simulation Considerations

Simulations ensure that the DDR and controller meet timing requirements and also ensure that the quality of the received waveform in terms of undershoot, overshoot and jitter and so on.

The following files are required for the DDR3 simulation:

- IBIS file of SmartFusion2/IGLOO2
- IBIS file of DDR3 memory
- PCB files of SmartFusion2/IGLOO2 board and DIMM, if used
- Connector models if DIMM is used

The following sections describe how to run the serial channel simulations.

3.10.3.1 Step 1: Gathering the Required Files

3.10.3.1.1 IBIS Models

To download the IBIS models of SmartFusion2/IGLOO2 and the IBIS-AMI models of DDR3 memory which is going to interface with SmartFusion2/IGLOO2, see the following web pages on the Microsemi website:

- www.microsemi.com/soc/download/ibis/SmartFusion2.aspx
- www.microsemi.com/soc/download/ibis/IGLOO2.aspx

3.10.3.1.2 PCB Trace Models

The PCB file needs to be converted into a compatible format of simulator software. For example, .HYP file format of PCB is required to simulate in Hyperlynx and SPD file format of PCB is required to simulate in Sigrity. Once the PCB file is loaded in the simulation tool, check the stack-up that matches the PCB stack-up and define the dielectric constant, Dk and dissipation factor, and Df of PCB material. The tool extracts wrong models, if the above points not defined properly. Some tools run the simulations on PCB file itself like Hyperlynx and some tools need S-parameter files of DDR3 traces to continue the simulations. To extract S-parameter models of PCB traces assign the ports on both sides of the traces and extract the S-parameter models of traces.

The following tools can be used to extract S-parameter models of PCB traces:

- Agilent's ADS
- Mentors Hyperlynx
- Sigrity's PowerSI

It is not mandatory to use above tools, there are many tools available in the market which can extract S-parameter models.


3.10.3.2 Step 2: Creating Simulation Topology

These blocks are taken from the Sigrity tool. Topology is the same in any tools. The simulation can be done in any tool, which supports DDR3 simulation.

The following figure shows the typical topology blocks involved in the DDR3 simulations.

- SmartFusion2/IGLOO2 IBIS: IBIS model of SmartFusion2/IGLOO2
- PCB: S-parameter model of PCB file, connector models and DIMM PCB models
- Connector model: Spice models of connector
- Memory IBIS: IBIS models of DDR3 memory

Figure 63 • DDR3 Simulation Topology

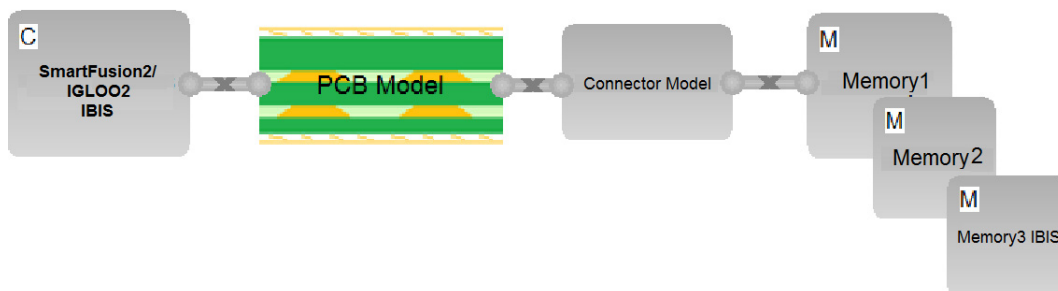

3.10.3.3 Step 3: Simulation Setup

- Assign IBIS models to SmartFusion2/IGLOO2 and memory
- Assign connector model if used
- Assign the models for on board termination resistors
- Identify the DDR3 nets and classify according to data, control and address bus
- Keep the appropriate ODT for SF2 and memory.
- Keep the 40 to 60 Ω ODT for data and 80 to 120 Ω for DQS
- Set the maximum frequency at which the system will operate. For SF2 its 333 MHz

3.10.3.4 Step 4: Results











Observe the following results:

- Setup and hold time between data signals and the respective DQS over all corners.
- Setup and hold time between Control/Command/Address signals and the clock over all corners.
- Overshoot and undershoot of all signals with respect to JEDEC specifications over all corners, and also DC threshold multi crossing that is due to the excessive ringing.

The simulation tool generates the report where all the details are available. For example, Hyperlynx generates the set of excel sheets which contain all setup and hold margin, overshoot, and undershoot information for all corners. It also generates driver and receiver waveforms for all the nets.

The following figure shows the file list where all the information regarding the simulation are stored.

Figure 64 • List of Reports Generated by Hyperlynx

Name	Date modified	Type	Size
 DDR_report_address_allcases_Typ.xls	5/30/2013 12:37 PM	Microsoft Office E...	132 KB
 DDR_report_address_violations_Typ.xls	5/30/2013 12:37 PM	Microsoft Office E...	11 KB
 DDR_report_address_worstcases_Typ.xls	5/30/2013 12:37 PM	Microsoft Office E...	11 KB
 DDR_report_data_allcases_Typ.xls	5/30/2013 12:37 PM	Microsoft Office E...	104 KB
 DDR_report_data_violations_Typ.xls	5/30/2013 12:37 PM	Microsoft Office E...	6 KB
 DDR_report_data_worstcases_Typ.xls	5/30/2013 12:37 PM	Microsoft Office E...	11 KB
 DDR_report_SI_measurements_Typ.xls	5/30/2013 12:37 PM	Microsoft Office E...	11 KB
 DDR_report_skew_allcases_Typ.xls	5/30/2013 12:37 PM	Microsoft Office E...	51 KB
 DDR_report_skew_violations_Typ.xls	5/30/2013 12:37 PM	Microsoft Office E...	6 KB
 DDR_report_skew_worstcases_Typ.xls	5/30/2013 12:37 PM	Microsoft Office E...	11 KB

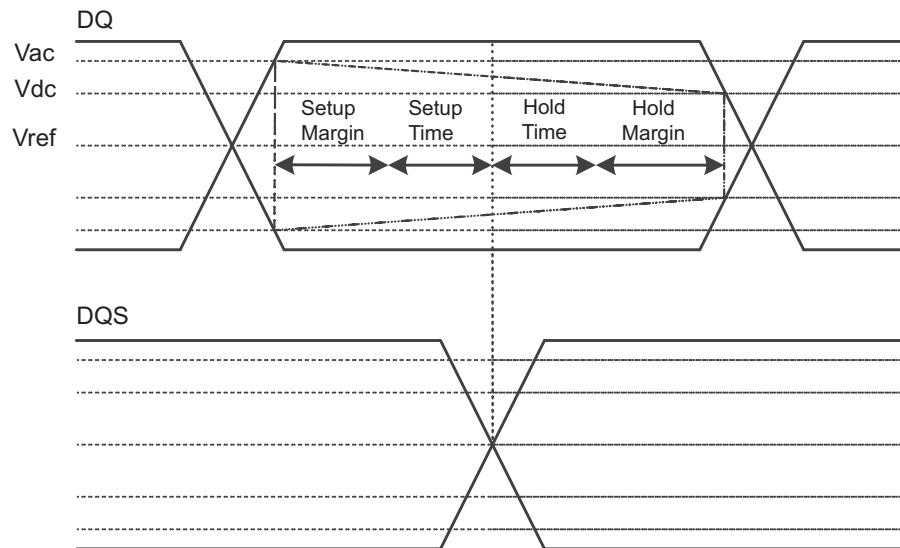
The reports give setup and hold time for each net and also signal integrity details where overshoot and undershoots are mentioned. The following figure shows the example of report for DQ0 net. It also shows that the DQ0 has enough setup and holds time margins.

Figure 65 • Setup and Time Margins of DQ0

	A	O	U
	Net Name	Setup Time Margin, $tDS(\text{margin}) = tDS(\text{min}) - tDS(\text{req})$	Hold Time Margin, $tDH(\text{margin}) = tDH(\text{min}) - tDH(\text{req})$, [ps]
1			
2	DDR2_DQ0	N/A	333.3
3	DDR2_DQ0	267.6	N/A
4	DDR2_DQ0	N/A	316.6

If any of the net is violating the setup and holding time margins, the length of the net should be changed accordingly. If there is any high peak overshoot or undershoot, it might be because of the high value termination resistor. It is required to adjust the value of ODT and re-iterate the simulation.

Figure 66, page 68 shows how to look at setup and hold time margins for DQ and DQS signals. Same is applicable to the margin between the Command/Control/Address and CLK signals.

Figure 66 • Setup and Time Margins for DQ and DQS Signals

3.11 References

- Power Distribution Network (PDN) by Eric Bogatin
- Sigrity PowerSI Tutorial

4 Creating Schematic Symbols Using Cadence OrCAD Capture CIS for SmartFusion2 and IGLOO2 Designs

Creating symbols manually for application can be a time consuming task and is error prone. Cadence OrCAD Capture is a popular schematic design entry tool for system-level design.

This application note describes the recommended procedure to create schematic symbols. The schematic symbols can be created using two methods:

- Using the Microsemi published pin assignment tables (PAT) in spreadsheet format. Pin Information is imported into OrCAD Capture CIS tool. This is a two step process as explained in [Creating Schematic Symbols using Pin Assignment Tables \(PAT\)](#), page 69. Use this method for creating schematic symbols using Microsemi defined pins.
- Using the data export feature of Libero SoC software. Pin information can be exported to a spreadsheet and then use OrCAD Design Capture CIS tool to create symbols. This is a three step process as explained in [Creating Schematic Symbols with User Defined Pin Names](#), page 76. Use this method for creating symbols using user defined pins for the fabric I/Os.

4.1 Creating Schematic Symbols using Pin Assignment Tables (PAT)

4.1.1 Preparing the PAT Layout File for Import into OrCAD Capture

1. Download the PAT files from the following path in the Microsemi website under Datasheets section:
 - www.microsemi.com/products/fpga-soc/soc-fpga/smartfusion2#documents
 - www.microsemi.com/products/fpga-soc/fpga/igloo2-fpga#documents
2. Open the *Pin_Assignment_Table_Public.xlsx file.

Figure 67 • Example PAT Spreadsheet - Initial view

PKG.PIN	M2S0501S/M2S0501T-FG896 Pin Name	Bank No	Direction	Total			Pin Parasitics (Applicable to Usable DIGITAL I/Os ONLY)						Unused Condition
				MSIOD (2.5V max)	MSIO (3.3V max)	DDRIO (2.5V max)	Net Length	SelfR(Ohm)	SelfL(nH)	SelfC(pF)	SelfG(uMho)	Delay(pS)	
A10	DDRIO80PB0/MDDR_DQS_ECC	0	I/O	N	N	Y	14.7524	0.69979	9.75479	1.7336	0	130.042	Libero Defined* DNC
A11	DDRIO88PB0/MDDR_DQ_ECC3	0	I/O	N	N	Y	14.1504	0.712199	9.25784	1.62799	0	122.767	Libero Defined* DNC
A12	DDRIO86PB0/MDDR_DQ0	0	I/O	N	N	Y	13.4834	0.669683	9.24447	1.57524	0	120.674	Libero Defined* DNC
A13	DDRIO84PB0/MDDR_DQS0	0	I/O	N	N	Y	13.4861	0.673458	8.70731	1.57518	0	117.114	Libero Defined* DNC
A14	DDRIO83NB0/MDDR_DQ4	0	I/O	N	N	Y	13.2354	0.675006	8.99641	1.52207	0	117.018	Libero Defined* DNC
A15	DDRIO80PB0/MDDR_DQ8	0	I/O	N	N	Y	13.3326	0.66684	9.24054	1.54588	0	119.519	Libero Defined* DNC
A16	DDRIO78PB0/GB8/CCC_NE0_CLK13/MD	0	I/O	N	N	Y	13.4351	0.694428	8.85242	1.57645	0	118.133	Libero Defined* DNC
A17	DDRIO76PB0/GB12/CCC_NE1_CLK12/MD	0	I/O	N	N	Y	13.3008	0.664554	9.24915	1.55802	0	120.043	Libero Defined* DNC
A18	DDRIO74PB0/MDDR_DQ16	0	I/O	N	N	Y	13.292	0.675689	8.72718	1.54978	0	116.298	Libero Defined* DNC
A19	DDRIO72PB0/MDDR_DQ32	0	I/O	N	N	Y	14.1135	0.678681	9.28264	1.62298	0	122.742	Libero Defined* DNC
A2	SERDES_1_TXD0_N	0	O	N	N	N							DNC
A20	DDRIO71NB0/MDDR_DQ20	0	I/O	N	N	Y	14.1485	0.684028	9.43141	1.64465	0	124.545	Libero Defined* DNC
A21	DDRIO68PB0/MDDR_DQ24	0	I/O	N	N	Y	14.677	0.725941	9.61066	1.69539	0	127.647	Libero Defined* DNC
A22	DDRIO66NB0/MDDR_DQS3_N	0	I/O	N	N	Y	15.0811	0.702886	9.71092	1.74809	0	130.29	Libero Defined* DNC
A23	DDRIO64PB0/MDDR_DQ28	0	I/O	N	N	Y	15.016	0.718421	9.5998	1.72399	0	128.647	Libero Defined* DNC
A24	DDRIO60PB0/MDDR_RESET_N	0	I/O	N	N	Y	15.0875	0.704002	9.88004	1.72551	0	130.568	Libero Defined* DNC
A25	DDRIO59PB0/MDDR_CLK	0	I/O	N	N	Y	15.502	0.722614	9.44108	1.80314	0	130.475	Libero Defined* DNC
A26	DDRIO57PB0/MDDR_BA2	0	I/O	N	N	Y	15.7885	0.706085	9.86659	1.77692	0	132.409	Libero Defined* DNC
A27	DDRIO55PB0/MDDR_ADDR3	0	I/O	N	N	Y	17.2149	0.75996	10.8156	1.95462	0	145.397	Libero Defined* DNC
A28	DDRIO55NB0/MDDR_ADDR4	0	I/O	N	N	Y	17.2833	0.763441	10.7336	1.95027	0	144.684	Libero Defined* DNC

3. Go to the sheet that has the device name that you require.
4. Retain the following columns and delete the remaining columns:
 - PGK.PIN
 - <Device> Pin Name
 - Direction
5. Insert a row at the beginning of the worksheet. See [Figure 68](#), page 70.

Figure 68 • Example PAT Spreadsheet - Editing Stage

	A	B	C	D	E	F	G	H
1								
2	A10	DDRIO90PB0/MDDR_DQS_ECC	I/O					
3	A11	DDRIO88PB0/MDDR_DQ_ECC3	I/O					
4	A12	DDRIO86PB0/MDDR_DQ0	I/O					
5	A13	DDRIO84PB0/MDDR_DQS0	I/O					
6	A14	DDRIO83NB0/MDDR_DQ4	I/O					
7	A15	DDRIO80PB0/MDDR_DQ8	I/O					
8	A16	DDRIO78PB0/GB8/CCC_NE0_CLK13/MDDR_DQS1	I/O					
9	A17	DDRIO76PB0/GB12/CCC_NE1_CLK12/MDDR_DQ12	I/O					
10	A18	DDRIO74PB0/MDDR_DQ16	I/O					
11	A19	DDRIO72PB0/MDDR_DQS2	I/O					
12	A2	SERDES_1_TXD0_N	O					
13	A20	DDRIO71NB0/MDDR_DQ20	I/O					
14	A21	DDRIO68PB0/MDDR_DQ24	I/O					
15	A22	DDRIO66NB0/MDDR_DQS3_N	I/O					
16	A23	DDRIO64PB0/MDDR_DQ28	I/O					
17	A24	DDRIO60PB0/MDDR_RESET_N	I/O					
18	A25	DDRIO59PB0/MDDR_CLK	I/O					
19	A26	DDRIO57PB0/MDDR_BA2	I/O					
20	A27	DDRIO55PB0/MDDR_ADDR3	I/O					
21	A28	DDRIO55NB0/MDDR_ADDR4	I/O					
22	A29	VSS						
23	A3	VSS						
24	A4	SERDES_1_TXD1_N	O					
25	A5	VSS						
26	A6	SERDES_1_TXD2_N	O					
27	A7	VSS						
28	A8	SERDES_1_TXD3_N	O					
29	A9	DDRIO91PB0/GB0/CCC_NW0_CLK13	I/O					
30	AA1	MSIOD134NB7	I/O					
31	AA10	CCC_SW0_PLL_VSSA						
32	AA11	SERDES_0_L01_VDDAIO						
33	AA12	SERDES_0_L23_VDDAIO						
34	AA13	VDDI5						
35	AA14	VDDI5						
36	AA15	VDDI5						
37	AA16	VDDI5						
38	AA17	VDDI5						
39	AA18	VDDI5						
40	AA19	VDDI5						
41	AA2	MSIOD134PB7	I/O					

6. Add the following headings for the columns. See [Figure 69](#), page 71:

- Number
- Name
- Type
- Pin Visibility
- Shape
- Pin Group
- Position
- Section

For Type, Shape, Position, and Section columns, enter the information manually to avoid warnings from the OrCAD Capture tool.

7. For **Type** column, choose and type one of the following options:

- Replace I with Input
- Replace O with Output
- Replace I/O with Bidirectional

Other pin types for the remaining pins:

- 3-State
- Open Collector
- Open Emitter
- Passive (Unused pins like DNC or NC)
- Power (Supply and ground pins)

8. Leave the **Pin Visibility** column blank. The check boxes are automatically populated in the **New Part Creation** dialog in the OrCAD Capture tool. See [Figure 72](#), page 74.

9. In the **Shape** column, enter one of the following shapes according to the requirement:

- Clock
- Dot
- Dot-Clock
- Line
- Short Clock

- Short Dot
- Short Dot clock
- Short
- Zero Length

The default shape for most of the FPGA symbol pins is **LINE**.

10. Leave the **Pin Group** column blank.
11. In the **Position** column, enter one of the following positions according to the requirement:
 - Bottom
 - Left
 - Right
 - Top
12. In the **Section** column, enter either a number or an alphabet based on the selection made for the Part Numbering option. OrCAD Capture supports two Part Numbering options, that is 1,2,3,4,... for Numeric option and A, B, C, D... for Alphabetical option. See [Figure 72](#), page 74
13. **Save** the Excel file with an appropriate name.

Figure 69 • Example PAT Spreadsheet - Final Stage

	A	B	C	D	E	F	G	H
1	Number	Name	Type	Pin Visibility	Shape	Pin Group	Position	Section
2	A1	VSS	Power		Line		Right	L
3	A10	DDRIO75NB0/MDDR_DQ15	Bidirectional		Line		Right	A
4	A11	VSS	Power		Line		Right	L
5	A12	DDRIO83PB0/MDDR_DM_RDQS0	Bidirectional		Line		Right	A
6	A13	DDRIO83NB0/MDDR_DQ4	Bidirectional		Line		Right	A
7	A14	DDRIO82PB0/MDDR_DQ5	Bidirectional		Line		Right	A
8	A15	DDRIO84PB0/MDDR_DQS0	Bidirectional		Line		Right	A
9	A16	VSS	Power		Line		Right	L
10	A17	DDRIO88NB0/MDDR_DQ_ECC2	Bidirectional		Line		Right	A
11	A18	DDRIO88PB0/MDDR_DQ_ECC3	Bidirectional		Line		Right	A
12	A19	DDRIO90PB0/MDDR_DQS_ECC	Bidirectional		Line		Right	A
13	A2	DDRIO53NB0/MDDR_ADDR7	Bidirectional		Line		Left	A
14	A20	DDRIO92PB0/MDDR_TMATCH_ECC_OUT	Bidirectional		Line		Right	A
15	A21	VSS	Power		Line		Right	L
16	A3	DDRIO53PB0/MDDR_ODT	Bidirectional		Line		Left	A
17	A4	DDRIO57NB0/MDDR_ADDR0	Bidirectional		Line		Left	A
18	A5	DDRIO55PB0/MDDR_ADDR3	Bidirectional		Line		Left	A
19	A6	VSS	Power		Line		Right	L
20	A7	DDRIO59NB0/MDDR_CLK_N	Bidirectional		Line		Left	A
21	A8	DDRIO62PB0/MDDR_RAS_N	Bidirectional		Line		Left	A
22	A9	DDRIO62NB0/MDDR_WE_N	Bidirectional		Line		Left	A
23	AA1	VSS	Power		Line		Right	L
24	AA10	DDRIO147NB5/CCC_SW0_CLKI2	Bidirectional		Line		Right	F
25	AA11	DDRIO148NB5/PROBE_B	Bidirectional		Line		Right	F
26	AA12	VSS	Power		Line		Right	L
27	AA13	SERDES_0_TXD2_N	Output		Line		Right	J
28	AA14	VSS	Power		Line		Right	L
29	AA15	SERDES_0_RXD2_P	Input		Line		Left	J
30	AA16	VSS	Power		Line		Right	L
31	AA17	SERDES_0_TXD0_P	Output		Line		Right	J
32	AA18	VSS	Power		Line		Right	L
33	AA19	SERDES_0_RXD0_N	Input		Line		Left	J
34	AA2	MSIO2PB3/USB_STP_B	Bidirectional		Line		Right	D
35	AA20	VSS	Power		Line		Right	L
36	AA21	MSIOD145NB6/SERDES_0_REFCLK0_N	Bidirectional		Line		Right	G
37	AA3	JTAG_TMS/M3_TMS/M3_SWDIO	Input		Line		Left	E
38	AA4	XTLOSC_MAIN_XTAL	Clock		Line		Left	J
39	AA5	NC	Passive		Line		Right	L
40	AA6	DDRIO186PB5/FDDR_ODT	Bidirectional		Line		Right	F
41	AA7	DDRIO186NB5/FDDR_ADDR7	Bidirectional		Line		Right	F


Recommendations for arranging pins in the **Section** column:

- Arrange individual bank pins in separate sections
- Arrange all power supply pins in one section
- Arrange all ground pins in one section
- All passive pins can be in one section
- Arrange the remaining pins like Clock, JTAG, SERDES in one section.

4.1.2 Generating a OrCAD Capture Schematic Symbol

1. Invoke Cadence OrCAD Capture CIS.
2. Go to **File > New > Library**, then select the *.olb file.
3. Go to **Design > New Part from Spreadsheet...**
The **New Part Creation Spreadsheet** dialog appears as shown in the following figure.
4. In the **New Part Creation Spreadsheet** dialog, specify the following:
 - Part Name
 - Number of sections
 - Part Ref Prefix - choose Alphabetic

Figure 70 • New Part Creation Spreadsheet Dialog

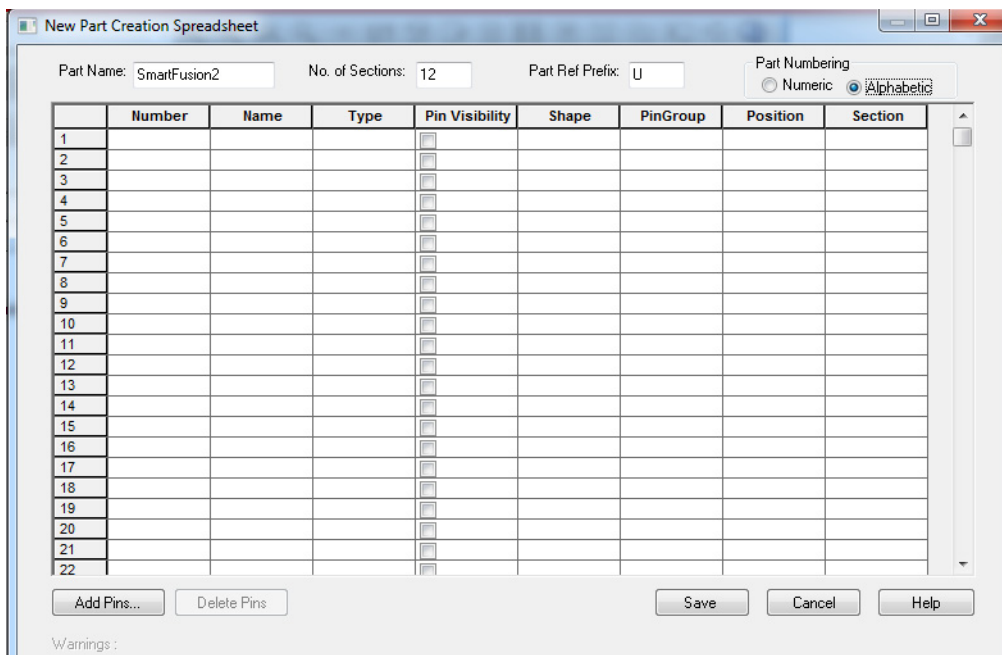

New Part Creation Spreadsheet

Part Name: SmartFusion2 No. of Sections: 12 Part Ref Prefix: U Part Numbering: ☐ Numeric ☒ Alphabetic

	Number	Name	Type	Pin Visibility	Shape	PinGroup	Position	Section
1				<input type="checkbox"/>				
2				<input type="checkbox"/>				
3				<input type="checkbox"/>				
4				<input type="checkbox"/>				
5				<input type="checkbox"/>				
6				<input type="checkbox"/>				
7				<input type="checkbox"/>				
8				<input type="checkbox"/>				
9				<input type="checkbox"/>				
10				<input type="checkbox"/>				
11				<input type="checkbox"/>				
12				<input type="checkbox"/>				
13				<input type="checkbox"/>				
14				<input type="checkbox"/>				
15				<input type="checkbox"/>				
16				<input type="checkbox"/>				
17				<input type="checkbox"/>				
18				<input type="checkbox"/>				
19				<input type="checkbox"/>				
20				<input type="checkbox"/>				
21				<input type="checkbox"/>				
22				<input type="checkbox"/>				

Add Pins... Delete Pins Save Cancel Help

Warnings :

- From the Example PAT Spreadsheet, select and copy all the cells, excluding the column headers as shown in the following figure.


Figure 71 • Example PAT Spreadsheet - Final Stage

	A	B	C	D	E	F	G	H
1	Number	Name	Type	Pin Visibility	Shape	Pin Group	Position	Section
2	A1	VSS	Power		Line		Right	L
3	A10	DDRIO75NB0/MDDR_DQ15	Bidirectional		Line		Right	A
4	A11	VSS	Power		Line		Right	L
5	A12	DDRIO83PB0/MDDR_DM_RDQS0	Bidirectional		Line		Right	A
6	A13	DDRIO83NB0/MDDR_DQ4	Bidirectional		Line		Right	A
7	A14	DDRIO82PB0/MDDR_DQ5	Bidirectional		Line		Right	A
8	A15	DDRIO84PB0/MDDR_DQS0	Bidirectional		Line		Right	A
9	A16	VSS	Power		Line		Right	L
10	A17	DDRIO88NB0/MDDR_DQ_ECC2	Bidirectional		Line		Right	A
11	A18	DDRIO88PB0/MDDR_DQ_ECC3	Bidirectional		Line		Right	A
12	A19	DDRIO90PB0/MDDR_DQS_ECC	Bidirectional		Line		Right	A
13	A2	DDRIO53NB0/MDDR_ADDR7	Bidirectional		Line		Left	A
14	A20	DDRIO92PB0/MDDR_TMATCH_ECC_OUT	Bidirectional		Line		Right	A
15	A21	VSS	Power		Line		Right	L
16	A3	DDRIO53PB0/MDDR_ODT	Bidirectional		Line		Left	A
17	A4	DDRIO57NB0/MDDR_ADDR0	Bidirectional		Line		Left	A
18	A5	DDRIO55PB0/MDDR_ADDR3	Bidirectional		Line		Left	A
19	A6	VSS	Power		Line		Right	L
20	A7	DDRIO59NB0/MDDR_CLK_N	Bidirectional		Line		Left	A
21	A8	DDRIO62PB0/MDDR_RAS_N	Bidirectional		Line		Left	A
22	A9	DDRIO62NB0/MDDR_WE_N	Bidirectional		Line		Left	A
23	AA1	VSS	Power		Line		Right	L
24	AA10	DDRIO147NB5/CCC_SW0_CLKI2	Bidirectional		Line		Right	F
25	AA11	DDRIO148NB5/PROBE_B	Bidirectional		Line		Right	F
26	AA12	VSS	Power		Line		Right	L
27	AA13	SERDES_0_TXD2_N	Output		Line		Right	J
28	AA14	VSS	Power		Line		Right	L
29	AA15	SERDES_0_RXD2_P	Input		Line		Left	J
30	AA16	VSS	Power		Line		Right	L
31	AA17	SERDES_0_TXD0_P	Output		Line		Right	J
32	AA18	VSS	Power		Line		Right	L
33	AA19	SERDES_0_RXD0_N	Input		Line		Left	J
34	AA2	MSIO2PB3/USB_STP_B	Bidirectional		Line		Right	D
35	AA20	VSS	Power		Line		Right	L
36	AA21	MSIOD145NB6/SERDES_0_REFCLK0_N	Bidirectional		Line		Right	G
37	AA3	JTAG_TMS/M3_TMS/M3_SWDIO	Input		Line		Left	E
38	AA4	XTLOSC_MAIN_XTAL	Clock		Line		Left	J
39	AA5	NC	Passive		Line		Right	L
40	AA6	DDRIO186PB5/FDDR_ODT	Bidirectional		Line		Right	F
41	AA7	DDRIO186NB5/FDDR_ADDR7	Bidirectional		Line		Right	F

6. Select the top left cell of **New Part Creation Spreadsheet** dialog and paste the copied data. Check if all the columns match between the Example PAT Spreadsheet and **New part creation Spreadsheet** dialog as shown in the following figure.

Note: In the **Pin Visibility** column, select all the check boxes. Some of the check boxes for the power pins might not be selected. If you want those pins to be visible, ensure that they are selected.

Figure 72 • New Part Creation Spreadsheet Dialog with Data

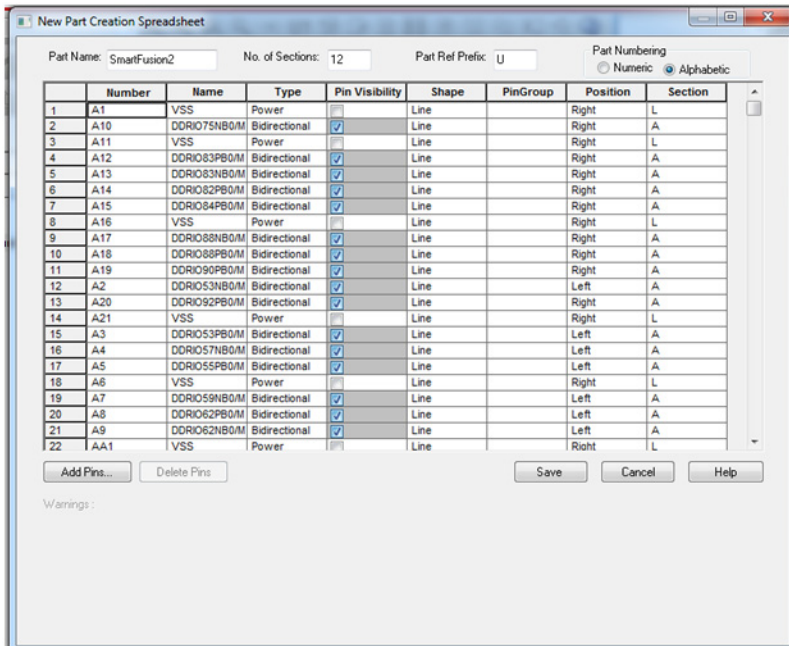


	Number	Name	Type	Pin Visibility	Shape	PinGroup	Position	Section
1	A1	VSS	Power	<input type="checkbox"/>	Line		Right	L
2	A10	DDRIO75NB0/M	Bidirectional	<input checked="" type="checkbox"/>	Line		Right	A
3	A11	VSS	Power	<input type="checkbox"/>	Line		Right	L
4	A12	DDRIO83PB0/M	Bidirectional	<input checked="" type="checkbox"/>	Line		Right	A
5	A13	DDRIO83NB0/M	Bidirectional	<input checked="" type="checkbox"/>	Line		Right	A
6	A14	DDRIO82PB0/M	Bidirectional	<input checked="" type="checkbox"/>	Line		Right	A
7	A15	DDRIO84PB0/M	Bidirectional	<input checked="" type="checkbox"/>	Line		Right	A
8	A16	VSS	Power	<input type="checkbox"/>	Line		Right	L
9	A17	DDRIO88NB0/M	Bidirectional	<input checked="" type="checkbox"/>	Line		Right	A
10	A18	DDRIO88PB0/M	Bidirectional	<input checked="" type="checkbox"/>	Line		Right	A
11	A19	DDRIO90PB0/M	Bidirectional	<input checked="" type="checkbox"/>	Line		Right	A
12	A2	DDRIO53NB0/M	Bidirectional	<input checked="" type="checkbox"/>	Line		Left	A
13	A20	DDRIO92PB0/M	Bidirectional	<input checked="" type="checkbox"/>	Line		Right	A
14	A21	VSS	Power	<input type="checkbox"/>	Line		Right	L
15	A3	DDRIO53PB0/M	Bidirectional	<input checked="" type="checkbox"/>	Line		Left	A
16	A4	DDRIO57NB0/M	Bidirectional	<input checked="" type="checkbox"/>	Line		Left	A
17	A5	DDRIO55PB0/M	Bidirectional	<input checked="" type="checkbox"/>	Line		Left	A
18	A6	VSS	Power	<input type="checkbox"/>	Line		Right	L
19	A7	DDRIO59NB0/M	Bidirectional	<input checked="" type="checkbox"/>	Line		Left	A
20	A8	DDRIO62PB0/M	Bidirectional	<input checked="" type="checkbox"/>	Line		Left	A
21	A9	DDRIO62NB0/M	Bidirectional	<input checked="" type="checkbox"/>	Line		Left	A
22	AA1	VSS	Power	<input type="checkbox"/>	Line		Right	L

7. Click **Save**.


Note: When you click save, the Design Rule Check (DRC) operation is triggered. If there are any errors reported during the DRC, modify the Example PAT Spreadsheet to fix those errors. If there are just warnings and if you want to ignore them, click **Continue** to proceed with generating the Part.

Figure 73 • New Part created in the Library

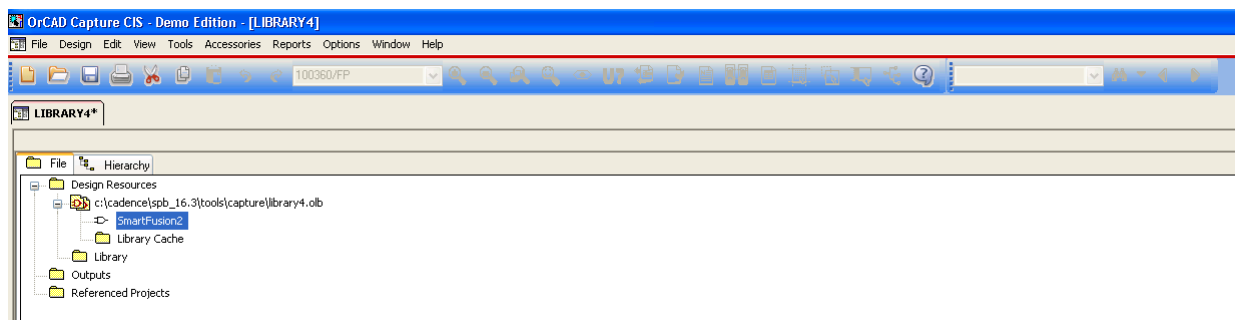

8. Double-click the part that is created to display the first section as shown in the following figure.


Figure 74 • Schematic Symbol - First Section

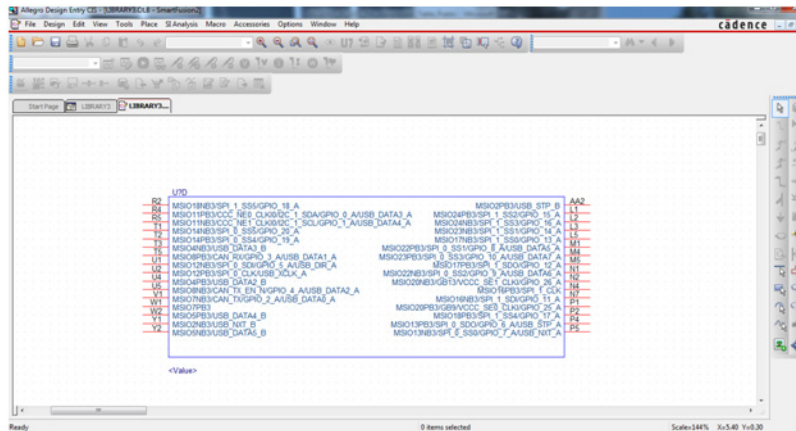

9. You can navigate to all the sections that are created.
- To go to the next part, go to **View > Next Part** or press Ctrl + N.
 - To go to the previous part, go to **View > Previous Part** or press Ctrl + B.
 - To see all the blocks of the schematic symbol, go to **View > Package**.

The schematic symbol is ready to use. The following figure shows all the blocks of the schematic symbol that are generated from the Example PAT spreadsheet.

Figure 75 • Package View of the Schematic Symbol

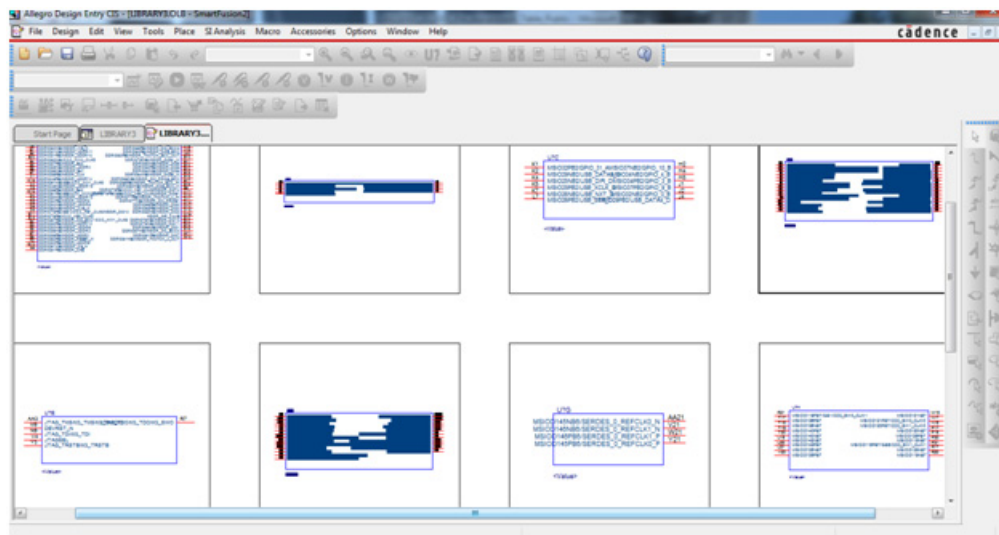


4.2 Creating Schematic Symbols with User Defined Pin Names

4.2.1 Exporting Pin Information from the Libero Design


1. Launch Libero and open project. For more information about how to use the System Builder wizard in the Libero design, see
http://coredocs.s3.amazonaws.com/Actel/Tool/SysBuilder/sf2_system_builder_ug_1.pdf
http://coredocs.s3.amazonaws.com/Libero/Tool/SysBuilder/igl2_system_builder_ug_1.pdf
2. Right-click port to change the name and click **Modify Port** as shown in the following figure. Change the name according to the requirement.

Figure 76 • Modifying Port Names

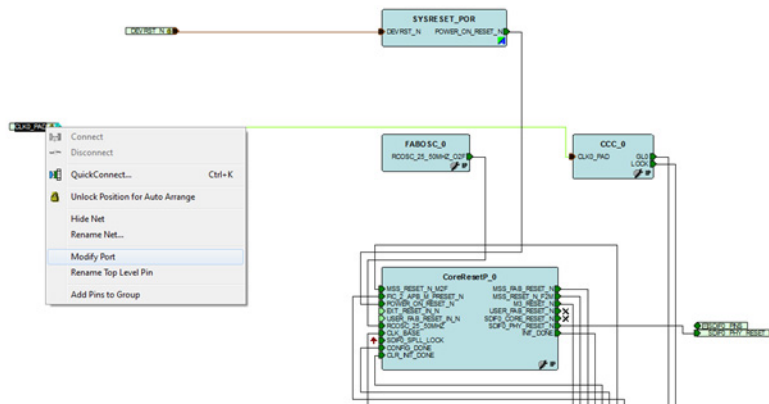

3. Check and verify all the pin names in the design. To verify the pin names, double-click **I/O Constraints** in the **Design Flow** tab as shown in the following figure.

Figure 77 • I/O Constraints

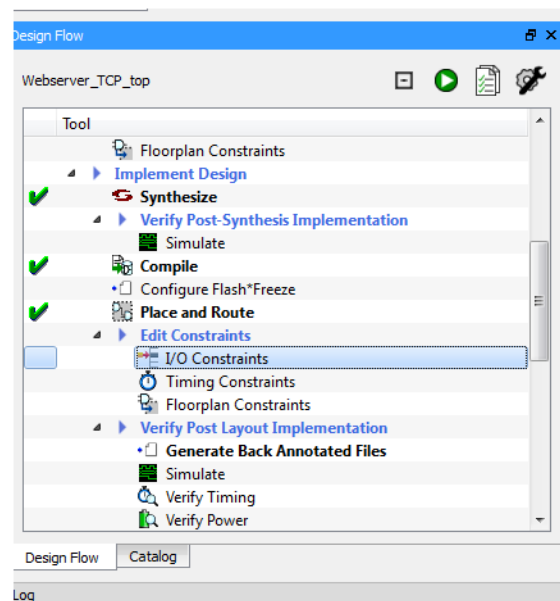


The **I/O Editor** dialog lists the port names with the updated pin names as shown in the following figure. The pin names that are not modified follow the Microsemi pin naming convention.

Note: For the **I/O Editor** dialog to open, the design must be synthesized and compiled.

Figure 78 • I/O Editor

I/O Editor						
Port Name ▲	Direction	I/O Standard	Pin Number	Locked	Bank Name	I/O state in Flash/Freeze mode
CLK0_PAD	Input	LVC MOS25	U7	<input checked="" type="checkbox"/>	Bank7	TRISTATE
DEVRST_N	Input		AC27	<input checked="" type="checkbox"/>	--	--
G4M_RCYRD_CLK1	Output	LVC MOS33	P9	<input checked="" type="checkbox"/>	Bank8	TRISTATE
G4M_RCYRD_CLK2	Output	LVC MOS33	R9	<input checked="" type="checkbox"/>	Bank8	TRISTATE
G4M_SYNCE_IN	Input	LVC MOS33	P3	<input checked="" type="checkbox"/>	Bank8	TRISTATE
G4M_SYNCE_OUT	Output	LVC MOS25	L23	<input checked="" type="checkbox"/>	Bank1	TRISTATE
GPIO_8_M2F	Output	LVC MOS25	A18	<input checked="" type="checkbox"/>	Bank0	TRISTATE
GPIO_9_M2F	Output	LVC MOS25	B18	<input checked="" type="checkbox"/>	Bank0	TRISTATE
GPIO_10_M2F	Output	LVC MOS25	D18	<input checked="" type="checkbox"/>	Bank0	TRISTATE
GPIO_11_M2F	Output	LVC MOS25	E18	<input checked="" type="checkbox"/>	Bank0	TRISTATE
GPIO_12_M2F	Output	LVC MOS25	A20	<input checked="" type="checkbox"/>	Bank0	TRISTATE
GPIO_13_M2F	Output	LVC MOS25	D20	<input checked="" type="checkbox"/>	Bank0	TRISTATE
GPIO_14_M2F	Output	LVC MOS25	E20	<input checked="" type="checkbox"/>	Bank0	TRISTATE
GPIO_15_M2F	Output	LVC MOS25	B20	<input checked="" type="checkbox"/>	Bank0	TRISTATE
MMUART_1_RXD_F2M	Input	LVC MOS25	R29	<input checked="" type="checkbox"/>	Bank3	TRISTATE
MMUART_1_TXD_M2F	Output	LVC MOS25	R24	<input checked="" type="checkbox"/>	Bank3	TRISTATE
PHY_MDC	Output	LVC MOS33	N5	<input checked="" type="checkbox"/>	Bank8	TRISTATE
PHY_MDIO	Input	LVC MOS33	R7	<input checked="" type="checkbox"/>	Bank8	TRISTATE
PHY_RST	Output	LVC MOS33	N4	<input checked="" type="checkbox"/>	Bank8	TRISTATE
REFCLK1_P	Input	LVDS	AF1	<input checked="" type="checkbox"/>	Bank6	TRISTATE
REFCLK1_N	Input	LVDS	AE1	<input checked="" type="checkbox"/>	Bank6	TRISTATE
RXD0_N	Input		AB9	<input checked="" type="checkbox"/>	--	--
RXD0_P	Input		AB8	<input checked="" type="checkbox"/>	--	--
RXD1_N	Input		AC10	<input checked="" type="checkbox"/>	--	--
RXD1_P	Input		AC9	<input checked="" type="checkbox"/>	--	--
RXD2_N	Input		AB11	<input checked="" type="checkbox"/>	--	--
RXD2_P	Input		AB10	<input checked="" type="checkbox"/>	--	--
RXD3_N	Input		AD11	<input checked="" type="checkbox"/>	--	--

Figure 79 • Exporting pin information from Libero

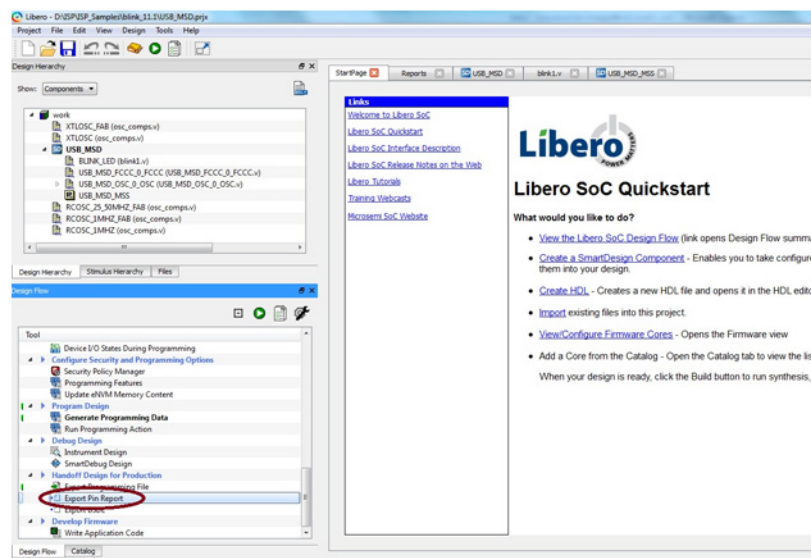


- To export the pin names, double-click **Export Pin Report** in the **Design Flow** tab. This report has the file extension . rpt.

The report is stored in the project directory. The path is:
<Libero Project Directory>\designer\project\export\<project Name>_top_pinrpt_number.rpt.

4.2.2 Preparing the Pin List for Import into OrCAD Capture CIS


1. Launch Microsoft Excel, and open the *.rpt file that has the exported pin information. Before you open, ensure that **All Files (*.*)** is the file type as shown in the following figure.

Figure 80 • Importing Pin Names to the Spreadsheet

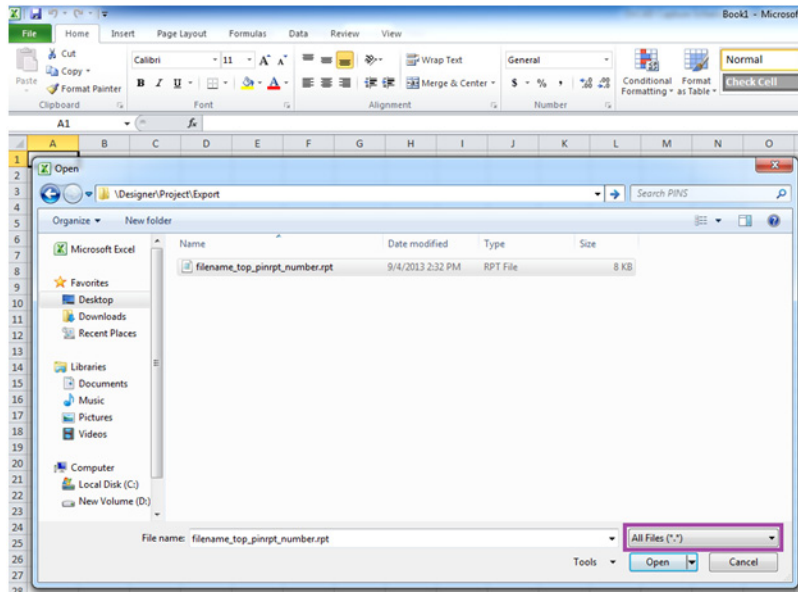


2. In the **Text Import Wizard - Step 1** dialog, select **Delimited**, start import at page 14 and click **Next**. The first 14 rows of the spreadsheet have data unrelated to the pin information. The following figure shows the **Text Import Wizard** with the **Delimited** option selected and the **Start import at page** option having the value 14.

Figure 81 • Importing Pin Names to the Spreadsheet—Step 1

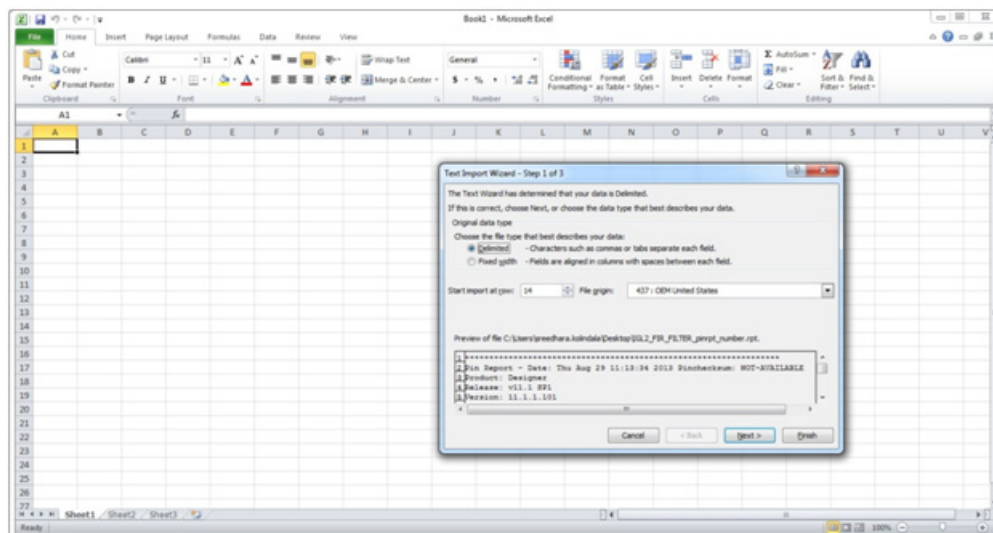

3. In the **Text Import Wizard - Step 2** dialog, select the following as Delimiters and click **Next**:
 - Tab
 - Space
 - I as other

Figure 82 • Importing Pin Names to the Spreadsheet—Step 2

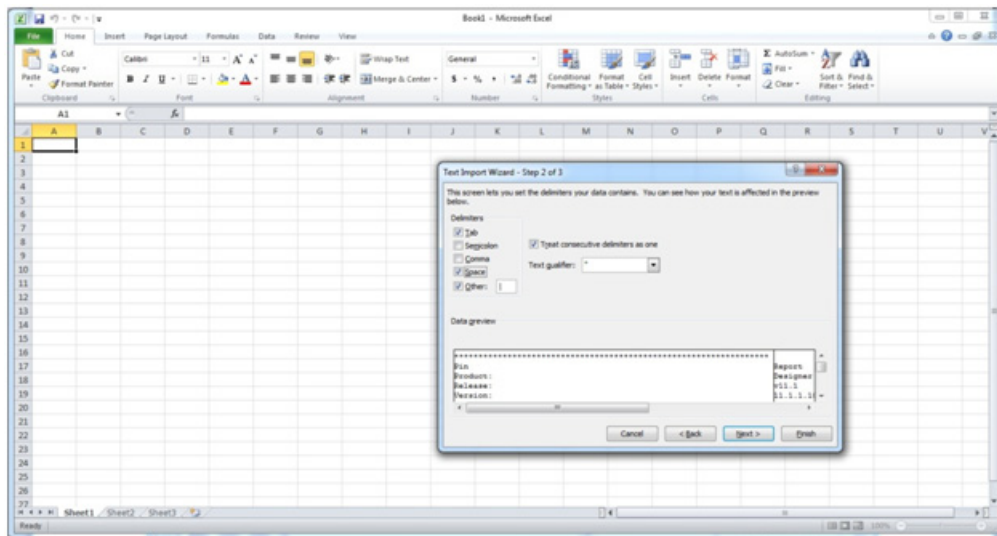

4. Click **Finish** to import the data in separate columns.

Figure 83 • Importing Pin Names to the Spreadsheet—Final Step

	A	B	C	D	E	F	G	H	I	J	K	L	M	N	O	P	Q	R	S
56	Q61	NC04	Reserved																
57	A883	CLK0_PAD	MSIO05P84/CCC_NEO_CLK0	Special	LVCMS025	Input	TRISTATE	None	No	OFF	---	---	OFF	OFF	---	---	---	---	---
58	A884	MSIO05NB4	Unassigned																
59	E20	VDD01	Reserved																
60	E21	MSIO20NB1	Unassigned																
61	E22	HPMS_INT_M2F[4]	MSIO25PB1	Assigned	LVCMS025	Output	TRISTATE	None	No	---	---	---	---	---	SLOW	---	4	5	
62	F1	VDDT	Reserved																
63	F17	DORH032NB0/MDDR_ADDR9	Unassigned																
64	F18	HPMS_INT_M2F[7]	MSIO24NB1	Assigned	LVCMS025	Output	TRISTATE	None	No	---	---	---	---	---	SLOW	---	4	5	
65	F19	HPMS_INT_M2F[8]	MSIO24PB1	Assigned	LVCMS025	Output	TRISTATE	None	No	---	---	---	---	---	SLOW	---	4	5	
66	F20	HPMS_INT_M2F[1]	MSIO21NB1	Assigned	LVCMS025	Output	TRISTATE	None	No	---	---	---	---	---	SLOW	---	4	5	
67	F21	COMM_BK4_INT	MSIO23PB1	Assigned	LVCMS025	Output	TRISTATE	None	No	---	---	---	---	---	SLOW	---	4	5	
68	F22	VDD01	Reserved																
69	G1	MSIO78NB7	Unassigned																
70	G18	HPMS_INT_M2F[18]	MSIO22NB1	Assigned	LVCMS025	Output	TRISTATE	None	No	---	---	---	---	---	SLOW	---	4	5	
71	G19	HPMS_INT_M2F[14]	MSIO21PB1/G86	Special	LVCMS025	Output	TRISTATE	None	No	---	---	---	---	---	SLOW	---	4	5	
72	G20	VSS	Reserved																
73	H18	VDD01	Reserved																
74	H19	HPMS_INT_M2F[5]	MSIO21NB1	Assigned	LVCMS025	Output	TRISTATE	None	No	---	---	---	---	---	SLOW	---	4	5	
75	H20	HPMS_INT_M2F[6]	MSIO21PB1/G85	Special	LVCMS025	Output	TRISTATE	None	No	---	---	---	---	---	SLOW	---	4	5	
76	H21	NC	Reserved																
77	I17	CCC_NE1_PIL_VDDA	Reserved																
78	I18	FC32_0_LOCK	MSIO20NB2	Assigned	LVCMS025	Output	TRISTATE	None	No	---	---	---	---	---	SLOW	---	4	5	
79	I19	NC	Reserved																
80	I20	NC	Reserved																
81	I21	VDD01	Reserved																
82	I22	NC	Reserved																
83	K1	FC32_0_CLK	MSIO05P84/CCC_NE1_CLK1	Special	LVCMS025	Output	TRISTATE	None	No	---	---	---	---	---	SLOW	---	4	5	
84	K2	MSIO05NB6	Unassigned																
85	K3	VSS	Reserved																
86	K34	VDD	Reserved																
87	K35	HPMS_INT_M2F[13]	MSIO18NB2	Assigned	LVCMS025	Output	TRISTATE	None	No	---	---	---	---	---	SLOW	---	4	5	
88	K36	HPMS_INT_M2F[12]	MSIO19NB2	Assigned	LVCMS025	Output	TRISTATE	None	No	---	---	---	---	---	SLOW	---	4	5	
89	K37	HPMS_INT_M2F[1]	MSIO19PB2	Assigned	LVCMS025	Output	TRISTATE	None	No	---	---	---	---	---	SLOW	---	4	5	
90	K38	MSIO20NB2	Unassigned																
91	K39	VSS	Reserved																
92	K20	HPMS_INT_M2F[13]	MSIO17NB2	Assigned	LVCMS025	Output	TRISTATE	None	No	---	---	---	---	---	SLOW	---	4	5	
93	K21	HPMS_INT_M2F[16]	MSIO17PB2	Assigned	LVCMS025	Output	TRISTATE	None	No	---	---	---	---	---	SLOW	---	4	5	

5. Retain the columns A, B, F and delete the remaining columns as they are not required for generating schematic symbols.

Figure 84 • Spreadsheet with the Pin Names Imported

	A	B	C	D	E	F	G	H	I	J	K	L	M	N	O	P	Q
56	AB12	VDDM4															
57	AB13	CLK0_PAD	Input														
58	AB14	MSIO305NB4															
59	E20	VDDI1															
60	E21	MSIO25NB1															
61	E22	HPMS_INT_M2F[4]	Output														
62	F1	VDDI7															
63	F17	DORIO32NB0/MDO08_ADDR9															
64	F18	HPMS_INT_M2F[7]	Output														
65	F19	HPMS_INT_M2F[8]	Output														
66	F20	HPMS_INT_M2F[1]	Output														
67	F21	COMM_BLK_INT	Output														
68	F22	VDDI1															
69	G1	MSIO78NB7															
70	G18	HPMS_INT_M2F[10]	Output														
71	G19	HPMS_INT_M2F[14]	Output														
72	G20	VSS															
73	H18	VDDI1															
74	H19	HPMS_INT_M2F[5]	Output														
75	H20	HPMS_INT_M2F[6]	Output														
76	H21	NC															
77	I17	CCC_NE1_PLL_VDDA															
78	I18	FIC32_0_LOCK	Output														
79	I19	NC															
80	I20	NC															
81	I21	VDDI1															
82	I22	NC															
83	K1	FIC32_0_CLK	Output														
84	K2	MSIOD85NB6															
85	K13	VSS															
86	K14	VDD															
87	K15	HPMS_INT_M2F[13]	Output														
88	K16	HPMS_INT_M2F[2]	Output														
89	K17	HPMS_INT_M2F[3]	Output														
90	K18	MSIO20PB2															
91	K19	VSS															
92	K20	HPMS_INT_M2F[15]	Output														
93	K21	HPMS_INT_M2F[0]	Output														
94	K22	NC															
95	L1	VSS															
96	L2	MSIOD86PB6															

6. Add the following headings for the columns. See [Figure 85](#), page 81.

- Number
- Name
- Type
- Pin Visibility
- Shape
- Pin Group
- Position
- Section

By default Number, Name and Type columns are populated from the report. For Type, Shape, Position, and Section columns, add information manually to avoid warnings from the OrCAD Capture tool.

7. For **Type** column, choose and type one of the following options:

- 3-State
- Bidirectional
- Input
- Open Collector
- Open Emitter
- Output
- Passive (Unused pins like DNC or NC)
- Power (Supply and ground pins)

8. Leave the **Pin Visibility** column blank. The check boxes are automatically populated in the **New Part Creation** dialog.

9. In the **Shape** column, enter one of the following shapes according to the requirement:

- Clock
- Dot
- Dot-Clock
- Line
- Short Clock
- Short Dot
- Short Dot clock
- Short
- Zero Length

The default shape for most of the FPGA symbol pins is the **LINE**.

10. Leave the **Pin Group** column blank.
11. In the **Position** column, enter one of the following positions according to the requirement:
 - Bottom
 - Left
 - Right
 - Top
12. In the **Section** column, enter either a number or an alphabet based on the selection made for the Part Numbering option. OrCAD Capture supports two Part Numbering options, that is, 1, 2, 3, 4,... for **Numeric** option and A, B, C, D... for **Alphabetical** option.
13. **Save** the Excel file with an appropriate name.

The following figure shows the final pin assignment spreadsheet.

Figure 85 • Final Example Spreadsheet to be Imported into OrCAD Capture

1	Number	Name	Type	Pin Visibility	Shape	Pin Group	Position	Section
2	AB13	CLK0_PAD	Input		Clock		Right	A
3	E22	HPMS_INT_M2F[4]	Output		Line		Right	A
4	F18	HPMS_INT_M2F[7]	Output		Line		Right	A
5	F19	HPMS_INT_M2F[8]	Output		Line		Right	A
6	F20	HPMS_INT_M2F[1]	Output		Line		Right	A
7	F21	COMM_BLK_INT	Output		Line		Right	A
8	G18	HPMS_INT_M2F[10]	Output		Line		Right	A
9	G19	HPMS_INT_M2F[14]	Output		Line		Right	A
10	H19	HPMS_INT_M2F[5]	Output		Line		Right	A
11	H20	HPMS_INT_M2F[6]	Output		Line		Right	A
12	J18	FIC32_0_LOCK	Output		Line		Right	A
13	K1	FIC32_0_CLK	Output		Line		Left	A
14	K15	HPMS_INT_M2F[13]	Output		Line		Left	A
15	K16	HPMS_INT_M2F[2]	Output		Line		Left	A
16	K17	HPMS_INT_M2F[3]	Output		Line		Left	A
17	K18	MSIO20PB2	Bidirectional		Line		Left	A
18	K19	VSS	Power		Short		Right	C
19	K20	HPMS_INT_M2F[15]	Output		Line		Left	A
20	K21	HPMS_INT_M2F[0]	Output		Line		Left	A
21	K22	NC	Passive		Line		Left	D
22	L6	VDDI6	Power		Short		Right	B
23	L9	VDD	Power		Short		Left	B
24	L18	HPMS_INT_M2F[9]	Output		Line		Left	A
25	L19	HPMS_FAB_RESET_N	Output		Line		Left	A

4.2.3 Generating a Capture Schematic Symbol

See Generating a OrCAD Capture Schematic Symbol, page 72“.

5 Board Design and Layout Checklist

This chapter provides a set of checks for designing hardware using Microsemi SmartFusion2 and IGLOO2 FPGAs. The checklists provided in this chapter are a high-level summary to assist the design engineers in the design process.

5.1 Prerequisites

Ensure that you have gone through the following chapters before reading this chapter:

- [Board Design Guidelines for SmartFusion2 SoC and IGLOO2 FPGAs](#), page 4
- [Layout Guidelines for SmartFusion2- and IGLOO2-Based Board Design](#), page 38

This checklist is intended as a guideline only. The SmartFusion2 and IGLOO2 families consists of FPGAs ranging from densities of 6 K to 100 K logic elements (LE).

5.2 Design Checklist

The following table lists the checks that design engineers must take care of while designing the system.

Table 23 • Design Checklist

S.No.	Checklist	Yes/No
Prerequisites		
1.	Read datasheet and pin description user guides: – IGLOO2 and SmartFusion2 Datasheet – IGLOO2 Pin Descriptions – SmartFusion2 Pin Descriptions	
2.	Check for available designs and development tools.	
3.	Refer to the board-level schematics of the SmartFusion2 Security Evaluation Kit or SmartFusion2 Advanced Development Kit .	
Design Specifications		
4.	Draw the high-level design with architectural block diagram including all the basic interfaces.	
5.	Specify all the I/O interfaces for all banks in the FPGA.	
6.	Create a detailed functional verification test plan.	
7.	Check for IP software that impacts the system design.	
Device Selection		
8.	Check for available device variants of the SmartFusion2 or IGLOO2 FPGA. Select a device based on the I/O pin count, transceivers, microcontroller subsystem (MSS) peripherals, phase-locked loops (PLLs), and speed grade.	
9.	Check device errata: – SmartFusion2 Errata – SmartFusion2 M2S150ES/M2S090ES Errata – IGLOO2 Errata	
10.	Compare the design requirements with the available interfaces and number of I/Os.	
11.	Estimate the required logic utilization, memory, number of I/O pins, and density.	

Table 23 • Design Checklist (continued)

S.No.	Checklist	Yes/No
12.	Vertical Migration If desiring pin compatibility within the same package, choose the largest density device for easy vertical migration without any pin conflict in case of future development. For more information, refer to the application notes available under Schematics/PCB section.	
13.	Identify the clocking requirements.	
14.	Verify that the number of differential channels is adequate.	
Design		
15.	Power Analysis Perform power analysis and check the results against the power budget. (Microsemi Power Calculator can be used to analyze the power consumption. Estimate the dynamic and static power consumption, and ensure that the design does not violate the power budget.)	
16.	Noise Margin Analysis Analyze the dynamic drive capability of output drivers to ensure that the drivers are not loaded beyond the limits (V_{OH} , V_{OL} , V_{IH} , and V_{IL}). Loading Analysis Analyze the dynamic drive capability of output drivers to confirm that the drivers are not loaded beyond the limits (C_L)	
17.	Programming and Debugging Scheme Check for the programming modes and the procedure to program the device. For programming or debugging through JTAG, add a 10-pin vertical header (2.54 mm pitch). For more information about programming, see IGLOO2 Programming User Guide and SmartFusion2 Programming User Guide .	
Power Supply		
18.	Reference Documentation – IGLOO2 and SmartFusion2 Datasheet , Operating Conditions section – IGLOO2 Pin Descriptions / SmartFusion2 Pin Descriptions – Figure 1, page 5 (for more detailed connectivity)	
19.	Voltage Rails The design can be created with just two voltage rails. See Obtaining a Two-Rail Design for Non-SerDes Applications , page 35.	
20.	VDD: Core Supply VDD operates at 1.2 V.	
21.	VPP: Programming Supply Charge pump and eNVM can operate at 2.5 V or 3.3 V.	
22.	VDDI Bank Supplies Connect VDDI pins to support the I/O standards of each bank. Ensure I/O power pin compatibility with I/O standards. Check for the banks that must be powered even when unused. For recommendations on unused bank supplies, see Table 18 , page 34. The recommendations vary from device to device.	

Table 23 • Design Checklist (continued)

S.No.	Checklist	Yes/No
23.	SerDes Power Supplies <ul style="list-style-type: none"> – SERDES VDD - VDD – SERDES VDDAIO - 1.2 V – SERDES VDDAPLL to REFRET through resistor-capacitor (RC) filter circuitry (2.5 V) – SERDES PLL VDDA to PLL VSSA through RC filter circuitry - 2.5 V or 3.3 V VDDA PLL Filter <ul style="list-style-type: none"> – REFRET for the SerDes serves as the local on-chip ground return path for VDDAPLL. Therefore, external board ground must not short with REFRET under any circumstances. – A high precision 1.21K_1% Ω resistor is required to connect between REXT and REFRET. <p>For detailed information about power supplies, see Figure 1, page 5.</p>	
24.	If SERDES transceiver is not used, the pins need to be connected as follows: <ul style="list-style-type: none"> – SERDES VDD - VDD – SERDES VDDAIO - 1.2 V – SERDES VDDAPLL - 1.2 V or 2.5 V – SERDES PLL VDDA - 2.5 V or 3.3 V – SERDES PLL VSSA - Ground 	
25.	V_{REF} Power Supply Design V _{REF} pins to be noise free. V _{REF} should be equal to half of VDDQ. See Figure 16 , page 30.	
26.	Other Supplies CCC PLL VDDA to PLL VSSA through RC filter circuitry- 2.5 V/ 3.3 V. DDR PLL VDDA to PLL VSSA through RC filter circuitry- 2.5 V/ 3.3 V. All PLL VDDA supplies must be tied to same supply source (either 2.5 V or 3.3 V). Using the Libero SoC software, a single supply can be selected globally.	
27.	Decoupling Capacitors Perform power integrity (PI) analysis through the PI tool, and analyze the decoupling capacitor values and placement on the PCB.	
28.	Unused Condition For unused conditions of power supply pins, see the corresponding pin assignment table available on the following pages: SmartFusion2 SoC FPGA Documentation IGLOO2 FGPA Documentation Also see Figure 4 , page 14.	
29.	Brownout Detection (BOD) Circuit Ensure that brownout detection is implemented standalone or included as part of power management circuitry. See Brownout Detection (BOD) , page 36.	

Table 23 • Design Checklist (continued)

S.No.	Checklist	Yes/No
Clocks		
30.	<p>Crystal Oscillators (External)</p> <ul style="list-style-type: none"> – Main crystal oscillator – Auxiliary (RTC) crystal oscillator (not available in the M2S050T) <p>RC Oscillators (Internal)</p> <ul style="list-style-type: none"> – 1-MHz RC oscillator – 50-MHz RC oscillator <p>IGLOO2 devices have only main crystal oscillator without auxiliary (RTC) crystal oscillator. For more information about crystal oscillators, see Table 14, page 20.</p> <p>FPGA Fabric Clock Sources</p> <p>The input clock frequency range for fabric clock conditioning circuits (FABCCC) depends on the usage of PLL for output clock generation:</p> <ul style="list-style-type: none"> – If the PLL is used, the PLL reference clock frequency must be between 1 MHz and 200 MHz. – If the PLL is bypassed, the FABCCC input clock frequency can be up to 400 MHz. <p>All CCC pins support external oscillators (differential or single ended).</p>	
31.	<p>Global buffer (GB) can be driven through dedicated global I/Os, CCC, or fabric (regular I/Os) routing.</p> <p>The global network is composed of GBs to distribute low-skew clock signals or high-fanout nets.</p> <p>Dedicated global I/Os drive the GBs directly and are the primary source for connecting external clock inputs (to minimize the delay) to the internal global clock network.</p> <p>For more information, see UG0449: SmartFusion2 and IGLOO2 Clocking Resources User Guide.</p>	
Reset		
32.	<p>DEVRST_N – Input</p> <p>The DEVRST_N pin must have a 10 KΩ pull-up resistor. The pin must not be left floating. If a push-button switch is used to generate reset, check for switch de-bounce. For more information about DEVRST_N, see Power Supply Flow, page 12.</p>	
JTAG		
33.	<p>In the JTAG interface, the VDDI bank supply must be powered up for programming. The following is a list of pins available for different activities:</p> <ul style="list-style-type: none"> – JTAGSEL: Low (pull-down) > ARM Cortex-M3 JTAG; High (pull-up) > FPGA fabric JTAG. – TMS: Internal weak pull-up resistor. – TCK: External pin. Should be pulled-down through 1 KΩ resistor. There is no internal pull-up resistor for this pin. – TDI: internal weak pull-up resistor. – TDO: no internal pull-up resistor. – TRSTB: internal weak pull-up resistor. <p>An FP4 or FP5 header (10 pin – 2.54 mm pitch) can be used to connect to FlashPro4 or FlashPro5.</p> <p>For more information about JTAG, see Figure 11, page 24 and Table 15, page 23.</p>	

Table 23 • Design Checklist (continued)

S.No.	Checklist	Yes/No
Programming		
34.	<p>The device can be programmed either through JTAG interface or serial peripheral interface (SPI) interface.</p> <p>FLASH_GOLDEN_N If pulled low, it indicates that the device is to be re-programmed from an image in the external SPI flash attached through the SPI interface. If pulled high, the SPI is put in slave mode. Add a 10kΩ external pull-up resistor to VDDI. Some devices do not support the FLASH_GOLDEN_N pin. Check the <i>PPAT spreadsheets</i> available on the following Microsemi webpages: SmartFusion2 SoC FPGA Documentation IGLOO2 FPGA Documentation For more information about dedicated pins including Flash_GOLDEN_N, see Table 16, page 25.</p>	
Configuring Pins in Open Drain Using Tri-state Buffer		
35.	<p>To configure fabric pins in open-drain mode, the tristate buffer input pin must always be grounded, and the I/O pin of the FPGA must be connected to the active-low enable pin of the buffer. For more information, see Figure 22, page 36.</p>	
SerDes Pins		
36.	<p>Dedicated I/O are available for the SerDes high-speed serial interface, which supports the PCIe, SGMII, XAUI, and JESD204B protocols.</p> <p>SERDES Clock: 100 MHz to 160 MHz LVDS source. The SerDes reference clock pins have internal on-die termination (ODT) settings. These settings can be enabled through the Libero software. The reference clock source (differential clock oscillator) is selected based on many parameters such as frequency range, output voltage swing, jitter (deterministic, random, and peak-to-peak), rise and fall times, supply voltage and current, noise specification, duty cycle, duty cycle tolerance, and frequency stability. An example clock source can be the CCLD-033- LVDS clock oscillator. SerDes clock requirements for different protocols are as follows:</p> <ul style="list-style-type: none"> – PCIe: 100 MHz – XAUI: 156.25 MHz – SGMII: 125 MHz – EPCS: 125 MHz <p>– SERDES TXD: The transmit pair must alone have AC-coupling capacitors near the SmartFusion2/IGLOO2 device. AC-coupling capacitors of 75-200 nF are required for link detection. If the SerDes unit is unused, these pins must remain floating (DNC).</p> <p>– SERDES RXD: The receive pair must have AC-coupling capacitors near the endpoint device. If the SerDes unit unused, these pins must always be connected to ground.</p> <p>For more information about SerDes, see SerDes, page 41.</p>	

Table 23 • Design Checklist (continued)

S.No.	Checklist	Yes/No
DDR Interface		
37.	<p>DDR Interface</p> <p>Short DDR TMATCH IN to DDR TMATCH OUT.</p> <p>Short DDR TMATCH ECC IN to DDR TMATCH ECC OUT.</p> <p>VDDI bank supply should be powered as per the application:</p> <ul style="list-style-type: none"> – For LPDDR - VDDI should be 1.8 V – For DDR2- VDDI should be 1.8 V – For DDR3- VDDI should be 1.5 V <p>DDR impedance calibration pin should be pulled down with the following resistors:</p> <ul style="list-style-type: none"> – For LPDDR- 150 Ω – For DDR2- 150 Ω – For DDR3- 240 Ω <p>Though calibration is not required, it is recommended to use corresponding resistor placeholder to connect the pin to the ground with or without a resistor.</p> <p>All data and data strobe signals have internal ODT settings, which can be enabled through the Libero software.</p>	
Hot-swapping and Cold-Sparing		
38.	<p>All user I/Os have internal clamp diode control circuitry for protection.</p> <p>MSIO pins (except PCI 3.3 V standard) support the hot-swapping and cold-sparing operations. MSIOD and DDRIO pins do not support hot swapping and cold-sparing operations</p>	
General Guidelines		
39.	For all MSIO, MSIOD, and DDRIO, a weak internal pull-up resistor is available. In unused condition, these pins can be left floating.	
40.	MSIOD and DDRIO support a maximum of 2.5 V. MSIO supports maximum of 3.3 V.	
41.	<p>There is one MSI special pin (MSIO) available that can be used as input only. This pin is differentially paired with FLASH_GOLDEN_N, which is always input only.</p> <p>For more information, see the following documents:</p> <ul style="list-style-type: none"> – IGLOO2 Pin Descriptions – SmartFusion2 Pin Descriptions 	
42.	One internal signal can be allocated for probing (for example, towards the oscilloscope feature). The two live probe I/O cells are dual-purpose. They can be used for the live probe functionality or used as user I/Os (MSIO).	
43.	MSS peripherals (SPI, I2C, USB, and UART) are available.	
44.	Provide pull-up resistors for all open-collector or open-drain pins, even if a pin is not used.	
45.	Provide separate pull-down resistors for all used open-emitter or open-source pins.	
46.	Enable internal pull-up/pull-down resistor option for all tri-state nets through the Libero tool.	
47.	Ensure that all the critical signals on the board are terminated properly.	
48.	Terminate the unused interface signals properly to avoid metastability and electromagnetic interference (EMI)/electromagnetic compatibility (EMC) problems.	

Table 23 • Design Checklist (continued)

S.No.	Checklist	Yes/No
49.	Provide a sufficient number of ground pins for board-to-board connectors to ensure signal integrity (SI) across connectors. Dense board-to-board connectors may cause severe cross-talk problems. The severity of crosstalk depends on the frequency of the signal and the spacing between signal pins on the connectors. (The number of ground pins may be obtained after performing SI analysis.) The severity can be reduced by providing ground pins between signal pins.	
50.	Use proper voltage-level translator devices for interfacing higher-operating-voltage devices with lower-operating-voltage devices.	
51.	Perform timing analysis of all components, taking into consideration the delays introduced by buffers in the data, address, or control paths.	
52.	Perform signal integrity analysis (pre-layout and post-layout) for all critical interfaces and all types of I/Os using input/output buffer information specification (IBIS).	
53.	Analyze the design for simultaneous switching noise (SSN) problems: – Use differential I/O standards and lower-voltage standards for high switching I/Os. – Reduce the number of simultaneously switching output pins within each bank. – Reduce the number of pins that switch voltage levels at the same time. – Use lower drive strengths for high switching I/Os. The default drive strength setting might be higher than the design requirement. – Spread output pins across multiple banks if possible. – If bank usage is substantially below 100%, spread the switching I/Os evenly throughout the bank to reduce the number of aggressors in a given area to reduce SSN. – Separate simultaneously switching pins from input pins that are susceptible to SSN.	
54.	Place important clock and asynchronous control signals near ground signals and away from large switching buses.	
55.	I/O Pin Assignment Use a spreadsheet to capture the list of design I/Os. Microsemi provides detailed pinout information that can be downloaded from the website and customized to store the pinout information for specific designs. Pinout details for various packages with different densities are available on the following pages: SmartFusion2 SoC FPGA Documentation IGLOO2 FGPA Documentation	
56.	Check if there are any incompatible I/O standards combined in the same bank.	
57.	Check if there are two interfaces with different voltage standards in the same bank.	
58.	See the bank location diagrams in the IGLOO2 Pin Descriptions / SmartFusion2 Pin Descriptions documents to assess the preliminary placement of major components on PCB.	

5.3 Layout Checklist

The following table lists the layout checks.

Table 24 • Layout Checklist

S.No.	Description	Yes/No
Power		
1.	Are 0402 or lesser size capacitors used for all decaps (less than value?)	
2.	Are power supply filters implemented on SERDES_x_VDDAPL, and SERDES_x_PLL_VDDA as shown in the Figure 28 , page 42 and Figure 40 , page 50 respectively?	
3.	Is precision 1.2 K resistor between SERDES_x_REFRET and SERDES_x_REXT used?	
4.	Are placement and layout guidelines followed for 1.2 K resistor?	
5.	Is the target impedance met on all power planes?	
6.	Are VREF planes for DDRx reference supply isolated from the noisy planes?	
7.	Are enough number of decoupling capacitors used for DDRx core and VTT supply? For more information about DDRx core and VTT supply, see Board Design Guidelines for SmartFusion2 SoC and IGLOO2 FPGAs , page 4.	
8.	Is one 0.1 μ F cap for two VTT termination resistors used for DDRx?	
9.	Is enough plane width provided for VTT plane?	
DDR3		
10.	Are length match recommendations followed according to the DDR3 guidelines?	
SerDes		
11.	Are length match recommendations followed according to the SerDes guidelines?	
12.	Are the DC blocking capacitors used for SerDes TX and if required on RX lines?	
13.	Is tight controlled impedance maintained along the SerDes traces?	
14.	Are differential vias well designed to match SerDes trace impedance?	
15.	Are DC blocking capacitor pads designed to match SerDes trace impedance?	
Dielectric Material		
16.	Is proper PCB material selected for critical layers?	

6 Appendix: Special Layout Guidelines - Crystal Oscillator

The placement of the crystal needs to be close to the SmartFusion2 or IGLOO2 device. Two capacitors are to be placed symmetrically around the crystal so that the lengths from the crystal pad to capacitor are equal, as shown in the following figure. Two traces from crystal to SmartFusion2/IGLOO2 should have equal lengths.

Figure 86 • Layout of the Crystal Oscillator


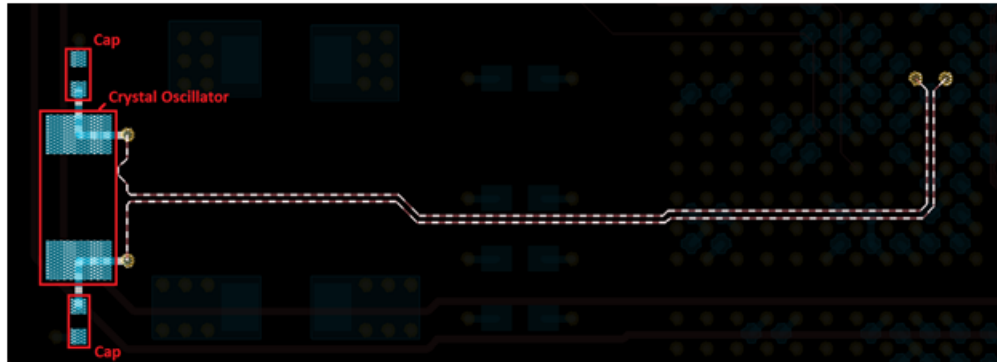


Figure 87 • Schematics of Crystal Oscillator

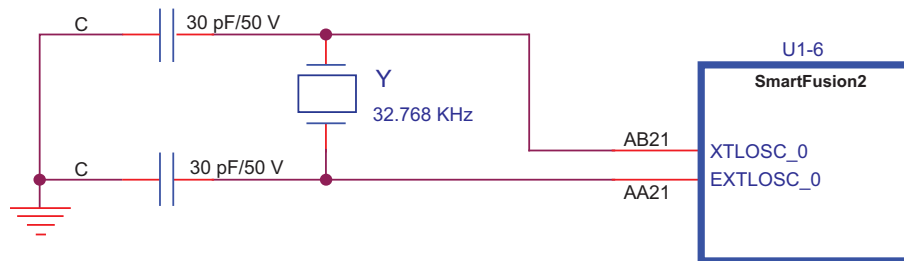

7 Appendix: Stack-Up

A good stack-up leads towards better performance. The number of layers in the stack-up is dependent on many factors such as form factor of the board, number of signals to be routed, and power requirements. Therefore, the designer chooses how many layers the board requires. The SmartFusion2 Development Kit/IGLOO2 Evaluation Kit has 16-layer stack-up, as shown in [Figure 88](#), page 92.

Note: All the guidelines in this document are with respect to 16-layer board stack-up.

Utilizing upper power layers should be used for high priority supplies. High-switching current supplies should be placed vertically closer to the devices to decrease the distance the currents need to travel through vias. Ground planes are placed adjacent to the high transient current power planes to reduce inductance and couple the high-frequency noise.

It is good to have power and ground layers on side-by-side layer. The benefits of this inter-plane capacitance provide better decoupling at high frequencies. The effect of via on power pins is reduced by having a power plane near the device.

Signal integrity depends on how well the traces have controlled impedance, so it is always recommended to have controlled impedance.

















Microsemi recommends that all critical high-speed signals like DDR and PCIe signals need to have ground reference. All signal layers should be separated from each other by ground or power planes. This minimizes crosstalk and provides balanced and clean transmission lines with properly controlled characteristic impedance between devices and other board components.

Best performance is obtained when using dedicated ground plane layers that are continuous across the entire board area. Power planes can provide adequate reference, however, the power planes should be related to the signals they serve to reference.

Note: Refrain from using unrelated power planes as a signal reference.

Slots should not interrupt the planes, or else they can possibly force current to find an alternate return path. This undesired return path could cause a localized bounce on the power or ground plane that can possibly be capacitive coupled to all signals adjacent to the planes.

Figure 88 • Stack-up Used in Development Board

Lamination Stack-up:			Thickness and Tolerance:		Base Material Requirements:	
L#/Type:	Description:		Cu+:	Lamination/PrePreg:	Type:	Description:
1 Mix		Core 0.0040 Q/H	.00035	.0040		NP 4000-13EP
2 Pin			.00060			
3 Mix		Pre-Preg (1 x 2113)		.0034		NP 4000-13EP
4 Pin		Core 0.0035 H/H	.00060	.0035		NP 4000-13EP
5 Mix		Pre-Preg (1 x 2113)		.0034 +/- 0.0003		NP 4000-13EP
6 Pin		Core 0.0035 H/H	.00060	.0035		NP 4000-13EP
7 Mix		Pre-Preg (1 x 1080)		.0022 +/- 0.0002		NP 4000-13EP
8 Pin		Core 0.0030 1/H	.00120	.0030		NP 4000-13EP
9 Mix		Pre-Preg (1 x 1080)		.0026 +/- 0.0003		NP 4000-13EP
10 Pin		Core 0.0030 H/1	.00060	.0030		NP 4000-13EP
11 Mix		Pre-Preg (1 x 1080)		.0023 +/- 0.0002		NP 4000-13EP
12 Pin		Core 0.0035 H/H	.00060	.0035		NP 4000-13EP
13 Mix		Pre-Preg (1 x 2113)		.0034 +/- 0.0003		NP 4000-13EP
14 Pin		Core 0.0035 H/H	.00060	.0035		NP 4000-13EP
15 Mix		Pre-Preg (1 x 2113)		.0034 +/- 0.0003		NP 4000-13EP
16 Pin		Core 0.0040 H/Q	.00060	.0040		NP 4000-13EP
			.00035			
Target Post-Lam Thickness: 0.0600 +/- 0.0030			Stack-up Notes:			
Copper Oz Legend: H = 1/2 Oz T = 3/8 Oz Q = 1/4 Oz S = 1/16 Oz			0.004 Q/H CORES MUST BE MADE OF (1 x 2116 PREG)			
			0.0035 H/H CORES MUST BE MADE OF (1 x 2113 PREG)			
			0.003 1/H CORES MUST BE MADE OF (1 x 1080 PREG)			

8 Appendix: Dielectric Material


The impedance of the traces depends on the geometry of the traces and the dielectric material used. The skew of the signal depends on the dielectric constant and loss of signal strength depends on the loss tangent of the material. The SmartFusion2 Development Kit board uses Nelco 4000-13 dielectric material. However, selection of the material is made based on the speed and length of the high-speed traces. Simulations are recommended on high-speed serial links to converge on the type of the material used.

If the total trace length is less than 20 inches with a speed at or below 3.125 Gbps, FR-4 may be acceptable. Another design option is to use low-loss dielectric PCB material, such as Rogers 4350, GETEK, or ARLON. It can provide increased eye-opening performance when longer trace interconnections are required. If longer traces or faster speed are required, consider using a high-speed material such as ROGERS 3450.

While designing for gigabit serial links, the weaving structure of PCB dielectric material should be taken into consideration. A PCB dielectric substrate is constructed from woven fiberglass fabrics strengthened and bound together with epoxy resin.

A typical weaving is shown in the following figure.

Figure 89 • Fiberglass Weaving¹

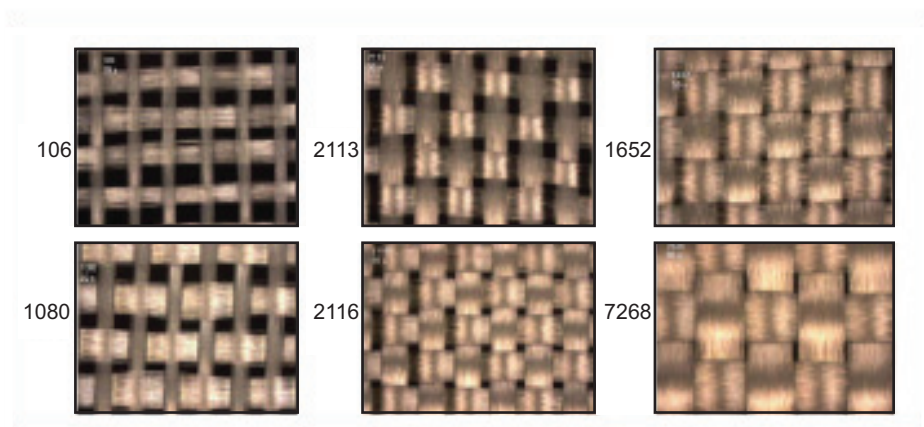


Depending on the density of weaving, the PCB materials are numbered as 106, 1080, 2113, 2116, 1652, and 7268. Trace routed on the PCB is non-homogeneity in dielectric constant due to weaving. This causes discontinuities in the trace impedance, which results in improper eye-opening at the receiving end. For further reading, refer to the [Solving PCB Fiber Weave Issues](#).

1. signal-integrity.tm.agilent.com/2011/pcb-fiber-weave

9 Appendix: Power Integrity Simulation Topology

The following figure shows the topology that is considered for simulating the power plane for power integrity analysis.

Figure 90 • Power Integrity Simulation Topology

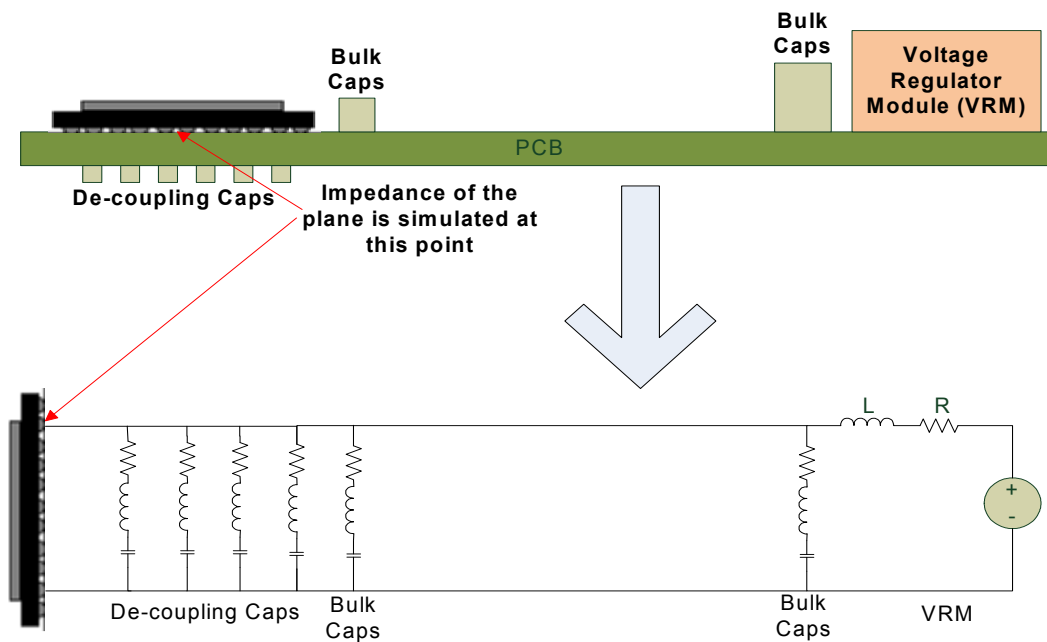

Note: Package parameters of SmartFusion2 are not considered for simulations.