

PARTS LIST

CAPACITORS – AXIAL CERAMIC RATED 16V OR HIGHER

4 x 47pF (*usually marked 47 or 470*)
2 x 47nF (*usually marked 47n or 473*)
18 x 100nF (*usually marked 100n or 104*)
1 x 1uF (*usually marked 1u or 105*)
1 x 22μF (*axial electrolytic rated 25V*)

RESISTORS – ALL ¼W 5% OR BETTER (4 BAND RESISTOR COLOUR CODES SHOWN)

2 x 75Ω	
1 x 180Ω	
1 x 330Ω	
1 x 470Ω	
2 x 680Ω	
12 x 1KΩ	
3 x 2.2KΩ	
1 x 4.7KΩ	
7 x 10KΩ	
1 x 220KΩ	
1 x 1MΩ	

SEMICONDUCTORS


9 x 1N4148 diode
1 x BC548B or similar NPN transistor
2 x 74HC00
1 x 74HC02
1 x 74HC04
2 x 74HC08
1 x 74HC11
2 x 74HC32
2 x 74HC74
1 x 74HC86
1 x 74HC165
1 x 74HC251
3 x 74HC257 (marked 257)
2 x 74LS257 (marked LS257, nearest keyboard)
1 x 74HC373
2 x 74HC393
1 x Z80 CPU Z84C0008PEG
1 x 7805 or 7805 switching replacement (rated at least 100mA, more if using expansion port)
1 x 27C256 Programmed EPROM
1 x 62256 32K SRAM 600mil wide
1 x 6.5 MHz Crystal (HC-49/U package)

CONNECTORS / SWITCHES

2 x Stereo 3.5mm Jack
1 x Phono jack
1 x 2.1 mm DC Jack
1 x miniature tactile switch 6x6mm (*for reset*)
40 x miniature tactile switch 6x6mm, 7mm high (*for keyboard*)
2 x 2 way and 7 x 3 way headers with jumper (*optional or wire links*)
2 x 23 or 2x2 and 2x20 socket (*for expansion port, if required*)
2 x 28pin, 1 x 40pin IC sockets
14 x 14pin, 7 x 16pin, 1 x 20pin IC sockets (*optional, not included*)

Tynemouth Software

COMPONENT PLACEMENT

 

JUMPERS

Jumpers or link wires need to be fitted to each of the jumper blocks. The positions shown above are the default configuration of centre negative supply, normal PAL video, top ROM address, normal border and NMI slow mode enabled.

Jumper		
Slow Mode	ZX81 style Fast / Slow mode	ZX80 style permanent Fast mode
Normal / Inverse	Normal (black on white) video	Inverse (white on black) video
Normal / Greyborder	Normal, border same as background	Grey crosshatch border
PAL / NTSC	PAL 50 Hz refresh rate	NTSC 60 Hz refresh rate
A15	High (5V) on ROM pin 1	Low (0V) on ROM pin 1
A14	High (5V) on ROM pin 27	Low (0V) on ROM pin 27
A13	High (5V) on ROM pin 26	Low (0V) on ROM pin 26

If in doubt, set all ROM jumpers to High, and repeat the 8K ROM image to fill up your EPROM.


The jumpers near the power connector set the polarity of the power input

	Centre negative, used by ZX Spectrum and Commodore 16 computers
	Centre positive, used by pretty much every other power supply

Power requirements are 9V DC. Current consumption is around, more if you plan to use the expansion port.


Tynemouth Software

COMPONENT DESIGNATORS

 


SCHEMATIC

 The first part of the schematic shows the Z80 and two expansion connectors (wired in parallel). A simple RC circuit provides a reset pulse. BUSRQ is the only input not used, so that is tied high. NMI and HALT are driven directly, and A6 is connected to the IRQ pin, and so none of these are not suitable for external inputs.



The databus is split as part of the display generation circuitry, using eight 1K resistors. The alternate databus is fed to the expansion connector. This allows the Z80 to see NOP operations and clock through the address space whilst the display circuitry is processing character data.


R11-18 8x 1K

 


Tynemouth Software

INPUT PORT

The IO decoding is fairly minimal. There is a single input port which is decoded only with A0, so it can be read on any address where A0 is low, all even numbered addresses. The input port is implemented using two multiplexor chips. These are shared with the NOP generator as both need to write to the CPU data lines. If a NOP is required, all the lines are connected to 0V which generates the opcode for NOP. If the keyboard is being read, the databus is connected to the input port. When neither are in use, the output of the multiplexor chips are set to high impedance.

 

 
The keyboard is read using bits 0-4 of the input port. There are five column lines, which are pulled high normally. When the keyboard is being scanned, the upper eight address lines are set so that one is low at a time. If a key is pressed on the 5x8 crosspoint keyboard on that row, the column line reads low.




Bit 5 of the input port is not used, it will always read as a 1.

Bit 6 of the input port is used for PAL/NTSC selection, low for NTSC, high for PAL.

 Bit 7 of the input port is used for cassette input. Data storage uses a cassette recorder (or these days a smart phone app). The cassette output uses the output of the VSync flip flop. This does not contain any horizontal sync pulses, so is cleaner than the original design which used the composite sync.




 When a read operation to the keyboard port occurs, this sets the VSync flip flop to generate the VSync pulse. Any IO write operation clears it again. When NMI mode is active, this mechanism is disabled to avoid unwanted sync pulses.




OUTPUT PORTS

 Ports 0xFE and 0xFD are used to control the slow mode. Writing to port 0xFE activates slow mode, writing to port 0xFD disables it again. If the jumper is set high this will create a NMI pulse when there is an HSync pulse. There is some additional logic which ensures the CPU is in the correct T state, WAIT will be pulled low (active) when HALT is high (inactive) and NMI is low (active).




ADDRESS MULTIPLEXING

 
The ROM address during normal read operations is switched to the CPU address bus, but during display generation, the address is composed of multiple parts. A spare gate on the multiplexor is used to form a logic gate to generate a signal when MREQ is low or Refresh is low. A second spare gate is used to delay the A15 line slightly to avoid a timing glitch.



 The lower three bits are generated from a line counter, this counts up each line, and is reset on a vertical sync so it is always on line 0 at the start.



 
Bits 3-8 are set based on the character currently being displayed, which is latched when data is valid at the start of the next cycle. The last gate of the multiplexor is again used as a logic gate to generate the latch signal when refresh is low, the clock is low and MREQ is high.




Tynemouth Software

RAM AND ROM

The address decoding use an 8 input multiplexor, controlled by the upper three address lines. This selects the RAM_CS for the address range split into eight 8K blocks. When the selected input is low, the RAM is enabled, and when high, the ROM is enabled. The 2K2 resistors hold both ROM and RAM disabled when not in a memory request or refresh cycle (i.e. the screen is being drawn). The 680Ω resistors allow the RAM_CS and ROM_CS lines to be overridden from the expansion port. The 10K resistor holds the RAM write line high, to put the chip in read mode when not being driven by the CPU. This allows it to be accessed during the refresh cycle when the screen is being drawn, a technique used for high resolution graphics.

 

 The ROM is wired for the selected 8K block. ROMs larger than 8K can be used with multiple banks being selected by jumpers on the ROM A13, A14 and A15 pins. In most cases, these can be all set high.



The memory map this creates is as follows, the 8K ROM, mirrored in the upper address space, and 32K RAM with the mirror at the top of RAM used for the display file.

Address Range	Use
0000-1FFF	ROM
2000-3FFF	RAM
4000-5FFF	RAM
6000-7FFF	RAM
8000-9FFF	RAM
A000-BFFF	ROM
C000-DFFF	RAM (during M1)
E000-FFFF	RAM (during M1)

16K of this is available to BASIC, and located where the normal 16K RAM pack would be, where most software would expect it (4000-7FFF).

