
The State of Hollow State Audio

in the Second Decade of the 21st Century



Richard A. Honeycutt



an Elektor Publication

LEARN > DESIGN > SHARE

Table of Contents

Chapter 1 • Origins and Destination of Hollow-State Audio	12
Introduction	12
Radio	12
Phonographs	15
Television	19
Other Markets	20
The Birth of Hollow-State Electronics	21
Early Tubes	21
Triodes	22
Tetrodes	23
Pentodes	24
Modern Tube Filaments and Envelopes	25
New Life for Vacuum Tube Technology	25
Chapter 2 • Basics of Hollow-State Electronics	27
Hollow-State Amplifiers	27
Vacuum Tube Biasing	29
Voltage Gain of Amplifier Stages	31
The Frequency Response of Hollow-State Amplifiers	33
Frequency Response Goals	34
Low-Frequency Response	35
High-Frequency Response	38
Hollow-State Power Amplifiers	39
Single-Ended Class-A Amps	40
Push-Pull Triode Amplifiers	42
Choices: Single-ended or Push-Pull; Triodes or Pentodes?	43
Achieving Higher Efficiency with Class AB and B Amplifiers	44
Class B Operation	44
Transformer-Coupled Push-Pull	44
Phase Splitters—Paraphase	45
Differential Amplifier (Long-Tailed Pair)	45
Single Triode or Split-Load Phase Inverter	47
Biasing and the AB Classes	48
Feedback	48
Complete Push-Pull Power Amplifier	50
Chapter 3 • Commercial Hollow-State Power Amplifiers	52
Classic Tube Power Amplifier Circuits	51
Knight 10-W Amplifier	53
Heathkit W5M	54
Fisher Model 70	55
Dynaco Mark II	56

McIntosh MC75	58
Pro Tube Power Amplifier Circuits	60
Western Electric's Early Days	60
RCA's Early Days	63
DuKane	65
Altec Lansing	67
Chapter 4 • Designing Hollow-State Preamplifiers	70
Controlled-Source Theory in Hollow-State Design	70
Ideal Current Sources	70
Controlled Sources	72
Active Loads	74
Designing Hollow-State Triode Audio Preamplifiers	75
Tube Choices	76
Tube Characteristics	77
Load Line	79
Capacitor Values	81
Linearity in Audio Preamplifiers	82
Grid-Current Limiting	84
Determining Distortion	85
Phonograph Preamplifiers	89
Dealing with Low Frequencies	89
Standardized Equalization	90
Phonograph Pickups	91
Power Supply Considerations	93
Tube-Type Microphone Preamplifiers	94
Mixers	94
Portable Racks	96
Modern Tube Microphone Preamps	97
Incorporating Triodes	100
Reflected Plate Amplifier	101
Starved Amplifier Operation	103
Triode Amplifiers	104
Low Control-Grid Voltages	106
Adding a Dual Op-Amp	109
Applying Starved Design to Pentodes	111
Space-Charge Tubes and Their Applications	111
Types of Space-Charge Tubes	112
A Project to Familiarize Ourselves with Design Using Space-Charge Tubes	116
The Power Supply	116
Control-Grid Bias	117
Grid-Leak Biasing	120
Changing Triodes	120
Input Resistance	121
Increasing the Input Resistance by Going Hybrid	122
Bias Adjustment	124
Modifying the Circuit to Accommodate Parts-Supply Issues	125

Chapter 5 • Vacuum Tube Characteristics and Load Lines	128
Finding Information on Vacuum Tubes	128
Data Sheets	128
Typical Operation	131
Plate and Transfer Characteristic Curves	133
Dependence of Parameters on Plate Current	133
Selecting the Operating Point for a Hollow-State Amplifier	136
First Steps.	136
Optimizing the Q-Point	138
AC Load Lines	139
Predicting Performance	140
Pentodes and Screen-Grid Voltages	145
Chapter 6 • The “Tube Sound”	147
Understanding Nonlinear Distortion	147
Introduction	147
Nonlinearity.	147
Modulation Distortion	147
Timbre	148
Perception of Distortion.	148
Frequency Response Graphs	149
Solid-State Amplifiers	149
The Great Debate.	150
Overdriving Amplifiers	150
How do different Amps distort differently?	152
Introduction	152
Distortion signatures	152
Perceptibility of Distortion	157
Other Possible Determinants of “Tube Sound”—Damping Factor	158
A Magical “X” Factor”?	159
Differences in Amp Sound: how do we find the Truth? (Investigations)	159
Accuracy or Pleasantness?.	159
Subjective Evaluation	160
Program Material	161
Test Procedures	163
Differences in Amp Sound—what is the Truth? (Results)	166
The Great Debate: Origin and Analysis	166
The Gold Standard of Testing.	166
Differences in Distortion Spectra	167
A/B/X Testing	167
Audio Pro’s Challenge	168
The Search Continues.	169
Choosing a Side.	170

Chapter 7 • Power Supplies for Hollow-State Audio Equipment	172
Overview, Transformers, Rectifiers	172
Sections of the Power Supply.	172
Power Transformers	173
Rectifiers.	176
Voltage Doublers.	179
Half-Wave Doubler	179
Full-Wave Doubler	180
Output Waveforms and Voltage Regulation	181
Power Supply Design	185
Filament Supply.	187
Sample Power Supply Design	188
Setting Specifications	188
Rectifier Type and Transformer Voltages and Currents	190
Filter Capacitor, Resistor, and Inductor Values	190
Bias Supply	192
Troubleshooting Power Supplies for Hollow-State Equipment	194
Blown Fuses	195
Low or Distorted Audio	199
Hum	199
Complete Failure to Operate	200
Chapter 8 • Selecting Tube Types.	201
Which Tube for Which Purpose?	201
Pre-WWII	201
Miniature Tube Types Introduced	203
Octal Triodes that are Still Available	205
Pentodes.	205
Which Power Tube for Which Purpose?	206
Triodes, Tetrodes, Pentodes	206
Beam Power Tubes	206
Power Triodes	214
Comparing Hollow-State Rectifiers	216
History	216
Specifications and Variations	216
Swapping Rectifier Tubes	220
Chapter 9 • Output Transformers	224
Introduction	224
Why Transformer-Couple the Output?	224
Description and Theory of Operation.	224
Specifying Output Transformers	226
Ideal and Real Output Transformers	226
Design Parameters: the Physics and Construction of Transformers	228

Chapter 10 • Tone Controls	233
The Introduction and Development of Tone Controls	233
Tone Switches	233
Electrical Filter Types	233
“One-Knob” Continuous Tone Controls	236
“Two-Knob” (Bass/Treble) Tone Controls	236
Tone Controls: Yes or No?	237
Midrange Controls in Instrument Amps, but Not in Home-Stereo Amplifiers	238
Guitar-Amp Tone Stacks	238
More on Loudness Controls	241
Chapter 11 • Dynamics Processing with Tubes	245
What is “Dynamics Processing?”	245
Operating Parameters of Dynamics Processors	247
Effects of Dynamics Processing	248
Classic Hollow-State Dynamics Processing Approaches	251
Voltage-Controlled Attenuators	251
Voltage-Controlled Amplifiers	253
Compressor Controls	257
Chapter 12 • Hollow-State Guitar Amplifiers	258
The Development of Tube Guitar Amplifiers	258
History	258
Circuitry	261
The Tone Character of Tube Guitar Amplifiers	265
Fundamentals and Harmonics	265
The Effect of the Speaker	266
Tone Controls	268
In Which Stage Does Clipping First Occur?	274
Distortion in Tube Guitar Amplifiers	275
When the Public Developed a Taste for Distortion	275
The Basics of Distortion	277
Effects of Guitar-Amp Design on Distortion Sound	281
Preamp	282
Tone Controls	283
Driver	283
Phase Splitter	285
Push-Pull Output Stage	286
Output Transformer	286
Overdriving the input	288
A Solid-State Comparison	290
Conclusion	291

Chapter 13 • Hollow-State Capacitor Microphones	292
Design and Development	292
Tube Impedance Translators for Capacitor Mics.	306
Chapter 14 • Troubleshooting Hollow-State Equipment	312
Elementary: What are the Symptoms?	312
Sherlock	312
Looking at it	316
Deeper and deeper.	318
Troubleshooting the Tough Ones	319
Divide and Conquer	319
Testing Tubes	326
Continuity Testers	326
Emission Testers	326
Mutual Conductance Testers	332
Dynamic Conductance Tester.	333
DC and AC Parametric Testers	333
Appendix A • Resources (in Order Referenced in Text).	335
Appendix B • Tube Data Sheets	336