

The Book of 555 Timer Projects

Over 45 Builds for the Legendary 555 Chip
(and the 556, 558)



Dogan Ibrahim

The Book of 555 Timer Projects

**Over 45 Builds for the Legendary
555 Chip (and the 556, 558)**



Dogan Ibrahim

-
- This is an Elektor Publication. Elektor is the media brand of

Elektor International Media B.V.

PO Box 11, NL-6114-ZG Susteren, The Netherlands

Phone: +31 46 4389444

- All rights reserved. No part of this book may be reproduced in any material form, including photocopying, or storing in any medium by electronic means and whether or not transiently or incidentally to some other use of this publication, without the written permission of the copyright holder except in accordance with the provisions of the Copyright Designs and Patents Act 1988 or under the terms of a licence issued by the Copyright Licensing Agency Ltd., 90 Tottenham Court Road, London, England W1P 9HE. Applications for the copyright holder's permission to reproduce any part of the publication should be addressed to the publishers.

- **Declaration**

The authors and publisher have used their best efforts in ensuring the correctness of the information contained in this book. They do not assume, and hereby disclaim, any liability to any party for any loss or damage caused by errors or omissions in this book, whether such errors or omissions result from negligence, accident or any other cause.

- **ISBN 978-3-89576-624-4** Print

ISBN 978-3-89576-625-1 eBook

- © Copyright 2024 Elektor International Media

www.elektor.com

Prepress Production: D-Vision, Julian van den Berg

Editor: Jan Buiting, MA

Printers: Ipskamp, Enschede, The Netherlands

Elektor is the world's leading source of essential technical information and electronics products for pro engineers, electronics designers, and the companies seeking to engage them. Each day, our international team develops and delivers high-quality content - via a variety of media channels (including magazines, video, digital media, and social media) in several languages - relating to electronics design and DIY electronics. www.elektormagazine.com

Contents

Preface	8
Chapter 1 • Introduction	10
1.1 Overview	10
1.2 Types of 555 timer chips	10
1.3 555 timer chip specifications	10
1.3.1 The NE555P chip	10
Chapter 2 • Operation of the 555 Timer Chip	13
2.1 Block Diagram	13
2.2 Astable Circuit Operation	13
2.2.1 Using a nomogram	16
2.2.2 555 astable online calculator	17
2.2.3 Astable circuit with duty cycle less than or equal to 50%	19
2.2.4 Astable circuit with duty cycle adjustable from 0% to 100%	21
2.2.5 Component values for required frequency and duty cycle range	22
2.2.6 A simpler circuit for 50% duty cycle	24
2.3 Monostable Circuit Operation	26
2.3.1 Using a nomogram	28
2.3.2 555 monostable online calculator	28
2.4 Bistable Circuit Operation	29
2.4.1 Using the Reset input	29
2.4.2 Using pins 2 and 6	30
2.5 Online Calculator Program for Designing 555 Astable and Monostable Circuits	31
2.6 555 Timer Output Current	31
2.7 Driving Heavy Loads	32
2.7.1 Using bipolar transistors	32
2.7.2 Using a MOSFET transistor	32
2.7.3 Using a relay	33
Chapter 3 • 555 Timer Projects	34
3.1 Overview	34
3.2 Project 1: Flashing LED	34

3.3 Project 2: Police Car Emergency Lights — Alternately Flashing Two LEDs	36
3.4 Project 3: Changing the LED Flash Rate	38
3.5 Project 4: Changing the LED Brightness	40
3.6 Project 5: Touch Sensor On/Off Switch.	43
3.7 Project 6: Pushbutton On/Off switch	45
3.8 Project 7: Switch-Off Delay.	46
3.9 Project 8: Switch-On Delay	48
3.10 Project 9: Light-dependent Sound	49
3.11 Project 10: Darkness Sensor.	52
3.12 Project 11: Light Sensor	54
3.13 Project 12: Astable Frequency Generator	55
3.14 Project 13: Tone Burst Generator.	57
3.15 Project 14: Drawer/Cupboard Light Switch	59
3.16 Project 15: Long Duration Timer with Decade Counter	60
3.17 Project 16: Long Duration Timer with Binary Counter.	63
3.18 Project 17: Chasing LEDs	64
3.19 Project 18: LED Roulette Game	67
3.20 Project 19: Simple Traffic Lights Controller	69
3.21 Project 20: Professional Traffic Lights Controller	71
3.22 Project 21: Sine Wave Output	73
3.23 Project 22: Continuity Tester.	76
3.24 Project 23: Simple Logic Probe	77
3.25 Project 24: Electronic Lock — Bistable Mode	79
3.26 Project 25: Electronic Lock — Monostable Mode.	81
3.27 Project 26: Extending the Monostable Duration — Retriggering	82
3.28 Project 27: Switch Contact Debouncing	84
3.29 Project 28: Schmitt Trigger Circuit.	85
3.30 Project 29: Monophonic Toy Electronic Organ	87
3.31 Project 30: 8-Tone Electronic Organ	90
3.32 Project 31: Multiple Sensor Alarm Circuit	92
3.33 Project 32: Monostable with Selectable Durations	93

3.34 Project 33: Electronic Metronome	95
3.35 DC Voltage Multipliers	97
3.35.1 Project 34: DC Voltage Doubler	97
3.35.2 Project 35: DC Voltage Tripler	99
3.35.3 Project 36: DC Voltage Quadrupler	100
3.36 Project 37: 7-segment LED Counter	100
3.37 Project 38: 2-digit, 7-segment LED Counter	105
3.38 Project 39: LED Dice	106
3.39 Project 40: 7-segment LED Dice	108
3.40 Project 41: DC Motor Control	111
3.41 Project 42: Servo Motor Control	114
3.42 Project 43: Temperature Alarm Circuit	116
3.43 Project 44: Temperature Controller	118
3.44 Project 45: DC Motor H-bridge Control	119
3.45 Project 46: Fastest Finger First Quiz Circuit — Two Participants	122
3.46 Project 47: Fastest Finger First Quiz Circuit — Six Participants in Three Groups	124
3.47 Using The 555 Timer Control Pin	126
3.47.1 Project 48: Voltage Controlled Oscillator	126
3.47.2 Project 49: Simple British Police Siren	128
3.48 Project 50: More Elaborate British Police Siren	130
Chapter 4 • The 556 and 558 Timer ICs	132
4.1 Overview	132
4.2 The 556 Timer IC	132
4.3 The 558 Timer IC	132
Chapter 5 • The CMOS Version of the 555 Timer	136
5.1 Overview	136
5.2 The LMC555 CMOS Timer	136
Chapter 6 • List of Components Used in the Projects	138
Appendix • Bibliography	139
Index	140