




Home » ROHM » ROHM TLR377GYZ Non Inverting Amplifier DC Sweep Simulation User Guide T

Contents [hide]

- 1 ROHM TLR377GYZ Non-Inverting Amplifier DC Sweep Simulation
- 2 General Cautions
- 3 Simulation Schematic
- 4 How to simulate
- 5 Peripheral Components
- 6 Recommended Products
- 7 Documents / Resources
 - 7.1 References



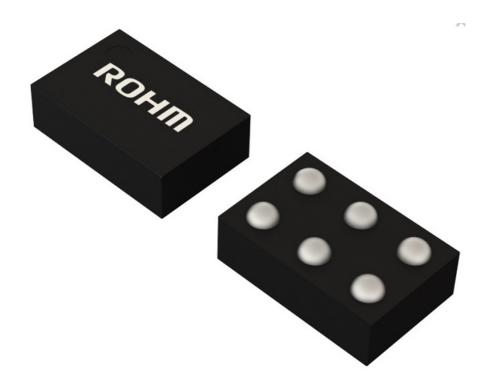ROHM TLR377GYZ Non-Inverting Amplifier DC Sweep Simulation



This circuit simulates a DC sweep response with an Op-Amp as a non-inverting amplifier. You can observe the output voltage when the input voltage is changed. You can customize the parameters of the components shown in blue, such as VSOURCE or peripheral components, and simulate the non-inverting amplifier with the desired operating condition. You can simulate the circuit in the published application note:

Operational amplifier, Comparator (Tutorial). [JP] [EN] [CN] [KR]

General Cautions

Caution 1: The values from the simulation results are not guaranteed. Please use these results as a guide for your design.

Caution 2: These model characteristics are specifically at Ta=25°C. Thus, the simulation result with temperature variances may significantly differ from the result the one done at the actual application board (actual measurement).

Caution 3: Please refer to the Application Note of Op-Amps for details of the technical information.

Caution 4: The characteristics may change depending on the actual board design, and ROHM strongly recommends double-checking those characteristics with the actual board where the chips will be mounted.

Simulation Schematic

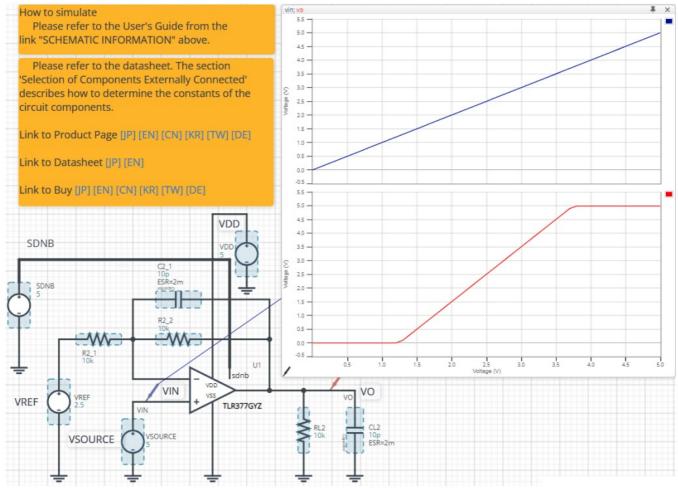


Figure 1. Simulation Schematic

How to simulate

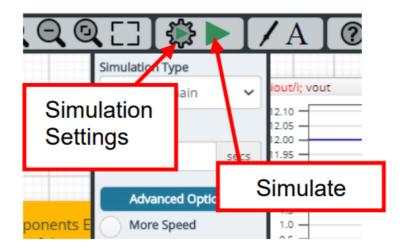


Figure 2. Simulation Settings and execution

The simulation settings, such as parameter sweep or convergence options, are configurable from the 'Simulation Settings' shown in Figure 2, and Table 1 shows the default setup of the simulation.

In case of a simulation convergence issue, you can change the advanced options to

solve it. The temperature is set to 27 °C in the default statement in 'Manual Options'. You can modify it.

Table 1. Simulation settings: default setup

Parameters	Default	Note		
Simulation Type	DC	Do not change Simulation Type		
Parameter Sweep	VSOURCE	VOLTAGE_LEVEL from 0 V to 5 V by 0.		
Advanced options	Balanced	_		
Advanced options	Convergence Assist	_		
Manual Options	.temp 27	_		

Simulation Conditions

Table 2. List of the simulation condition parameters

Instance Name	Туре	Parameters	Defaul t Valu e	Variable Range		Unit
				Min	Max	S
VSOURC E	Voltage Sour	Voltage_level	5	0	5.5	V
		AC_magnitude	0.0	fixed		V
		AC_phase	0.0	fixed		0
VDD	Voltage Sour ce For Op-A mp	Voltage_level	5	1.8 <i>(No te1)</i>	5.5(N ote1)	V
		AC_magnitude	0.0	fixed		V
		AC_phase	0.0	fixed		0
						1

		Voltage_level	2.5	VSS	VDD	V
VREF	Voltage Sour	AC_magnitude	0.0	fixed		V
		AC_phase	0.0	fixed		0
	Voltage Sour	Voltage_level	5	VSS	VDD	V
SDNB	ce For Shutd own Setting	AC_magnitude	0.0	fixed		V
		AC_phase	0.0	fixed		0

(Note 1) Set it to the guaranteed operating range of the Op-Amps.

Op-Amp model

Table 3 shows the model pin function implemented. Note that the Op-Amp model is the behavioral model for its input/output characteristics, and neither protection circuits nor functions unrelated to the purpose are implemented.

Table 3. Op-Amp model pins used for the simulation

Pin Name	Description
+IN	Non-inverting input
-IN	Inverting input
VDD	Positive power supply
VSS	Negative power supply / Ground
OUT	Output
SDNB	Shutdown setting

Peripheral Components

Bill ofMaterialsI


Table 4 shows the list of components used in the simulation schematic. Each of the


capacitors has the parameters of the equivalent circuit shown below. The default values of equivalent components are set to zero, except for the ESR of You can modify the values of each component.

Table 4. List of capacitors used in the simulation circuit

Туре	Instance Name	Default Value	Variable Range		Units
	instance maine	Delault value	Min	Max	Offics
	R2_1	10k	1k	1M	Ω
Resistor	R2_2	10k	1k	1M	Ω
	RL2	10k	1k	1M, N C	Ω
Capacitor	C2_1	10	10	100	pF
	CL2	10	free, NC		pF

Capacitor Equivalent Circuits

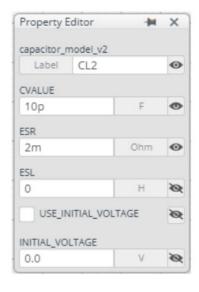

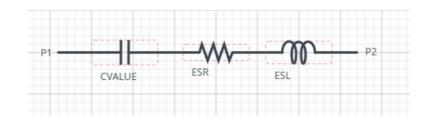

The default value of ESR is $m\Omega\Omega$.

(Note 2) These parameters can take any positive value or zero in simulation, but it does not guarantee the operation

of the IC in any condition. Refer to the datasheet to the adequate value of parameters.

Recommended Products

Op-Amp

TLR377GYZ: Ultra Small Package & High Precision Rail-to-Rail Input/Output CMOS Operational Amplifier. [JP] [EN] [CN] [KR] [TW] [DE] Technical Articles and Tools can be found in the Design Resources on the product web page.

Notice

- The information contained in this document is intended to introduce ROHM Group (hereafter referred to aasasHM products. When using ROHM products, please verify the latest specifications or datasheets before use.
- 2. ROHM products are designed and manufactured for use in general electronic equipment and applications (such as Audio Visual equipment, Office Automation equipment, telecommunication equipment, home appliances, amusement devices, etc.) or specified in the datasheets. Therefore, please contact the ROHM sales representative before using ROHM products in equipment or devices requiring extremely high reliability and whose failure or malfunction may cause danger or injury to human life or body or other serious damage (such as medical equipment, transportation, traffic, aircraft, spacecraft, nuclear power controllers, fuel control, automotive equipment including car accessories, etc. hereafter referred to as Specific Applications). Unless otherwise agreed in writing by ROHM in advance, ROHM shall not be in any way responsible or liable for any damages, expenses, or losses incurred by you or third parties arising from the use of ROHM Products for Specific Applications.
- 3. Electronic components, including semiconductors, can fail or malfunction at a certain rate. Please be sure to implement, at your responsibility, adequate safety measures, including but not limited to fail-safe design against physical injury, and damage to any property, which a failure or malfunction of products may cause.
- 4. The information contained in this document, including application circuit examples and their constants, is intended to explain the standard operation and usage of ROHM products, and is not intended to guarantee, either explicitly or implicitly, the operation of the product in the actual equipment it will be used. As a result, you are solely responsible for it, and you must exercise your independent verification and judgment in

the use of such information contained in this document. ROHM shall not be in any way responsible or liable for any damages, expenses, or losses incurred by you or third parties arising from the use of such information.

- 5. When exporting ROHM products or technologies described in this document to other countries, you must abide by the procedures and provisions stipulated in all applicable export laws and regulations, such as the Foreign Exchange and Foreign Trade Act and the US Export Administration Regulations, and follow the necessary procedures under these provisions.
- 6. The technical information and data described in this document, including typical application circuits, are examples only and are not intended to guarantee to be free from infringement of third parties intellectual property or other rights. ROHM does not grant any license, express or implied, to implement, use, or exploit any intellectual property or other rights owned or controlled by ROHM or any third parties concerning the information contained herein.

No part of this document may be reprinted or reproduced in any form by any means without the prior written consent of ROHM.

- 7. All information contained in this document is current as of the date of publication and subject to change without notice. Before purchasing or using ROHM products, please confirm the latest information with the ROHM sales representative.
- 8. ROHM does not warrant that the information contained herein is error-free. ROHM shall not be in any way responsible or liable for any damages, expenses, or losses incurred by you or third parties resulting from errors contained in this document.

Thank you for accessing ROHM product information.

More detailed product information and catalogs are available, please contact us.

ROHM Customer Support System

www.rohm.com

2023 ROHM Co., Ltd. All rights reserved.

Documents / Resources



ROHM TLR377GYZ Non Inverting Amplifier DC Sweep Simulation [pdf] U ser Guide

TLR377GYZ, TLR377GYZ Non Inverting Amplifier DC Sweep Simulation, TLR377GYZ, Non Inverting Amplifier DC Sweep Simulation, Inverting Amplifier DC Sweep Simulation, DC Sweep Simulation

References

- User Manual
- ROHM
- ▶ DC Sweep Simulation, Inverting Amplifier DC Sweep Simulation, Non Inverting Amplifier DC Sweep Simulation, ROHM, Simulation, TLR377GYZ, TLR377GYZ Non Inverting Amplifier DC Sweep Simulation

Leave a comment

Your email address will not be published. Required fields are marked*

Comment*

Name

Email

Website

Save my name, email, and website in this browser for the next time I comment.

Post Comment

Search:

e.g. whirlpool wrf535swhz

Search

Manuals+ | Upload | Deep Search | Privacy Policy | @manuals.plus | YouTube

This website is an independent publication and is neither affiliated with nor endorsed by any of the trademark owners. The "Bluetooth®" word mark and logos are registered trademarks owned by Bluetooth SIG, Inc. The "Wi-Fi®" word mark and logos are registered trademarks owned by the Wi-Fi Alliance. Any use of these marks on this website does not imply any affiliation with or endorsement.