



---

# Vanderveen Trans Tube Amplifiers



Menno van der Veen



an Elektor Publication

LEARN | DESIGN | SHARE

● This is an Elektor Publication. Elektor is the media brand of Elektor International Media B.V.

78 York Street

London W1H 1DP, UK

Phone: (+44) (0)20 7692 8344

© 2015: Menno van der Veen

First published in the United Kingdom 2015

● All rights reserved. No part of this book may be reproduced in any material form, including photocopying, or storing in any medium by electronic means and whether or not transiently or incidentally to some other use of this publication, without the written permission of the copyright holder except in accordance with the provisions of the Copyright Designs and Patents Act 1988 or under the terms of a licence issued by the Copyright Licensing Agency Ltd., 90 Tottenham Court Road, London, England W1P 9HE. Applications for the copyright holder's permission to reproduce any part of the publication should be addressed to the publishers.

● The publishers and the author have used their best efforts in ensuring the correctness of the information contained in this publication. They do not assume, and hereby disclaim, any liability to any party for any loss or damage caused by errors or omissions as a result from negligence, accident or any other cause.

● British Library Cataloguing in Publication Data

A catalogue record for this book is available from the British Library

● **ISBN 978-1-907920-34-9**

© Copyright 2015: Menno van der Veen

Translator: Kenneth Cox

Prepress Production: D-Vision, Julian van den Berg

First published in the United Kingdom 2015

Printed in the Netherlands by Wilco

149023-I/EN



Elektor is part of EIM, the world's leading source of essential technical information and electronics products for pro engineers, electronics designers, and the companies seeking to engage them. Each day, our international team develops and delivers high-quality content - via a variety of media channels (e.g., magazines, video, digital media, and social media) in several languages - relating to electronics design and DIY electronics. [www.elektor.com](http://www.elektor.com)

LEARN

DESIGN

SHARE

---

**Table of Contents**

<b>Introduction</b> . . . . .	<b>5</b>
About the Author . . . . .	.6
<b>1 Historical Background of Transconductance</b> . . . . .	<b>9</b>
<b>2 Basic Principle of Transconductance</b> . . . . .	<b>11</b>
<b>3 Why Is DC Coupling Necessary?</b> . . . . .	<b>15</b>
3-1: The prototype amplifier. . . . .	15
3-2: General characteristics of the prototype amplifier . . . . .	18
3-3: Local negative feedback over filters . . . . .	20
3-4: Why is DC coupling required? . . . . .	21
<b>4 Vanderveen Transie: DC-coupled SE Amplifiers.</b> . . . . .	<b>23</b>
4-1: Converting the one-tube amp into the Vanderveen Transie 1. . . . .	26
4-2: Measured performance of the Vanderveen Transie 1. . . . .	29
4-3: Subjective assessment of the Transie 1 . . . . .	34
4-4: A bit more power with the Transie 2. . . . .	34
<b>5 Strict Requirements for Trans</b> . . . . .	<b>37</b>
5-1: Requirements for the output transformer . . . . .	37
5-2: Requirements for the voltage-controlled current source . . . . .	39
5-3: DC coupling and autobias settings . . . . .	39
5-4: Output stage: pentode, ultra-linear or triode? . . . . .	39
5-5: Component matching . . . . .	40
<b>6 Trans Test with Opamp Current Source</b> . . . . .	<b>43</b>
6-1: Basic design with opamp current source . . . . .	43
6-2: Implementation of current source A and current sink B . . . . .	44
6-3: Active autobias circuit. . . . .	46
6-4: Trans circuit for each output tube. . . . .	47
6-5: The complete push-pull Trans amplifier. . . . .	48
6-6: Conclusion and outlook. . . . .	52
<b>7 Vanderveen Trans-30 Tube Amplifier</b> . . . . .	<b>55</b>
7-1: Basic design of the Vanderveen Trans-30 . . . . .	55
7-2: Trans circuit for each output tube. . . . .	56

7-3: Trans-30 autobias circuit. . . . .	57
7-4: The complete Vanderveen Trans-30 circuit . . . . .	59
7-5: Objective performance figures . . . . .	61
7-6: Subjective results . . . . .	65
7-7: Postscript on the Vanderveen Trans-30. . . . .	66
<b>8 A Deeper Analysis of Trans . . . . .</b>	<b>67</b>
8-1: About distortion in output transformers . . . . .	67
8-2: Is PPP an alternative to Trans? . . . . .	69
8-3: Characteristics of Trans output tubes . . . . .	72
8-4: Remarkable high-frequency behavior . . . . .	75
8-5: Local versus overall negative feedback . . . . .	78
<b>9 Epilog and Conclusions . . . . .</b>	<b>81</b>
<b>10 Appendix 10-A: Pierre Toulezet on Transformer Distortion. . . . .</b>	<b>83</b>
Appendix 10-B: Pierre Toulezet on PPP Amplifiers . . . . .	87
<b>11 References . . . . .</b>	<b>101</b>
<b>Contact Information and Resources . . . . .</b>	<b>103</b>